
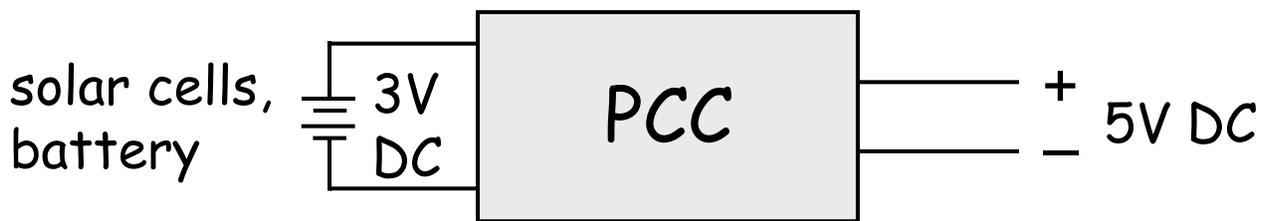


**6.002**

**CIRCUITS AND  
ELECTRONICS**

# **Power Conversion Circuits and Diodes**

# Power Conversion Circuits (PCC)

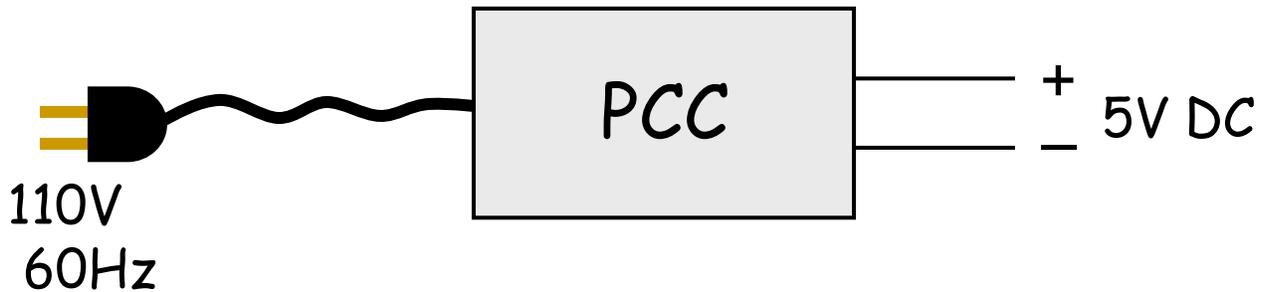

DC-to-DC UP converter


Power efficiency of converter important,  
so use lots of devices:

MOSFET switches, clock circuits,  
inductors, capacitors, op amps, diodes



**Reading:** Chapter 16 and 4.4 of A & L.

## First, let's look at the diode

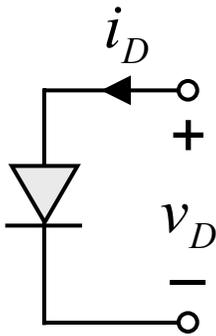



$$i_D = I_S \left( e^{\frac{v_D}{V_T}} - 1 \right)$$

$$I_S = 10^{-12} \text{ A}$$

$$V_T = 0.025 \text{ V}$$

$$V_T = \frac{kT}{q}$$

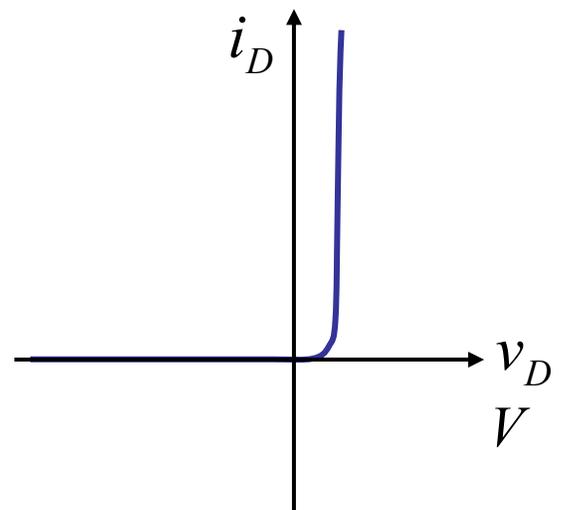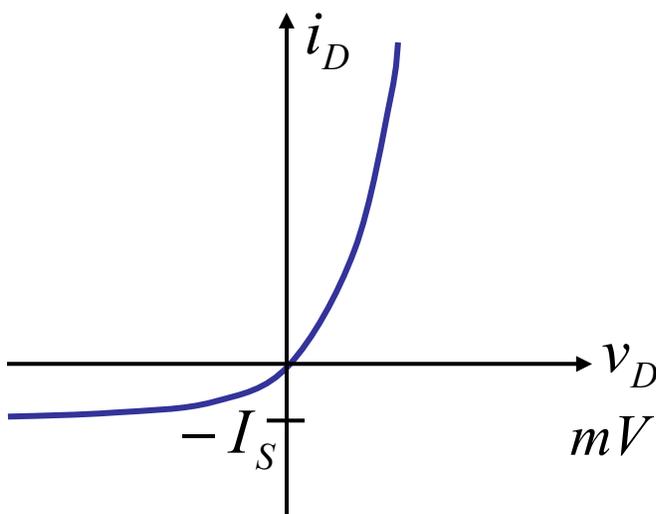$k$  → Boltzmann's constant  
 $T$  → temperature in Kelvins  
 $q$  → charge of an electron




Can use this exponential model with analysis methods learned earlier

- analytical
- graphical
- incremental


(Our fake expodweeb was modeled after this device!)

# Another analysis method: piecewise-linear analysis

P-L diode models:


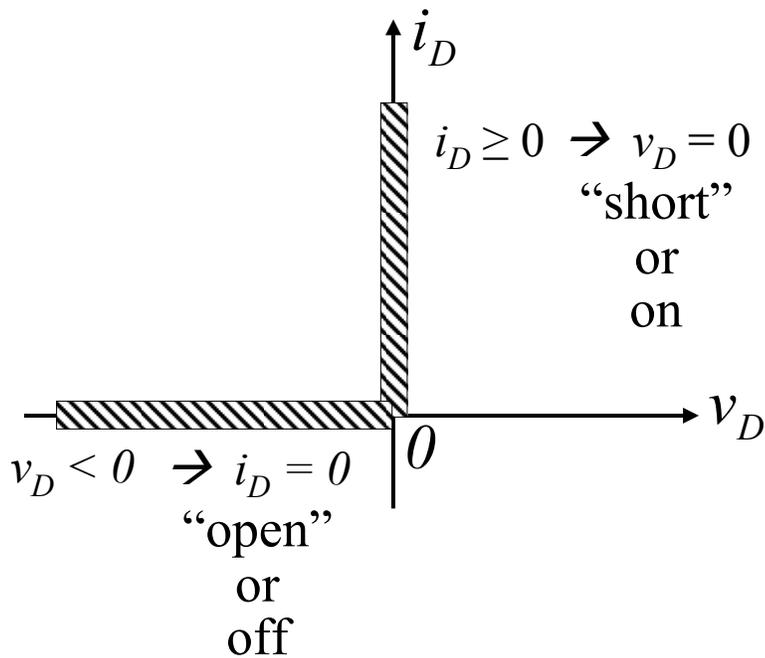


Ideal diode model

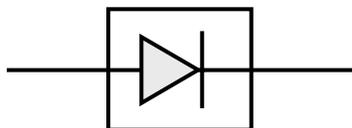
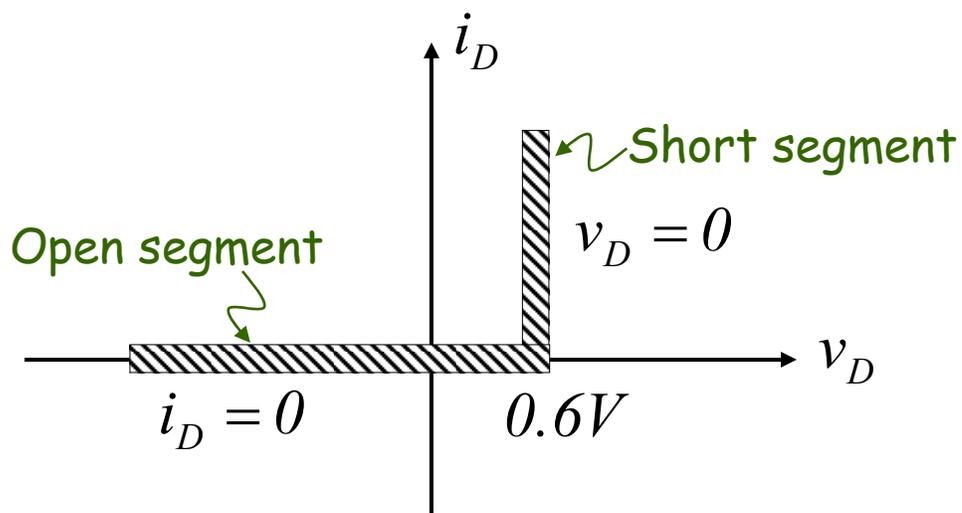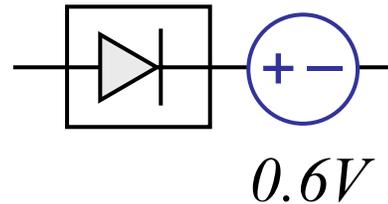
# Another analysis method: piecewise-linear analysis

"Practical" diode model  
ideal with offset



# Another analysis method: piecewise-linear analysis


## Piecewise-linear analysis method

- Replace nonlinear characteristic with linear segments.
- Perform linear analysis within each segment.

# Example


(We will build up towards an AC-to-DC converter)

Consider

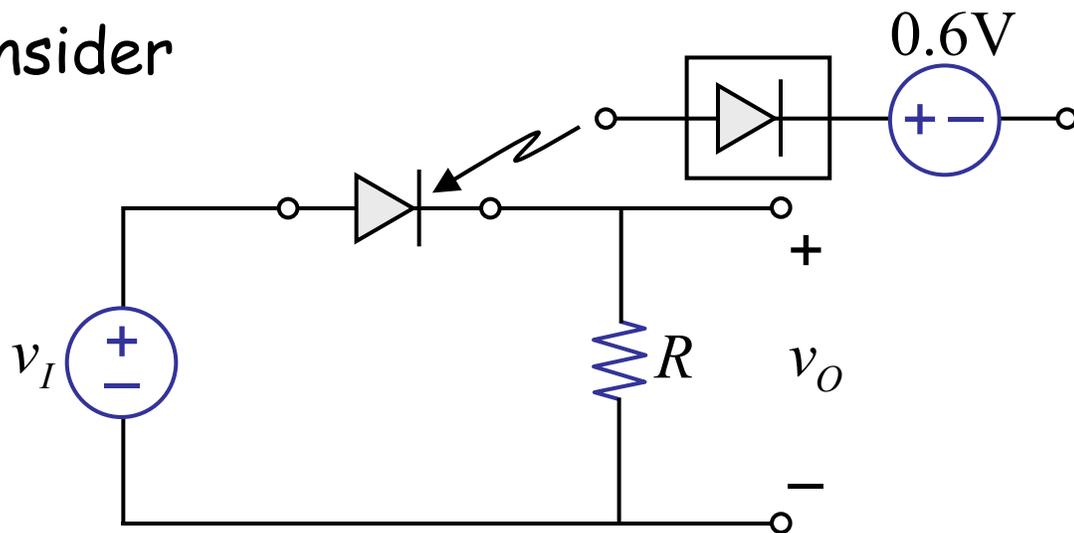


$v_I$  is a sine wave


# Example

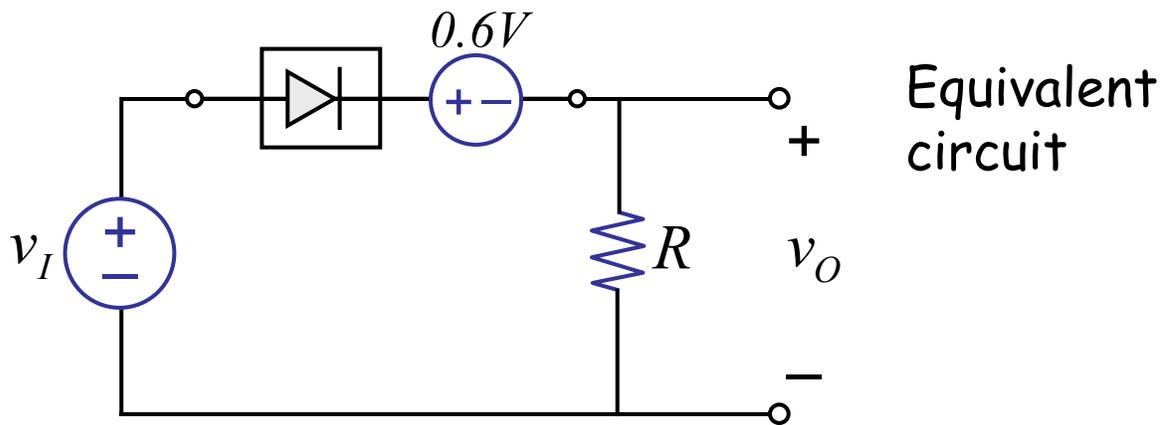


"Short segment":

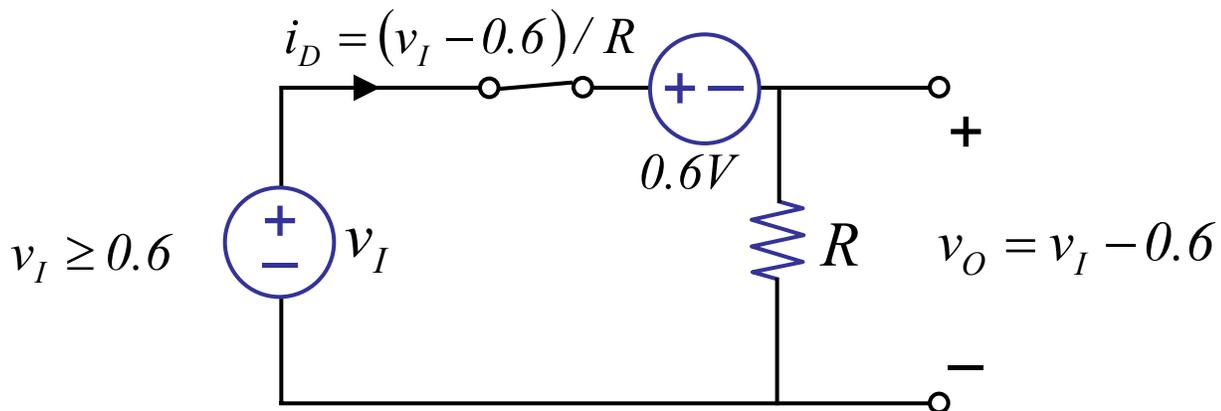


"Open segment":

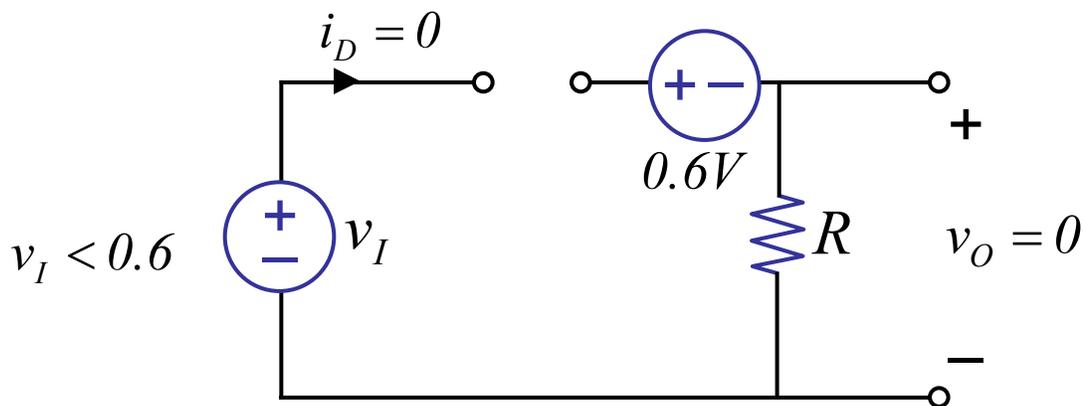


# Example

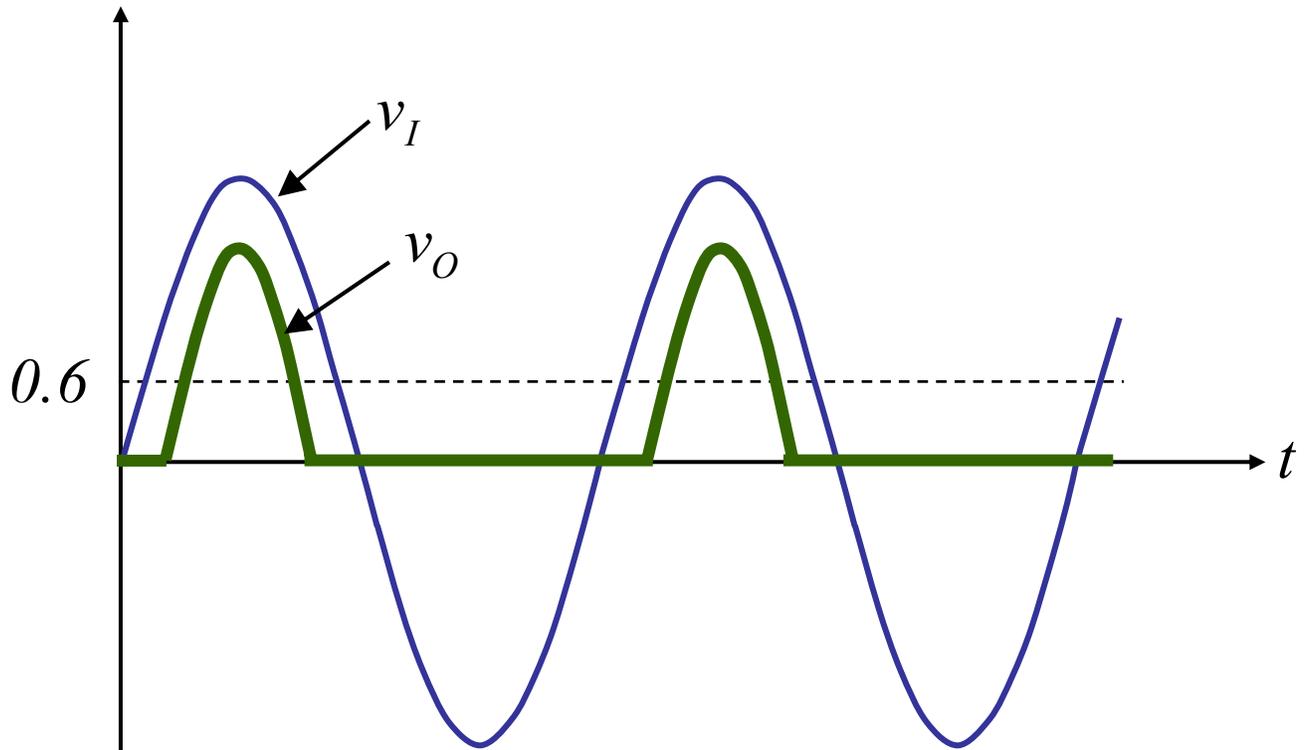

Now consider — a half-wave rectifier

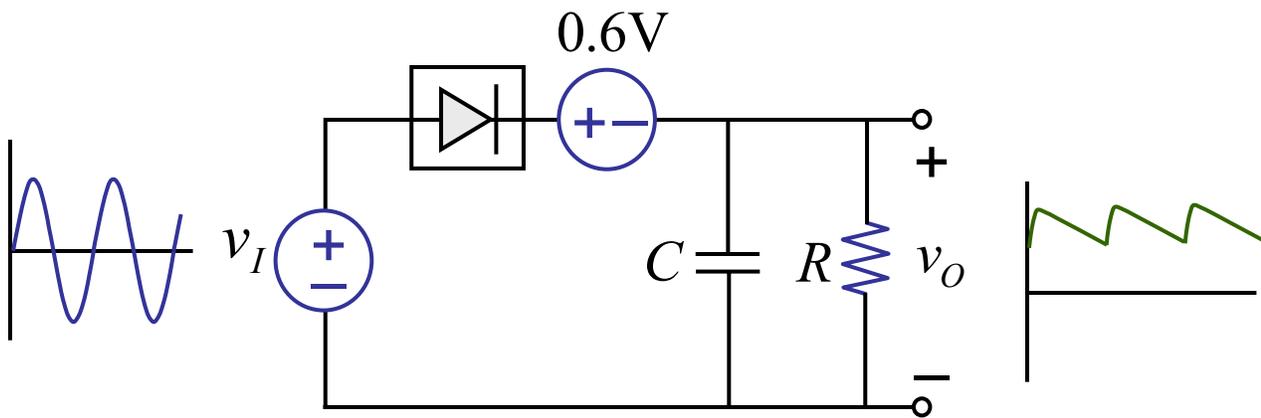


# A half-wave rectifier

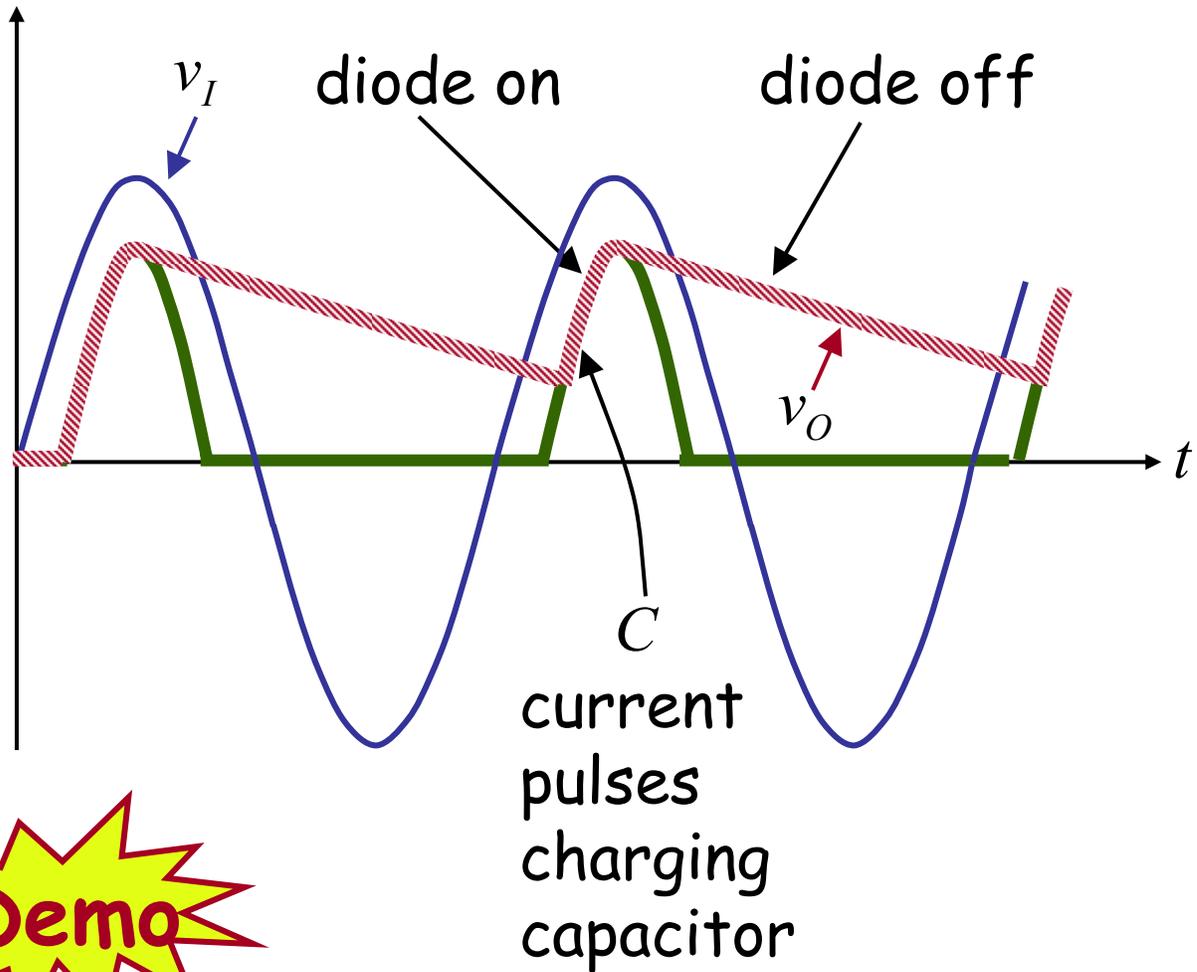


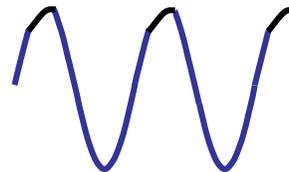
**Demo**

MIT's supply shows "snipping" at the peaks (because current drawn at the peaks)



# DC-to-DC UP Converter

Do not use  
resistive  
elements!

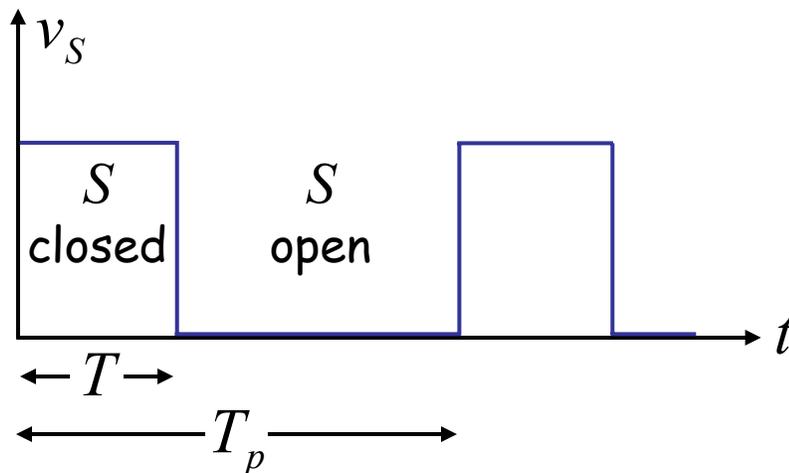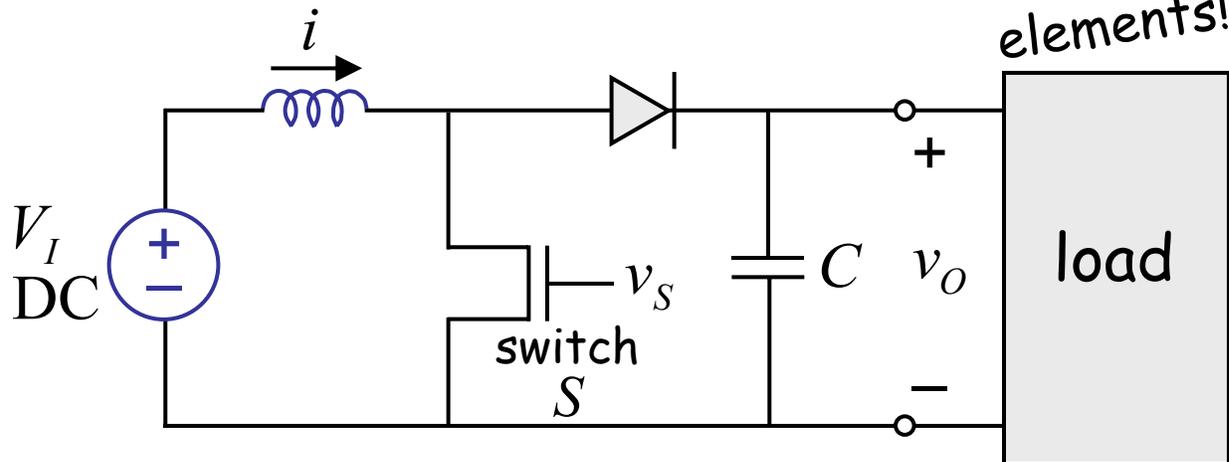



The circuit has 3 states:

- I.  $S$  is on, diode is off  
 $i$  increases linearly
- II.  $S$  turns off, diode turns on  
 $C$  charges up,  $v_O$  increases
- III.  $S$  is off, diode turns off  
 $C$  holds  $v_O$  (discharges into load)

## More detailed analysis

I. Assume  $i(0) = 0$ ,  $v_o(0) > 0$



$S$  on at  $t = 0$ , diode off

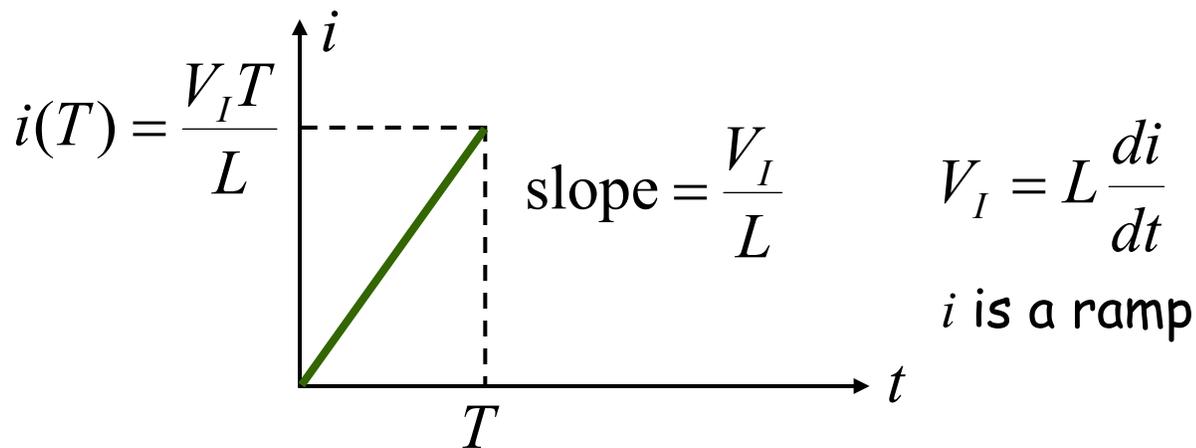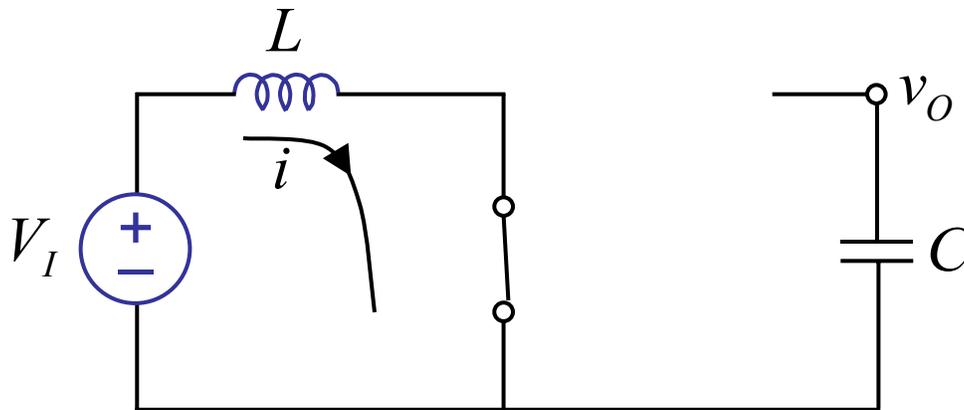

$$\Delta E = \text{energy stored at } t = T : \frac{1}{2} Li(T)^2$$


$$\Delta E = \frac{V_I^2 T^2}{2L}$$

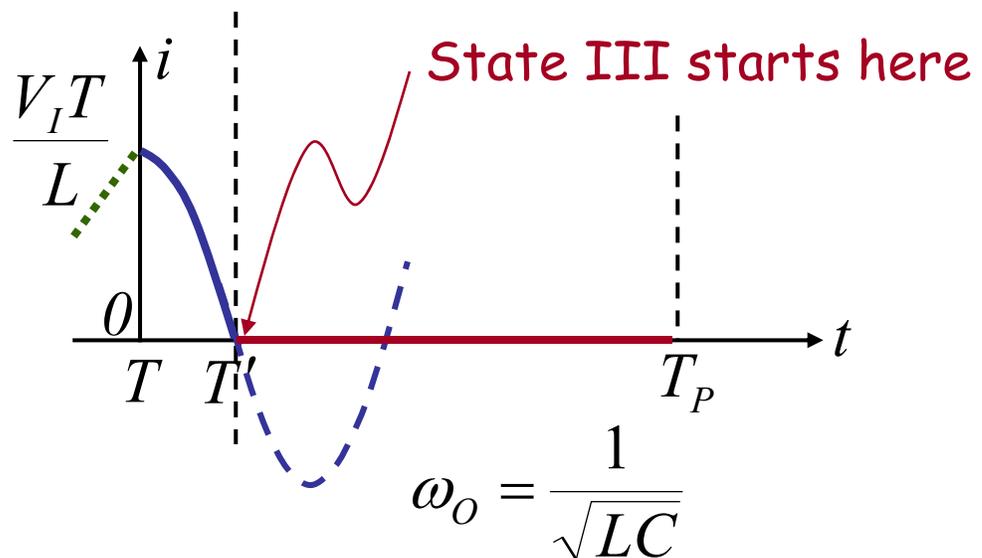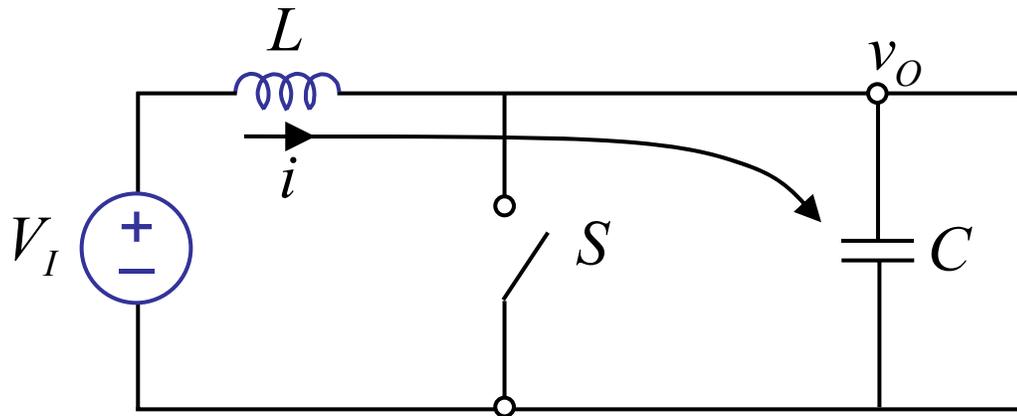**II.**  $S$  turns off at  $t = T$   
 diode turns on (ignore diode voltage drop)




Diode turns off at  $T'$  when  $i$  tries to go negative.

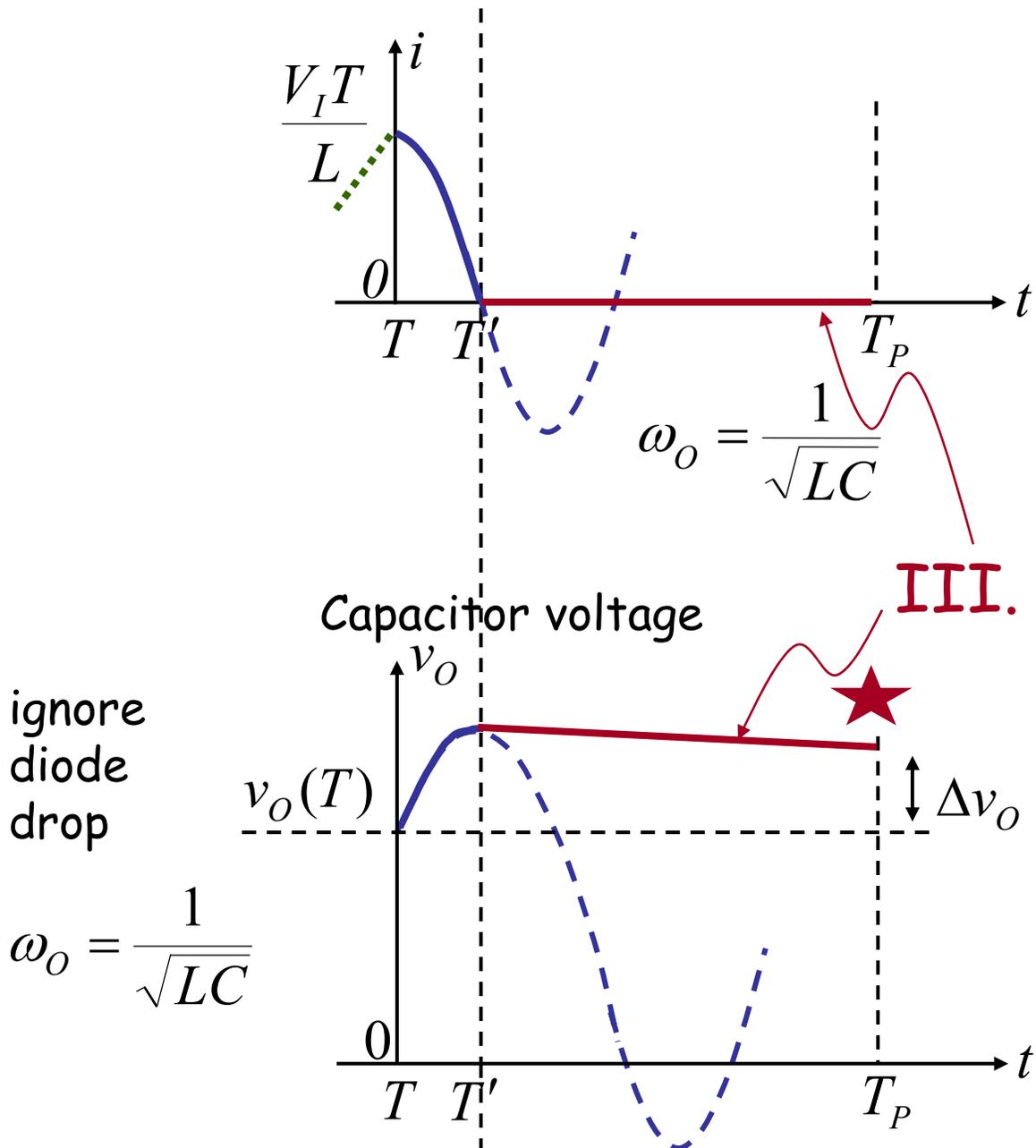**II.**  $S$  turns off at  $t = T$ , diode turns on  
 Let's look at the voltage profile




Diode turns off at  $T'$  when  $I$  tries to go negative.

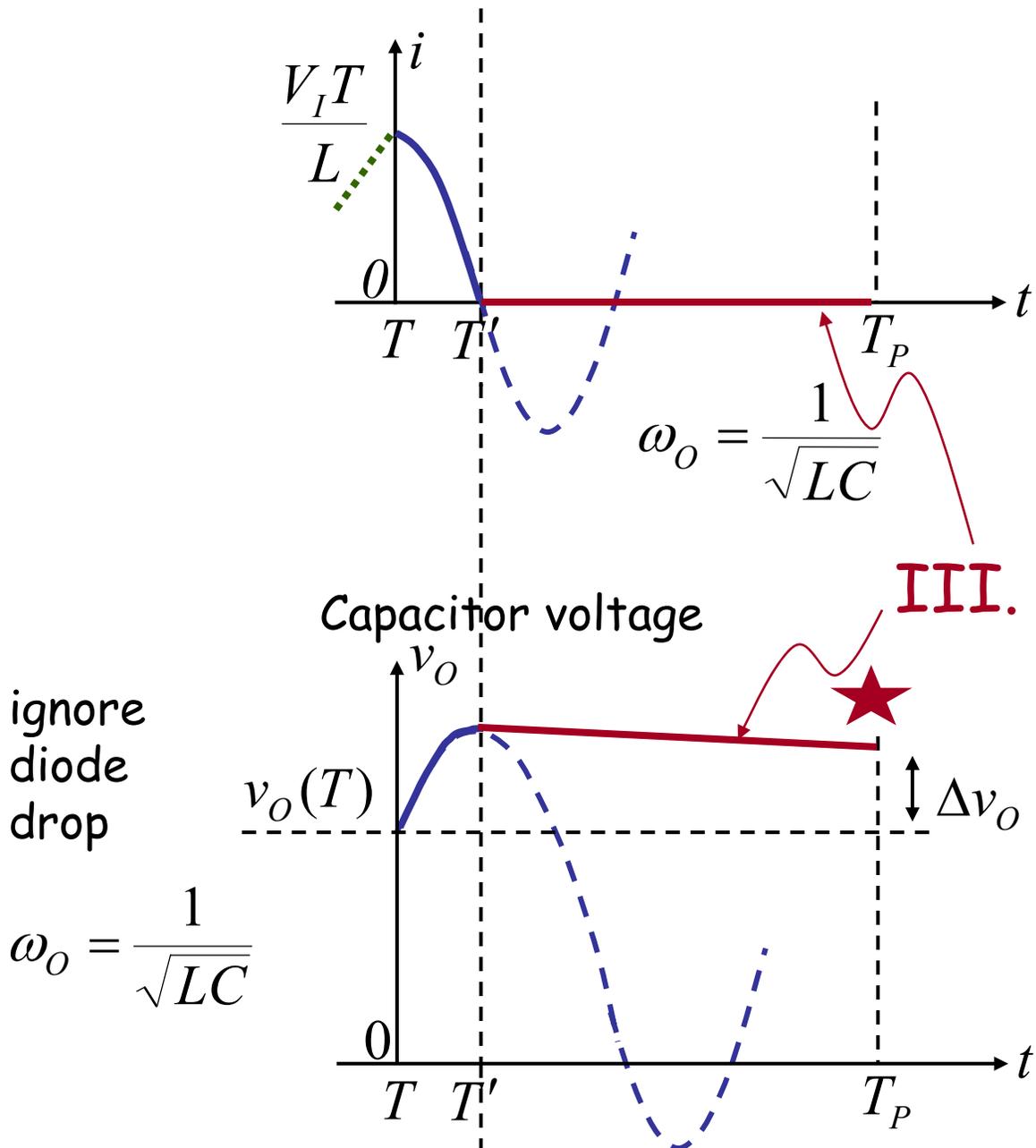**II.**  $S$  turns off at  $t = T$ , diode turns on  
 Let's look at the voltage profile




Diode turns off at  $T'$  when  $I$  tries to go negative.


### III. $S$ is off, diode turns off

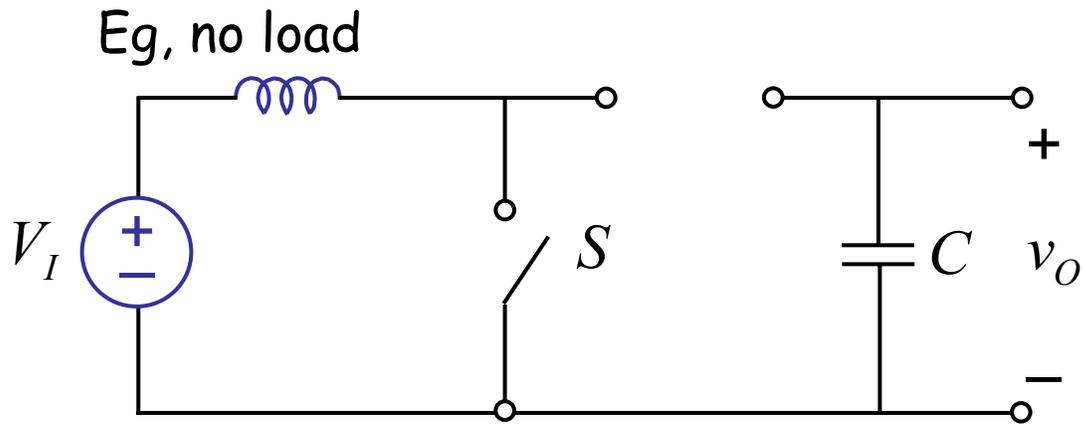

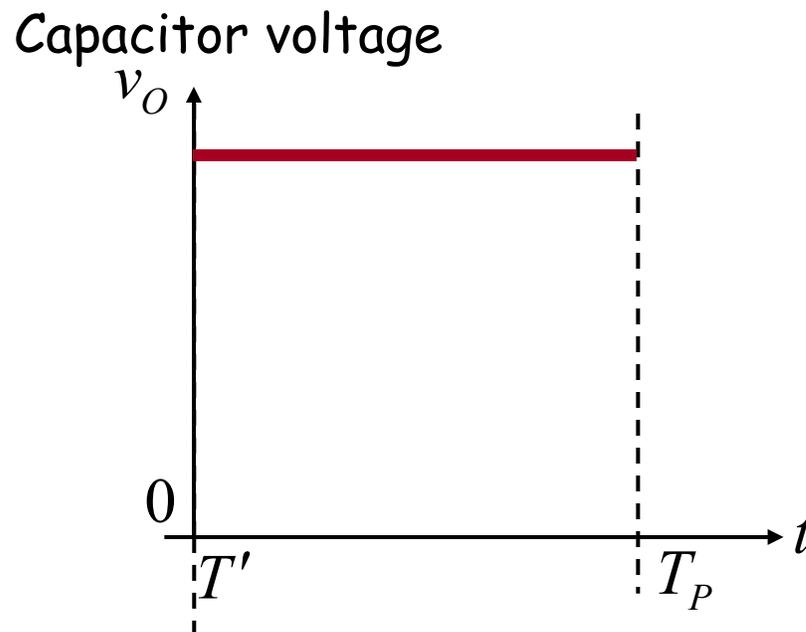$C$  holds  $v_O$  after  $T'$   
 $i$  is zero



### III. $S$ is off, diode turns off

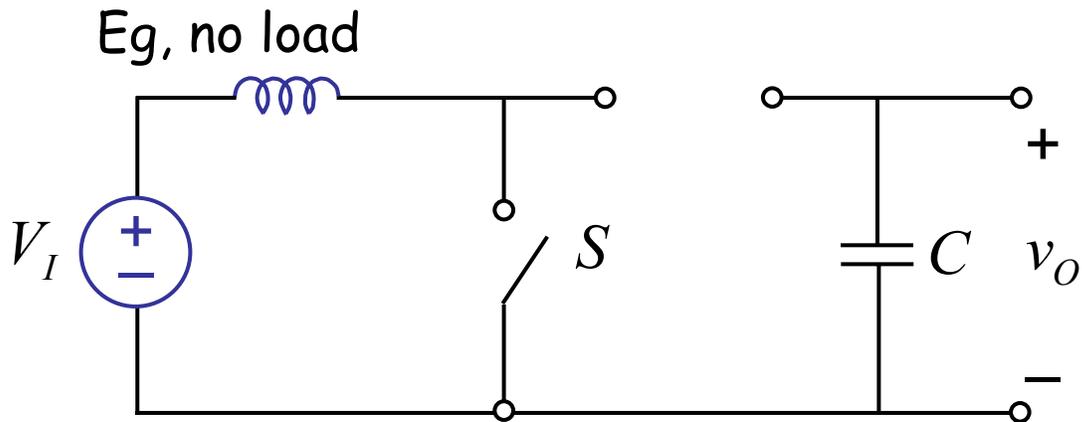


$C$  holds  $v_O$  after  $T'$   
 $i$  is zero

until  $S$  turns ON at  $T_P$ , and cycle repeats

I II III I II III ...

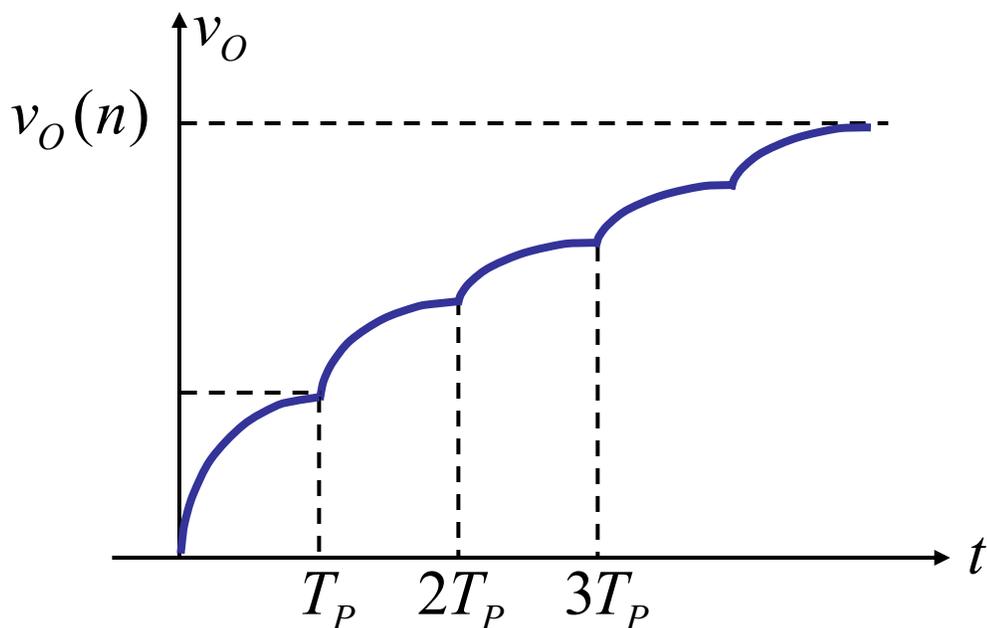Thus,  $v_O$  increases each cycle, if there is no load.



What is  $v_o$  after  $n$  cycles  $\rightarrow v_o(n)$ ?

Use energy argument ... (KVL tedious!)

Each cycle deposits  $\Delta E$  in capacitor.

$$\Delta E = \frac{1}{2} \frac{V_I^2 T^2}{L} \quad \left\{ \begin{array}{l} \Delta E = \frac{1}{2} L i(t=T)^2 \\ = \frac{1}{2} L \left( \frac{V_I T}{L} \right)^2 \end{array} \right.$$

After  $n$  cycles, energy on capacitor

$$n\Delta E = \frac{nV_I^2 T^2}{2L}$$


This energy must equal  $\frac{1}{2} C v_o(n)^2$

so,  $\frac{1}{2} C v_o^2(n) = \frac{nV_I^2 T^2}{2L}$

or  $v_o(n) = \sqrt{\frac{nV_I^2 T^2}{LC}} \quad \left\{ \omega_o = \frac{1}{\sqrt{LC}} \right.$

$$v_o(n) = V_I T \omega_o \sqrt{n}$$
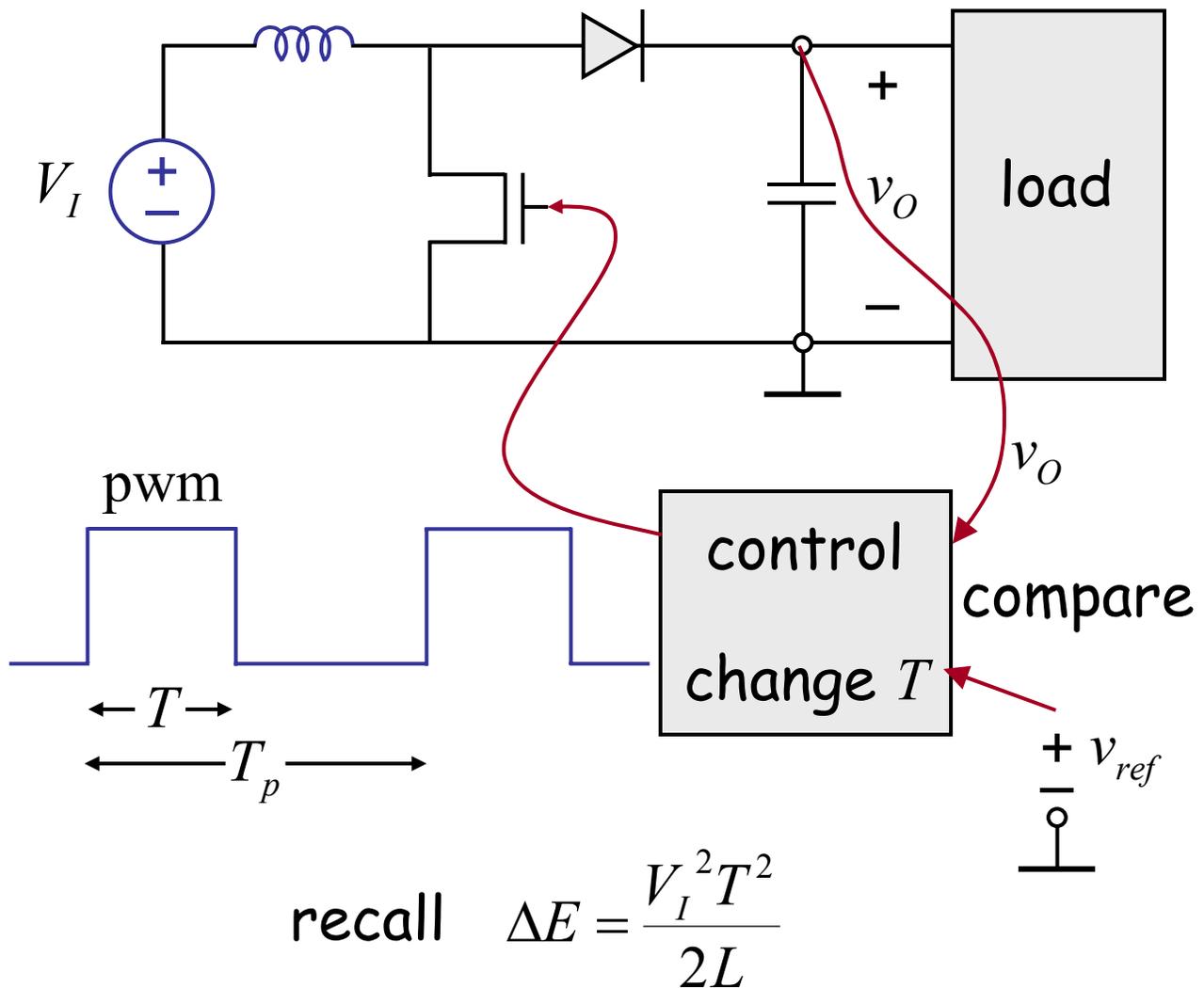
# How to maintain $v_O$ at a given value?



Another example of negative feedback:

if  $(v_O - v_{ref}) \uparrow$  then  $T \downarrow$

if  $(v_O - v_{ref}) \downarrow$  then  $T \uparrow$