

**Massachusetts Institute of Technology
Electrical Engineering and Computer Science Department**

6.002 Electronic Circuits

**Homework #6
Handout F00-031**

Issued: Oct. 12, 2000 - Due: Oct. 20, 2000

Read Sections 8.1 - 8.2

Exercise 6-1: Exercise 8.1 from Chapter 8

Exercise 6-2: Exercise 8.2 from Chapter 8

Problem 6-1: (Exercise 8.5 from Chapter 8 with part e omitted)

Consider again the MOSFET amplifier shown in Figure 9.44 (See Notes). Assume as before that the amplifier is operated under the saturation discipline.

- a) What is the range of valid input voltages for the amplifier? What is the corresponding range of valid output voltages?
- b) Assuming we desire to use voltages of the form $A\sin(\omega t)$ as AC inputs to the amplifier, determine the input bias point V_I for the amplifier which will allow for the maximum input swing under the saturation discipline. What is the corresponding output bias point voltage V_O ?
- c) What is the largest value of A that will allow the saturation region operation for the bias point determined in (b)?
- d) What is the small signal gain of the amplifier for the bias point determined in (b)?

Problem 6-2: (Problem 8.1 from Chapter 8 with part c omitted)

This problem studies the small-signal analysis of the MOSFET amplifier discussed in Problem 7.3 (Figure 7.75) in the previous chapter.

- a) First consider the biasing the amplifier. Determine V_{IN} , the bias component of v_{IN} , so that v_{OUT} is biased to V_{OUT} where $0 < V_{OUT} < V_S$. Find V_{MID} , the bias component of v_{MID} in the process.
- b) Next, let $v_{IN} = V_{IN} + v_{in}$ where v_{in} is considered to be a small perturbation of V_{IN} around V_{IN} . Make the substitution for v_{IN} and linearize the resulting expression for v_{OUT} . Your answer should take the form $v_{OUT} = V_{OUT} + v_{out}$, where v_{out} takes the form $v_{out} = Av_{in}$. Note that v_{out} is the small-signal output and A is the small-signal gain. Derive an expression for A .

Problem 6-3: (Problem 8.2 from Chapter 8 with parts e and f omitted)

Consider again the buffer described in Problem 7.5 (Figure 7.76) in the previous chapter. Perform a small-signal analysis of this circuit according to the following steps. Assume that the MOSFET operates in its saturation region and continue to use the SCS MOSFET model.

- a) Draw the small-signal circuit model of the buffer.
- b) Show that the small-signal transconductance g_m of the MOSFET is given by

$$g_m = K(V_{IN} - V_{OUT} - V_T)$$

where V_{IN} and V_{OUT} are the bias, or operating-point, input and output voltages, respectively.

- c) Determine the small-signal gain of the buffer. That is, determine the ratio v_{out}/v_{in} .
- d) Determine the small-signal output resistance of the buffer. That is determine the equivalent resistance of the buffer at the output port of its small-signal model with $v_{in} = 0$. (Hint: This is the Thevenin equivalent resistance of the small-signal circuit looking into the output port.)
- e) Determine the small-signal input resistance of the buffer. That is determine the equivalent resistance of the buffer at the input port of its small-signal model. (Hint: This is the Thevenin equivalent resistance of the small-signal circuit looking into the input port.)