

6.002


**CIRCUITS AND
ELECTRONICS**

Inside the Digital Gate

Review

The Digital Abstraction

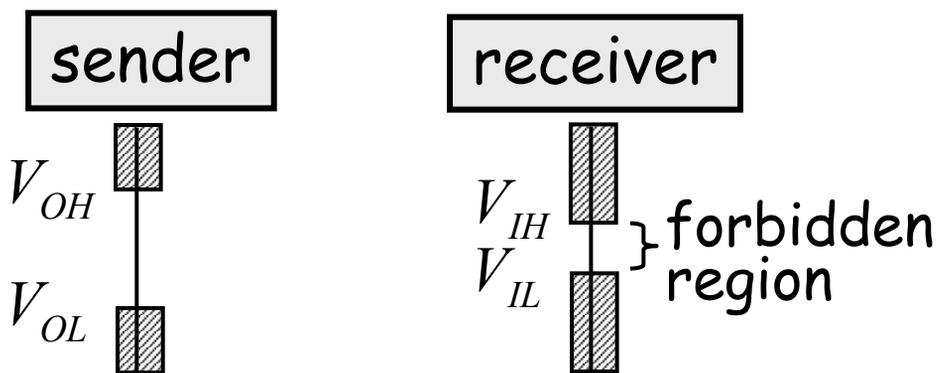- Discretize value 0, 1
- Static discipline
meet voltage thresholds




Specifies how gates must be designed

Review


Combinational gate abstraction

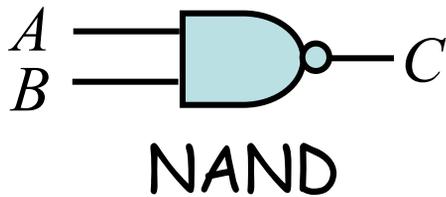- ➔ outputs function of input alone
- ➔ satisfies static discipline



A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

For example: a digital circuit

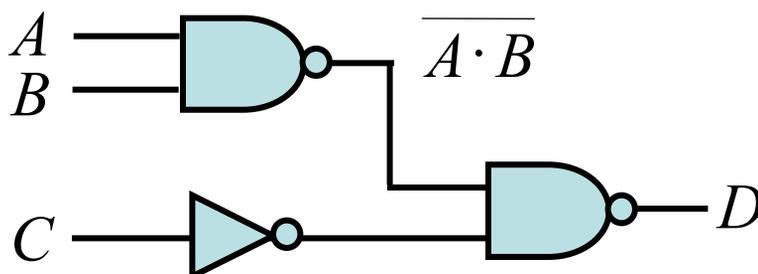


$$D = \overline{(\overline{C} \cdot (\overline{A \cdot B}))}$$

3 gates here

- A Pentium III class microprocessor is a circuit with over 4 million gates!!
- The RAW chip being built at the Lab for Computer Science at MIT has about 3 million gates.

How to build a digital gate

Analogy

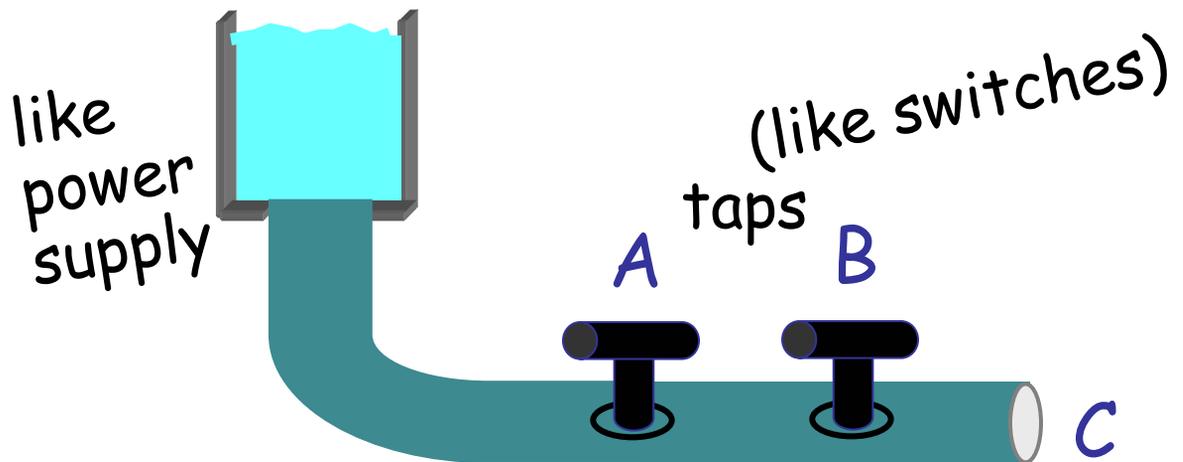

if $A=ON$ AND $B=ON$


C has H_2O

else


C has no H_2O

Use this insight to build an AND gate.

How to build a digital gate

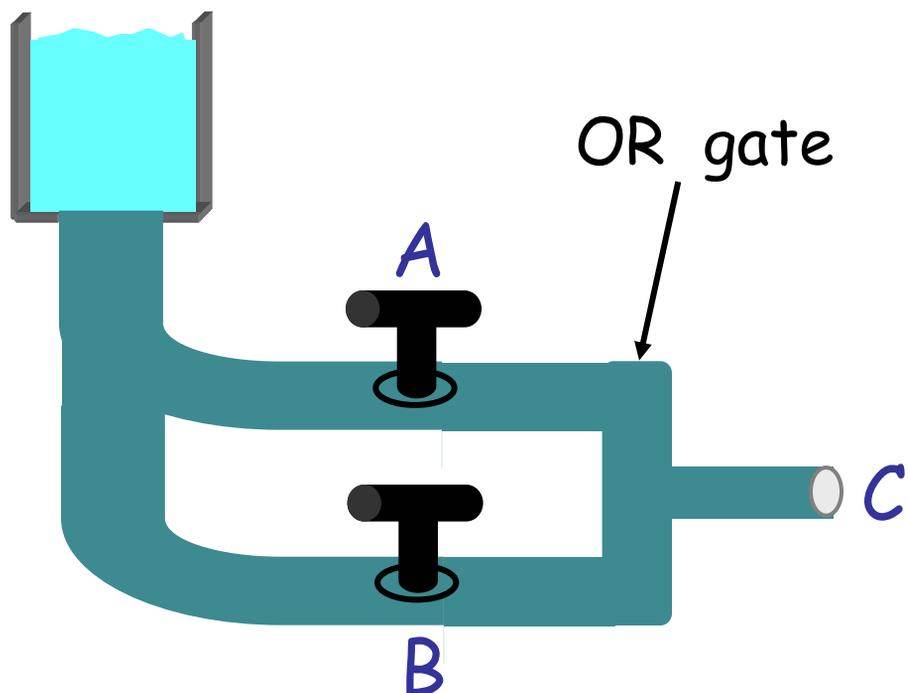

Electrical Analogy

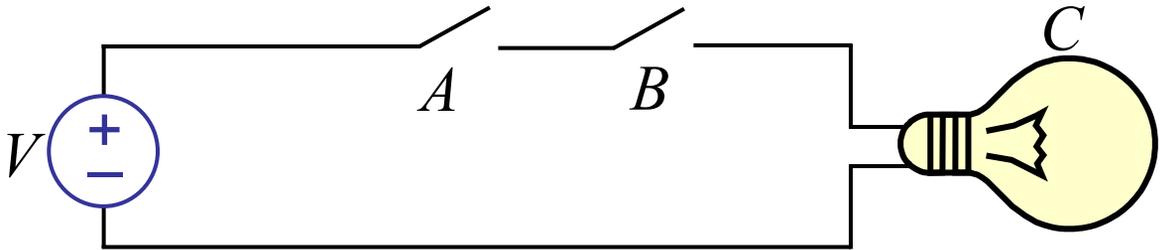


Bulb C is ON if A AND B are ON,
else C is off

Key: "switch" device

Electrical Analogy

Key: "switch" device

equivalent ckt

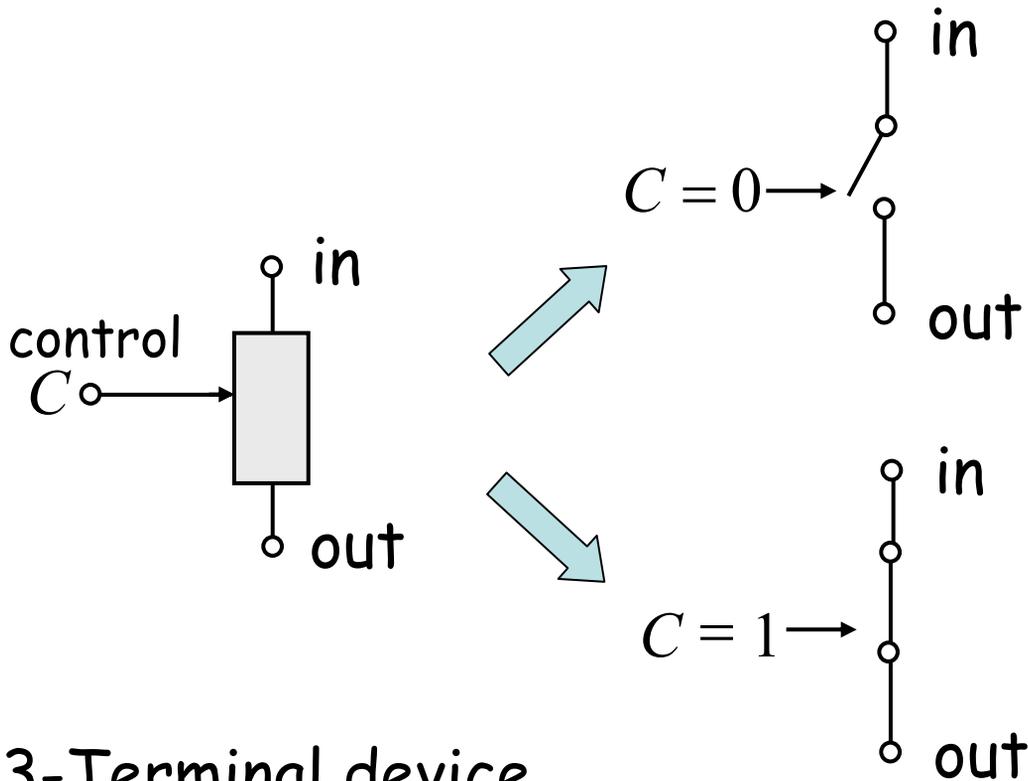




3-Terminal device
if $C = 0$

short circuit between in and out
else


open circuit between in and out

For mechanical switch,
control \longrightarrow mechanical pressure

Consider

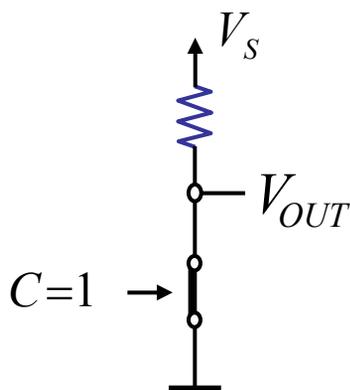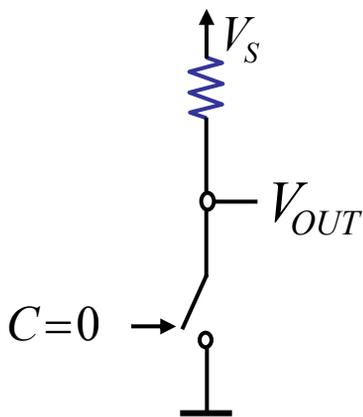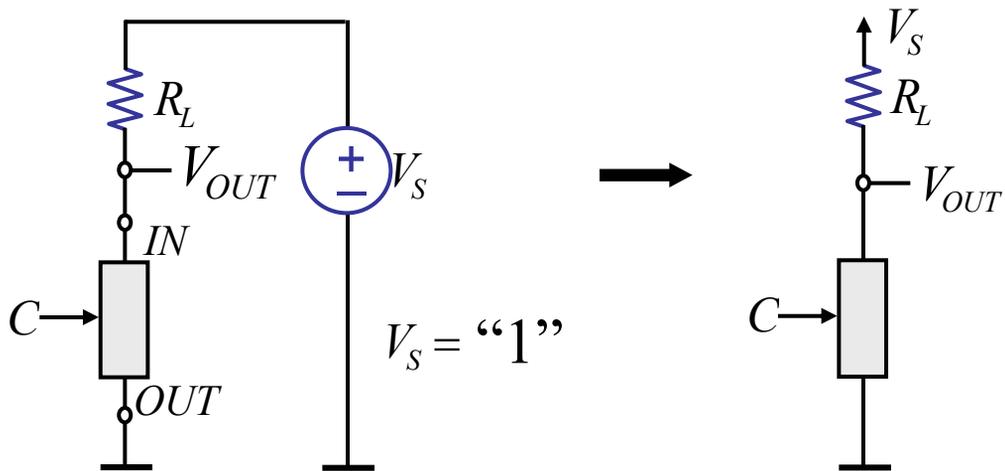


Truth table for

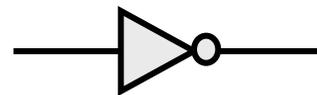


C	V_{OUT}
0	1
1	0


What about?

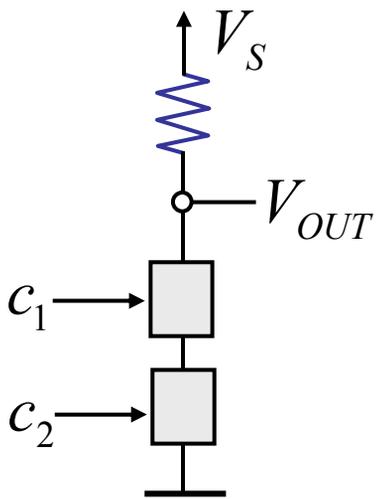


Truth table for

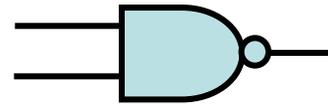

c_1	c_2	V_O
0	0	1
0	1	1
1	0	1
1	1	0

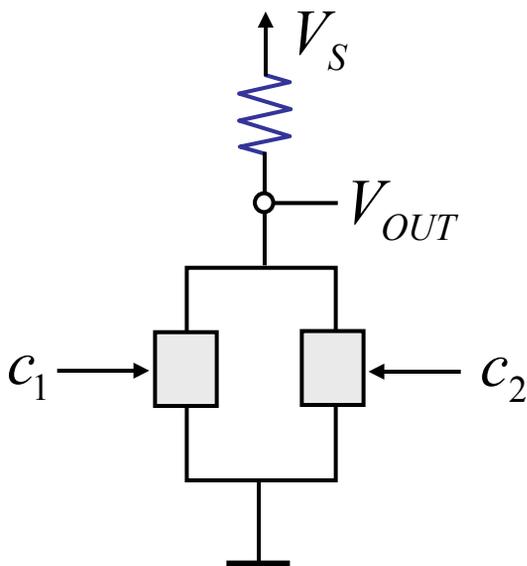


Truth table for

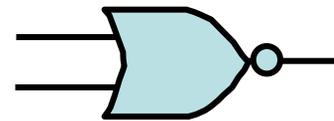

c_1	c_2	V_O
0	0	1
0	1	0
1	0	0
1	1	0


What about?

can also build compound gates

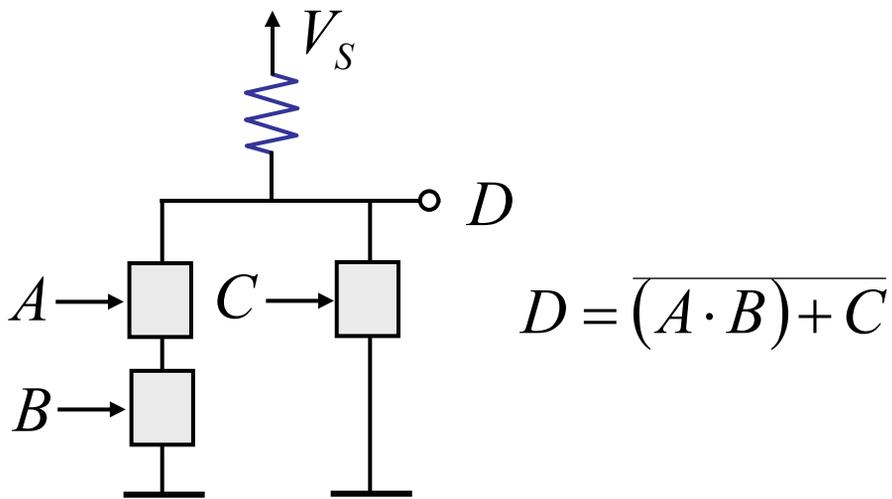

The MOSFET Device

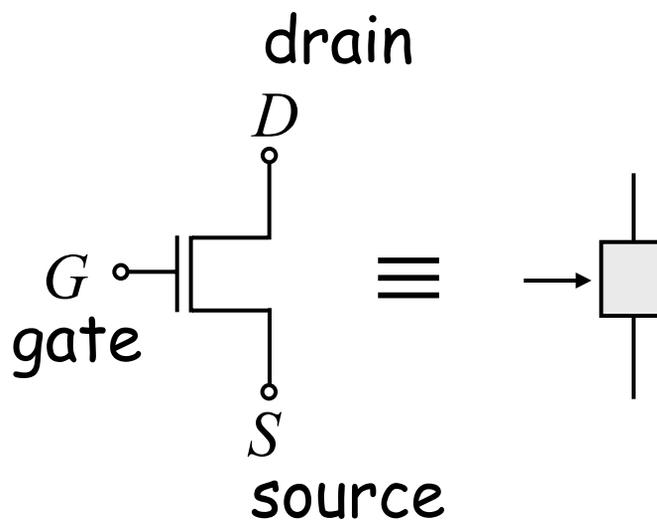Metal-Oxide
Semiconductor
Field-Effect
Transistor






3 terminal lumped element
behaves like a switch

G : control terminal
 D, S : behave in a symmetric
manner (for our needs)

The MOSFET Device

Understand its operation by viewing it as a two-port element —

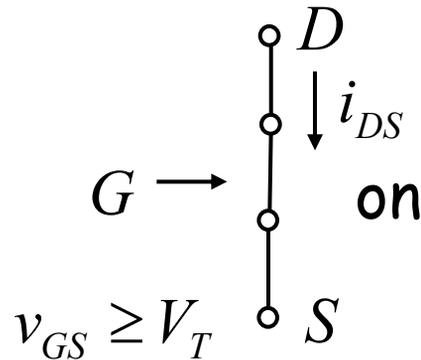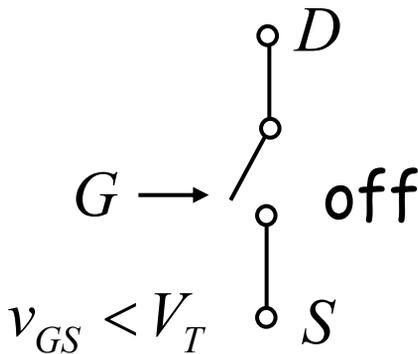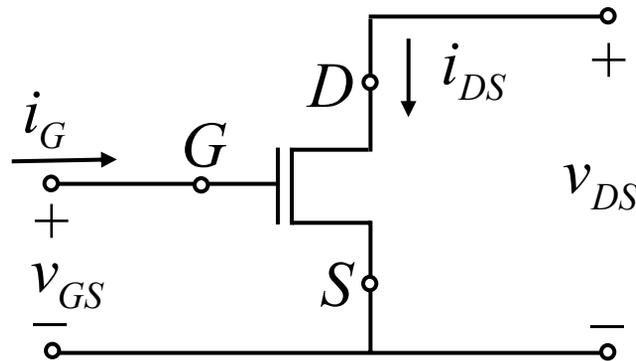Check out the textbook for its internal structure.





$V_T \approx 1V$ typically


"Switch" model (S model) of the MOSFET



Check the MOS device
on a scope.

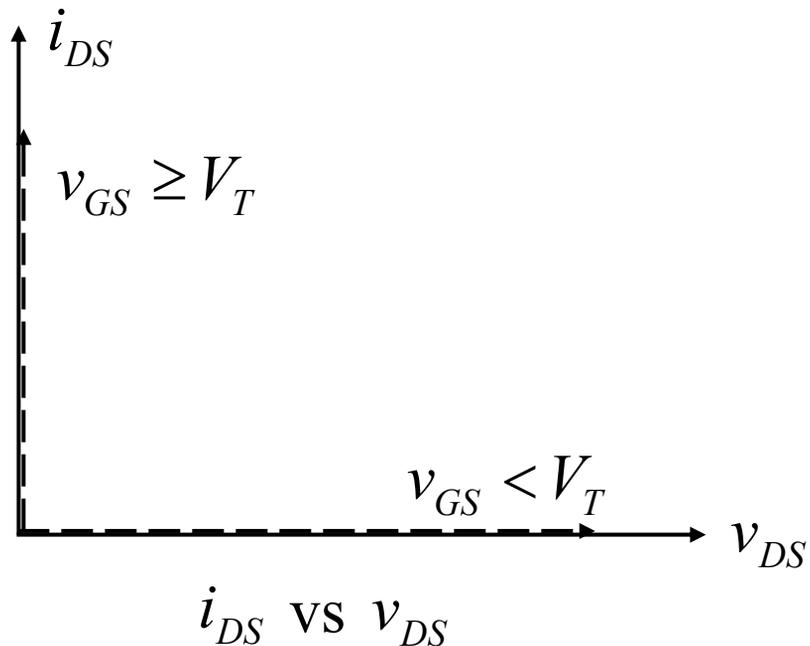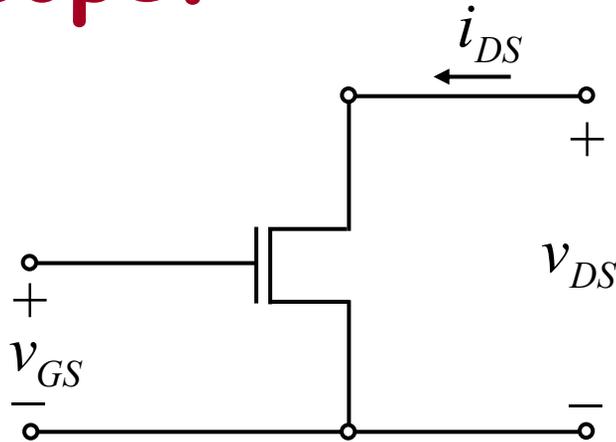

A MOSFET Inverter

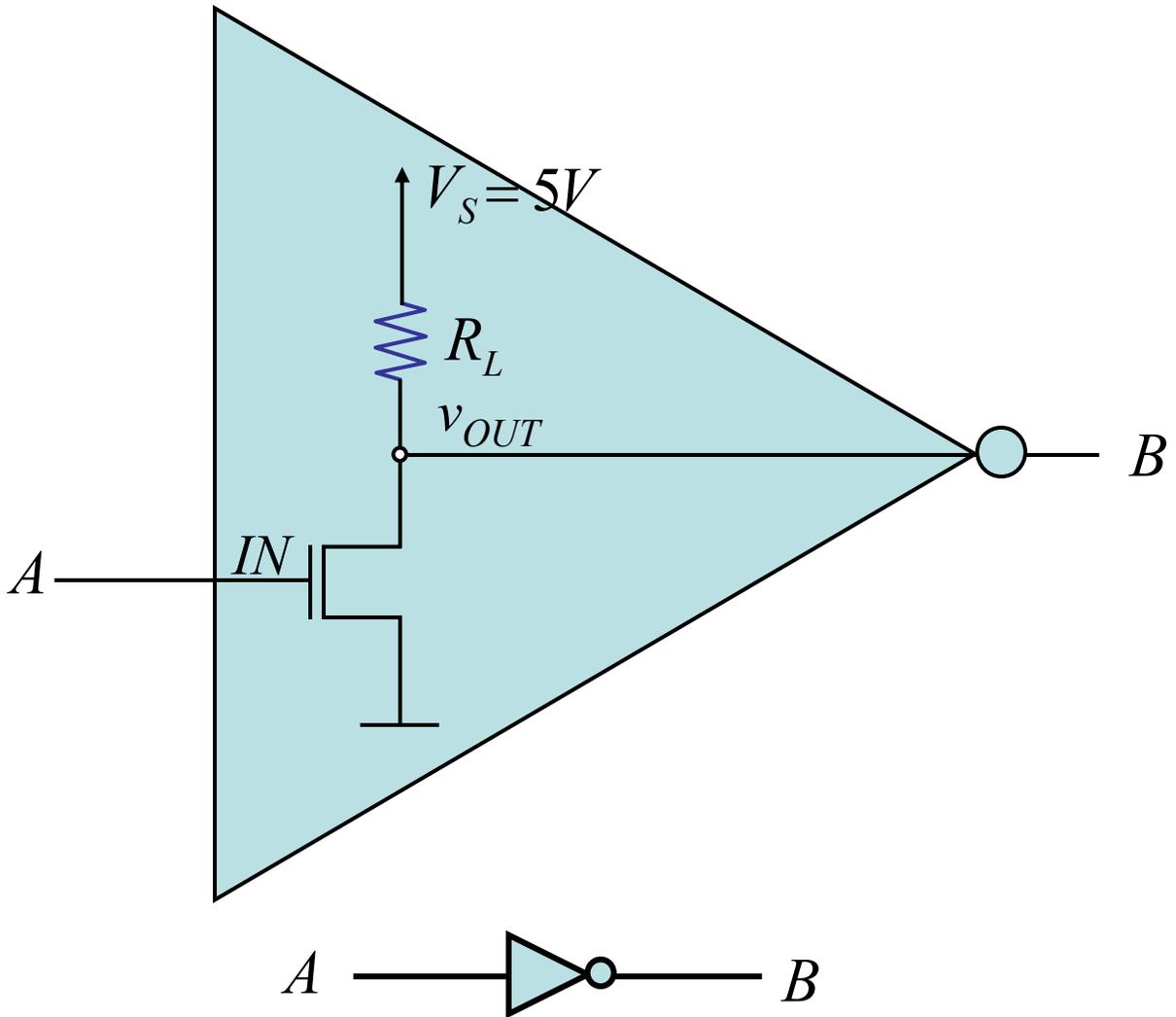


Note the power of abstraction.

The abstract inverter gate representation hides the internal details such as power supply connections, R_L , GND , etc.

(When we build digital circuits, the \uparrow and \perp are common across all gates!)

Example

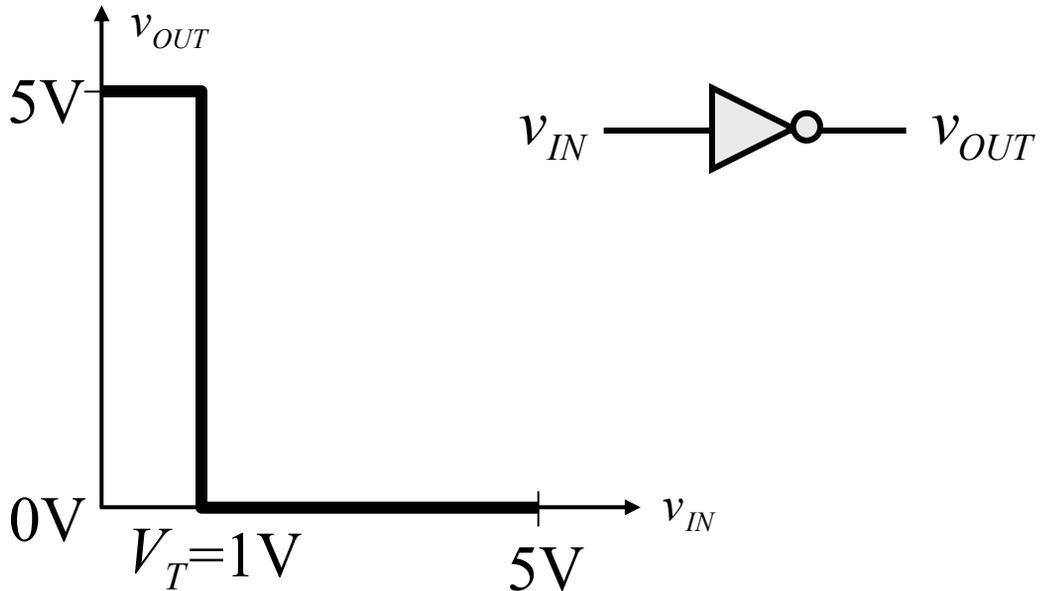

The T1000 model laptop desires gates that satisfy the static discipline with voltage thresholds. Does our inverter qualify?

$$V_{OL} = 0.5V$$



$$V_{IL} = 0.9V$$

$$V_{OH} = 4.5V$$

$$V_{IH} = 4.1V$$

sender

receiver

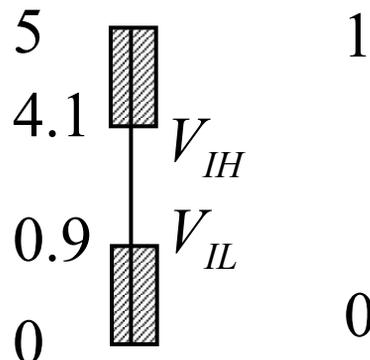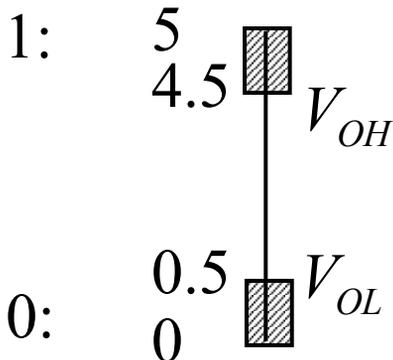

Our inverter satisfies this.

E.g.:




Does our inverter satisfy the static discipline for these thresholds:

$$\left. \begin{array}{ll} V_{OL} = 0.2\text{V} & V_{IL} = 0.5\text{V} \\ V_{OH} = 4.8\text{V} & V_{IH} = 4.5\text{V} \end{array} \right\} \text{yes}$$

$$\left. \begin{array}{ll} V_{OL} = 0.5\text{V} & \overset{\times}{V_{IL} = 1.5\text{V}} \\ V_{OH} = 4.5\text{V} & V_{IH} = 3.5\text{V} \end{array} \right\} \text{no}$$




Switch resistor (SR) model of MOSFET

...more accurate MOS model

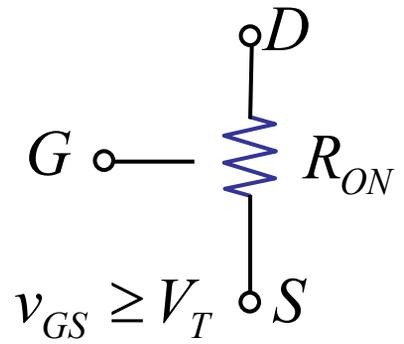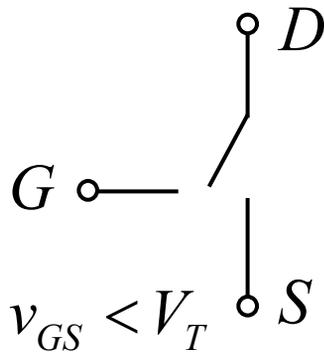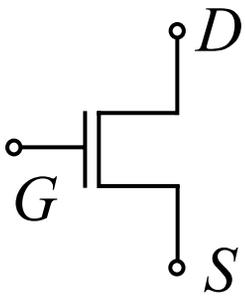


e.g. $R_{ON} = 5K\Omega$


SR Model of MOSFET

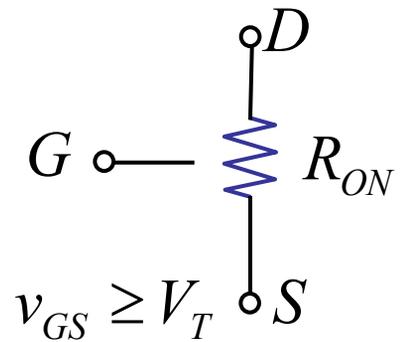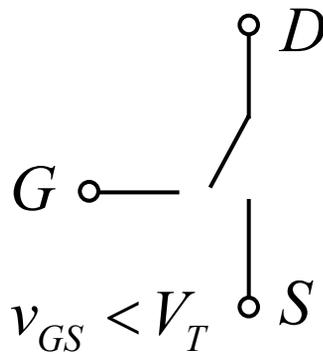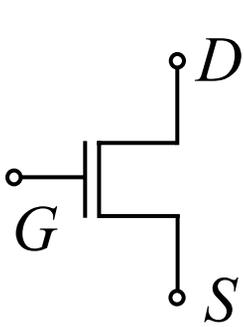



MOSFET
S model

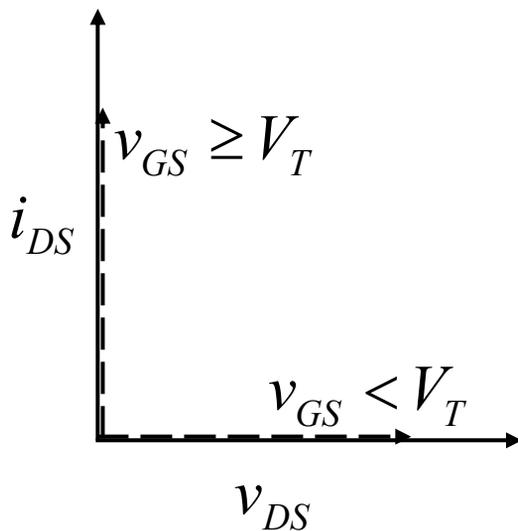


MOSFET
SR model

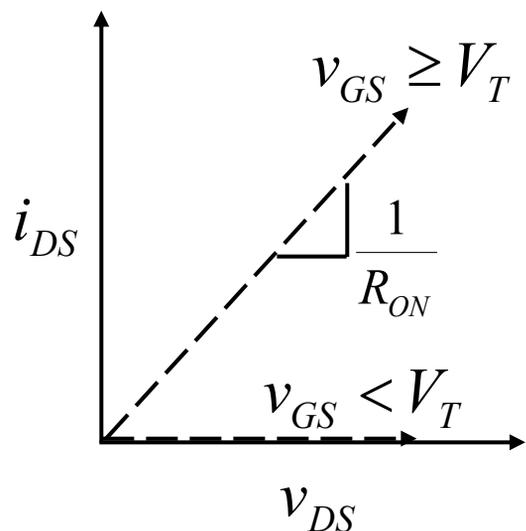


Using the SR model

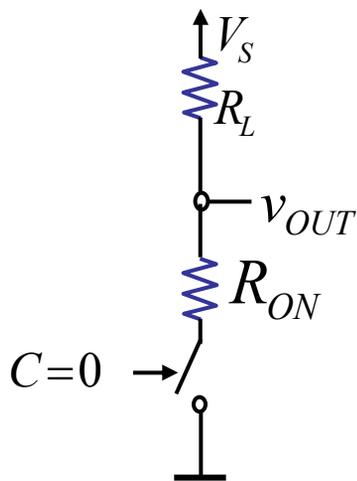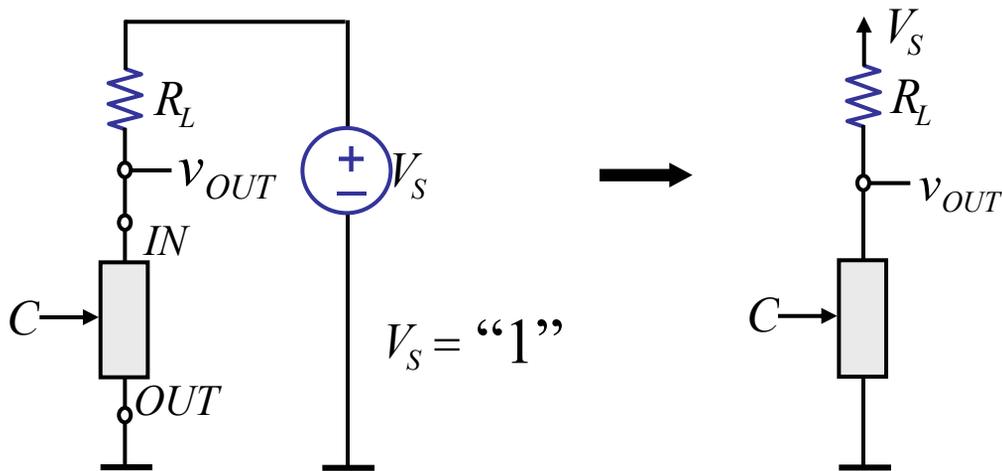

Truth table for

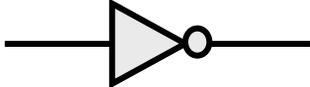

C	V_{OUT}
0	1
1	0

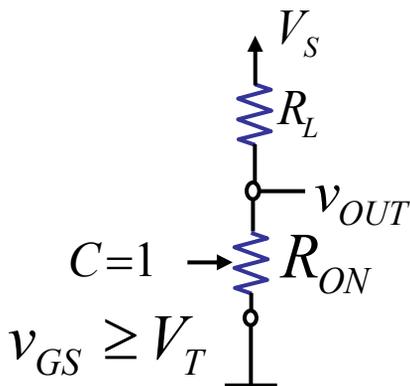

Choose R_L , R_{ON} , V_S such that:

$$v_{OUT} = \frac{V_S R_{ON}}{R_{ON} + R_L} \leq V_{OL}$$