


6.002

**CIRCUITS AND
ELECTRONICS**


Op Amps Positive Feedback

Negative vs Positive Feedback

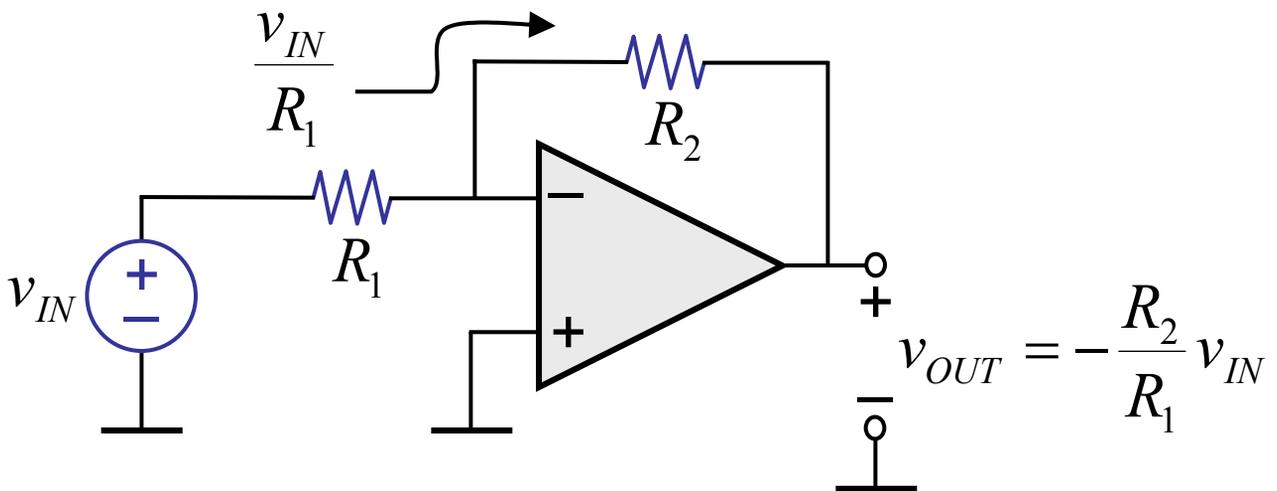Consider this circuit — *negative feedback*



and this — *positive feedback*


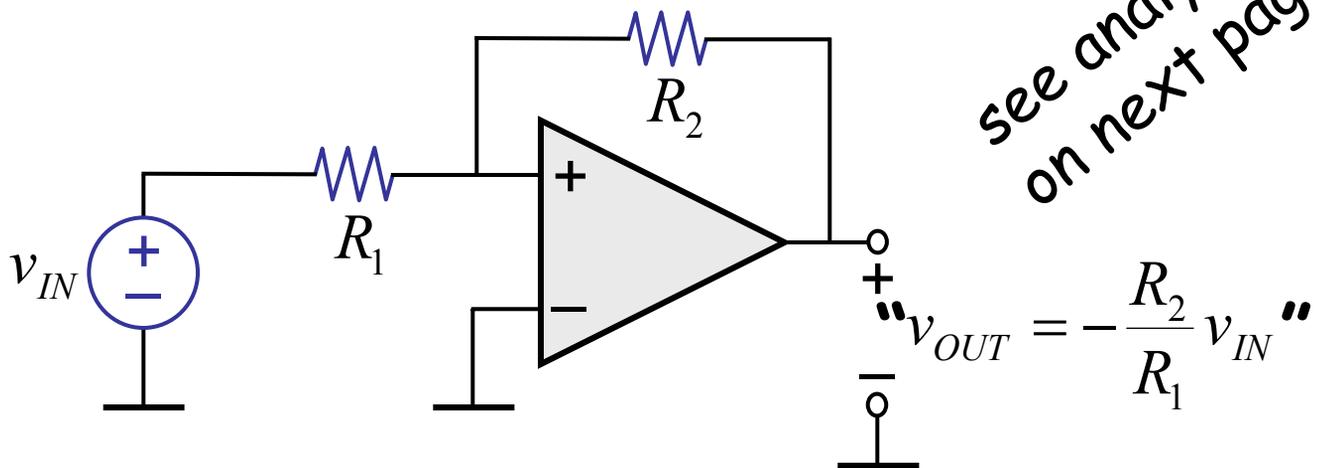


What's the difference?

Consider what happens when there is a perturbation...
Positive feedback drives op amp into saturation:

$$v_{OUT} \rightarrow \pm V_S$$

Static Analysis of Positive Feedback Ckt

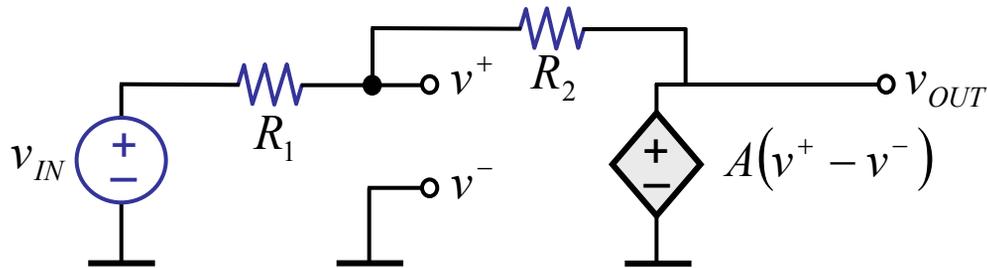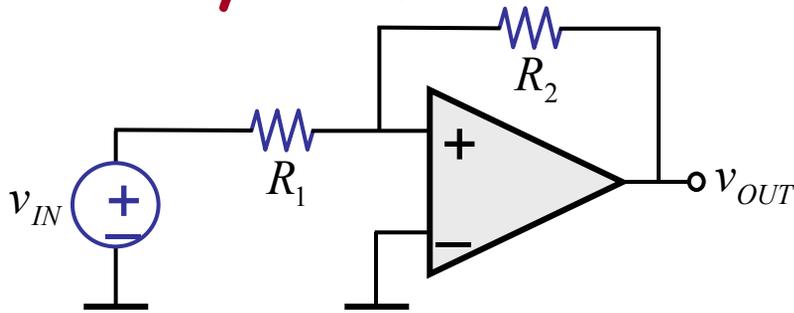

$$v_{OUT} = A(v^+ - v^-)$$

$$= Av^+$$


$$= A \left[\frac{v_{OUT} - v_{IN}}{R_1 + R_2} \cdot R_1 + v_{IN} \right]$$

$$= \frac{AR_1}{R_1 + R_2} v_{OUT} - \frac{AR_1 v_{IN}}{R_1 + R_2} + Av_{IN}$$

$$v_{OUT} \left[\cancel{1} - \frac{AR_1}{R_1 + R_2} \right] = v_{IN} A \left[\cancel{1} - \frac{R_1}{R_1 + R_2} \right]$$


$$v_{OUT} = \left[\frac{\cancel{1} - \frac{R_1}{R_1 + R_2}}{\cancel{-\frac{AR_1}{R_1 + R_2}}} \right] \cdot \cancel{A} v_{IN} = -\frac{R_2}{R_1} v_{IN}$$

Representing dynamics of op amp...

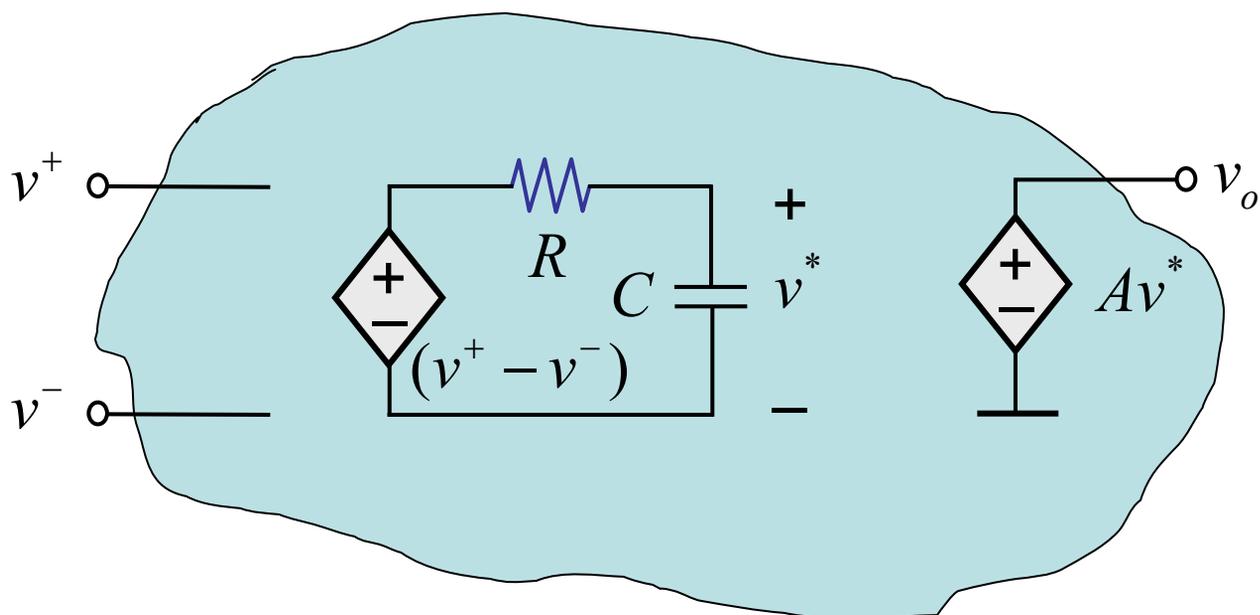


Representing dynamics of op amp...

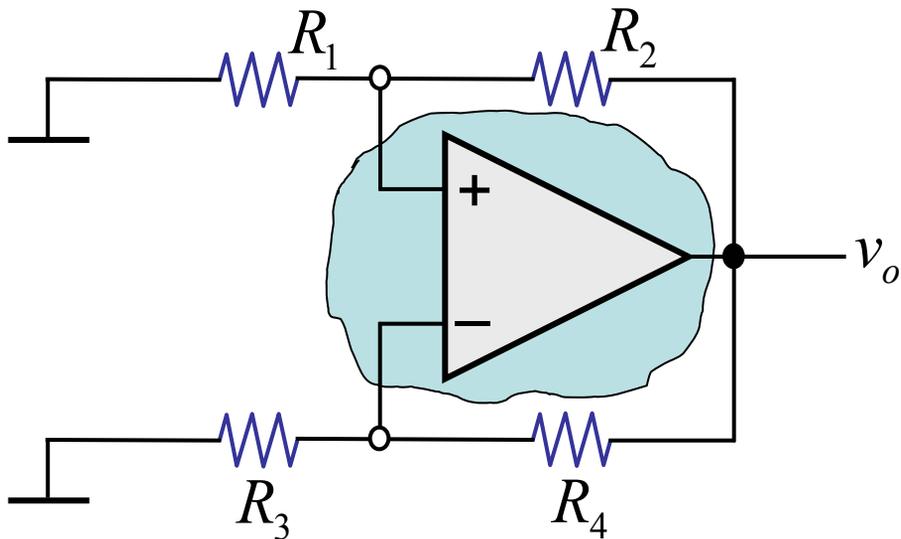Consider this circuit and let's analyze its dynamics to build insight.



Circuit model

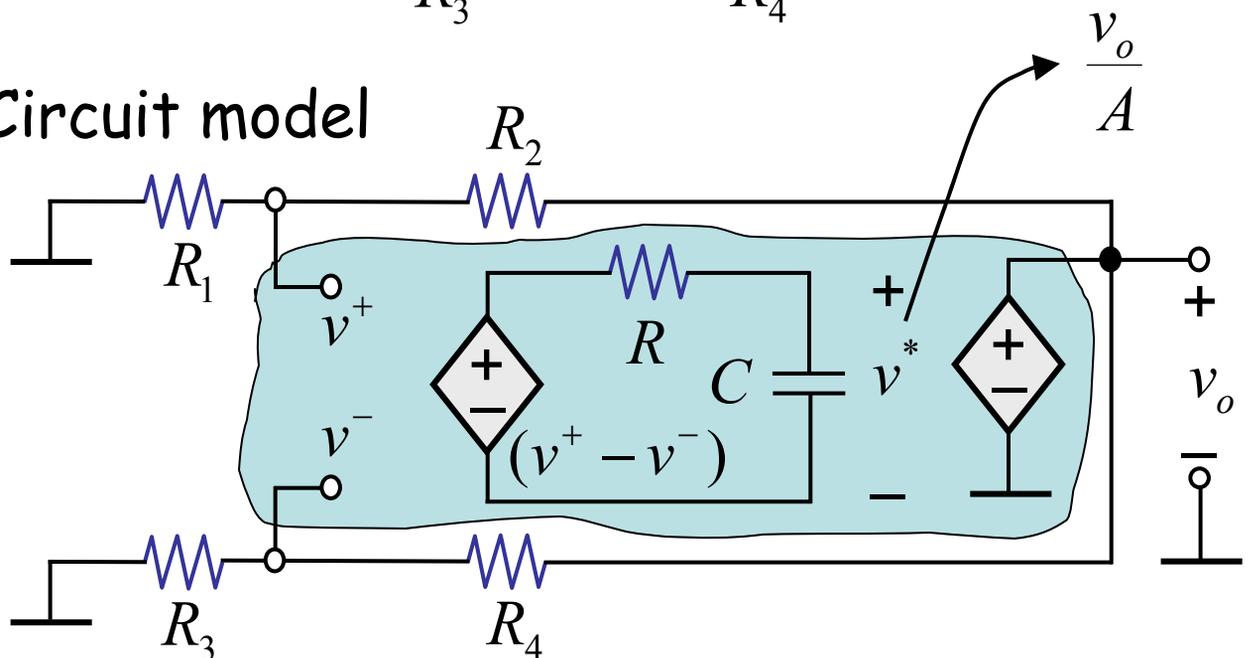

Let's develop equation representing time behavior of v_o .

Dynamics of op amp...

$$v_o = Av^* \quad \text{or} \quad v^* = \frac{v_o}{A}$$

$$RC \frac{dv^*}{dt} + v^* = v^+ - v^-$$

$$\frac{RC}{A} \frac{dv_o}{dt} + \frac{v_o}{A} = v^+ - v^-$$

$$= (\bar{\gamma}^+ - \bar{\gamma}^-) v_o$$

$$v^+ = \frac{v_o R_1}{R_1 + R_2} = \bar{\gamma}^+ v_o$$

$$v^- = \frac{v_o R_3}{R_3 + R_4} = \bar{\gamma}^- v_o$$

or

$$\frac{dv_o}{dt} + \left[\frac{1}{RC} + \frac{A}{RC} (\bar{\gamma}^- - \bar{\gamma}^+) \right] v_o = 0$$

neglect

$$\frac{dv_o}{dt} + \underbrace{\frac{A}{RC} (\bar{\gamma}^- - \bar{\gamma}^+)}_{\text{time}^{-1}} v_o = 0$$

or

$$\frac{dv_o}{dt} + \frac{v_o}{T} = 0 \quad \text{where} \quad T = \frac{RC}{A(\bar{\gamma}^- - \bar{\gamma}^+)}$$

$$v_o(0) = 0$$

Consider a small disturbance to v_o (noise).

$$\text{if } \bar{\gamma} > \bar{\gamma}^+$$

T is positive

$$v_o = K e^{-\frac{t}{T}} \quad \text{stable}$$

$$\text{if } \bar{\gamma}^+ > \bar{\gamma}$$



T is negative

$$v_o = K e^{\frac{t}{|T|}} \quad \text{unstable}$$

$$\text{if } \bar{\gamma}^+ = \bar{\gamma}$$




T is very large

$$v_o = K \quad \text{neutral}$$

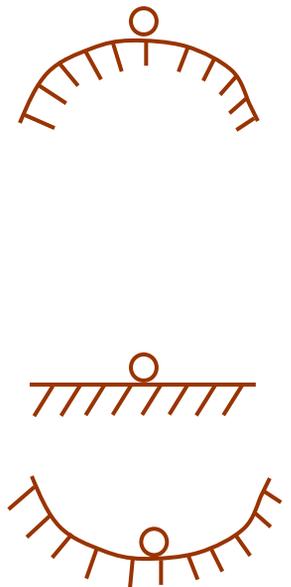
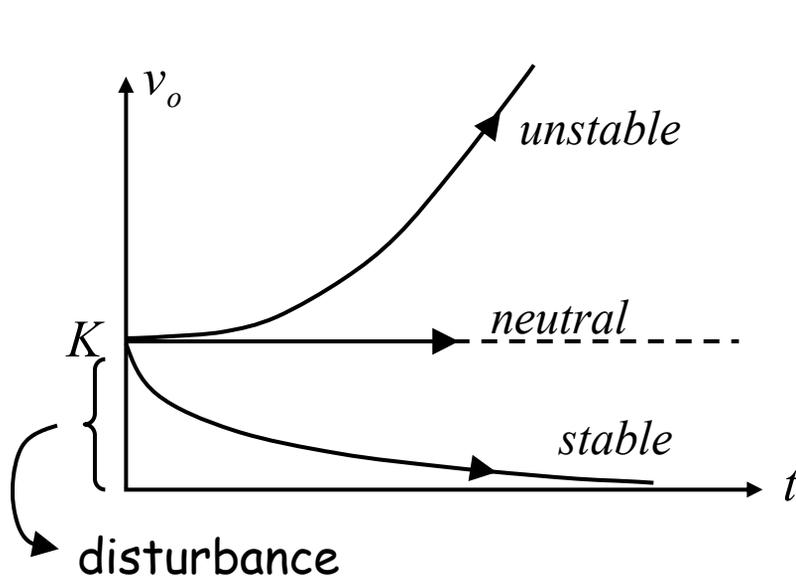


Now, let's build some useful circuits with positive feedback.

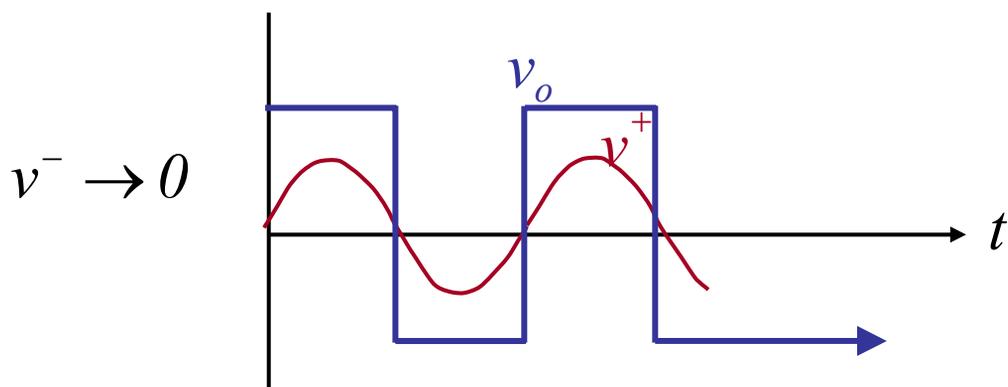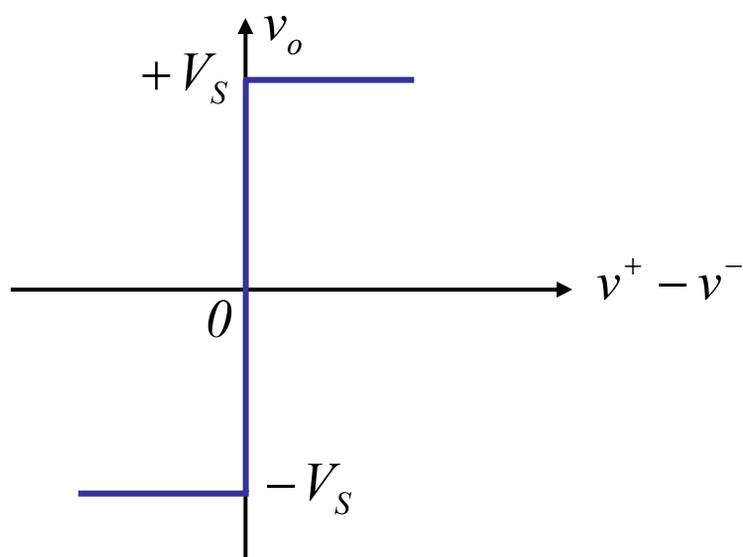
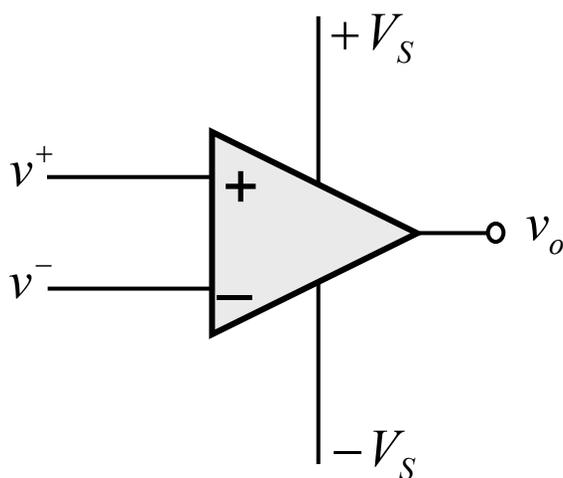
One use for instability: Build on the basic op amp as a comparator




Now, use positive feedback

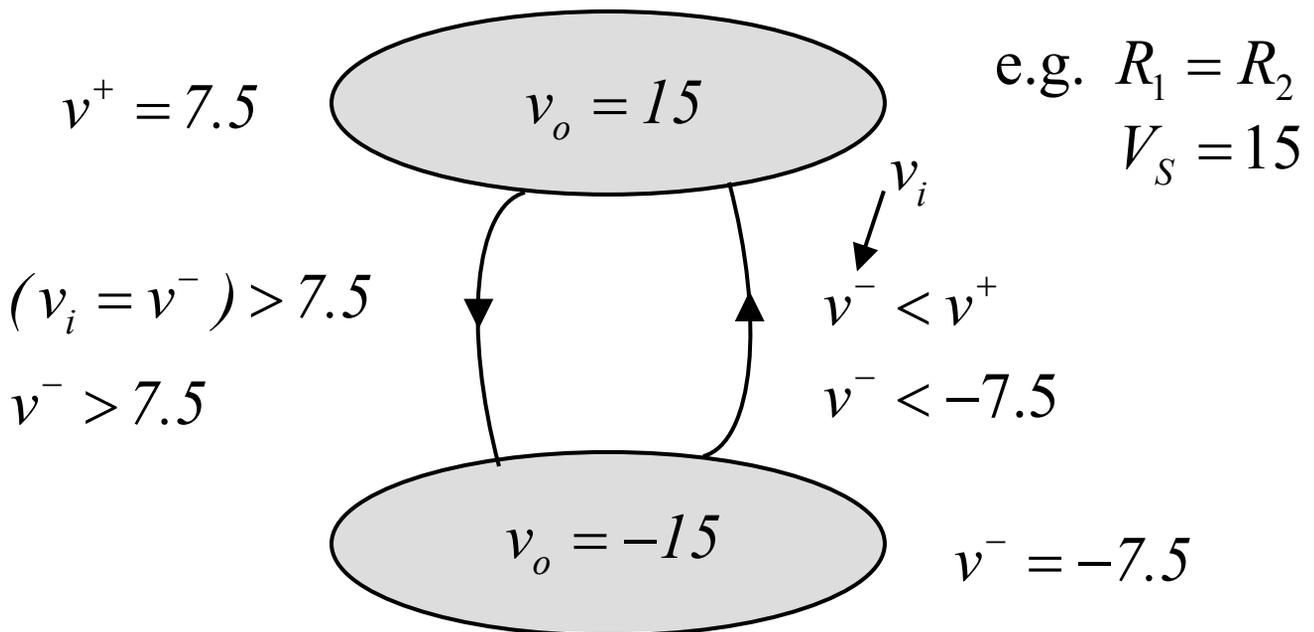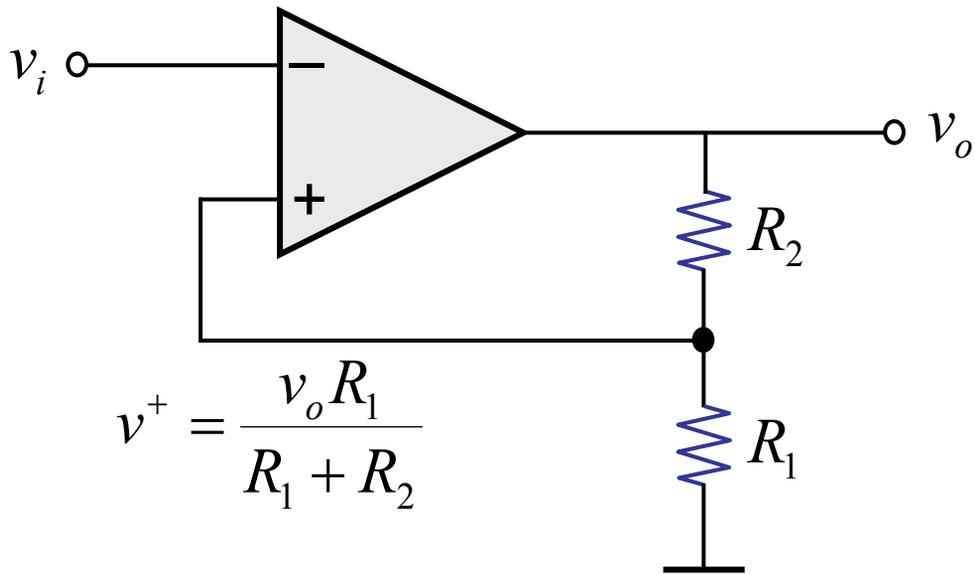


Now, use positive feedback

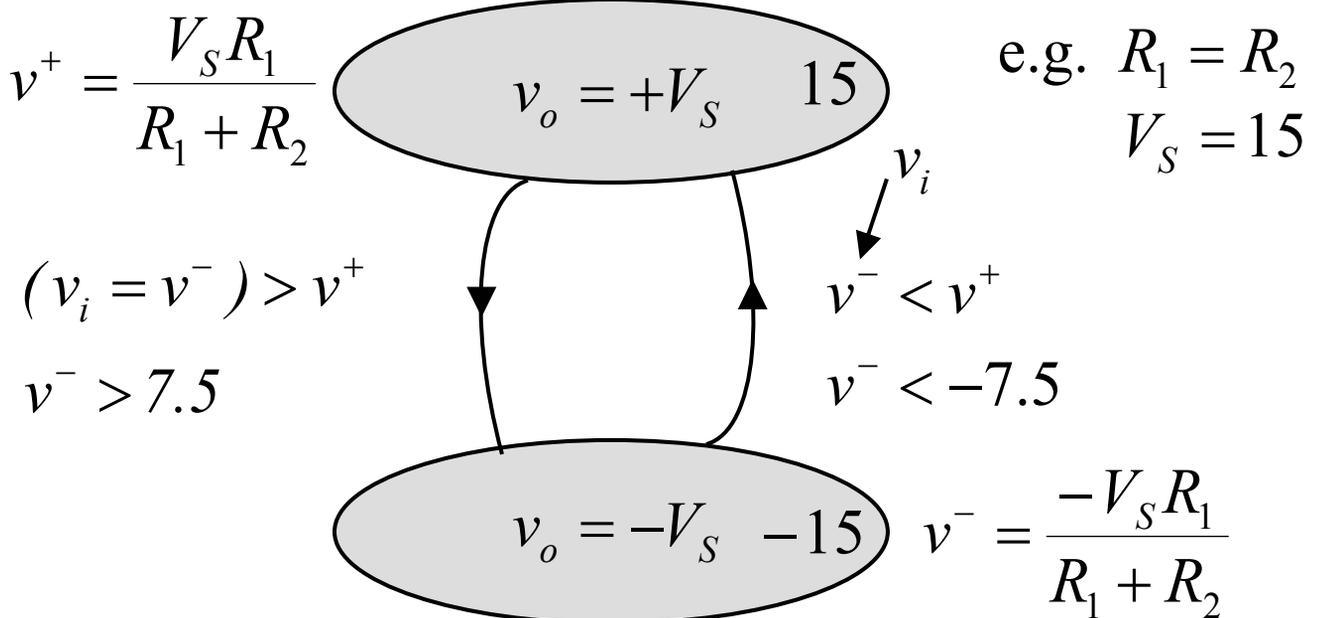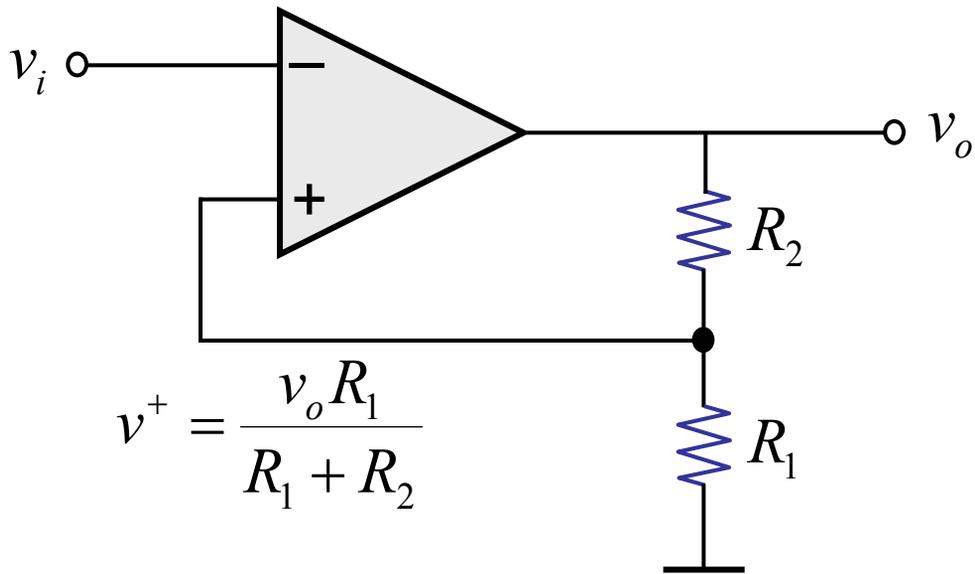

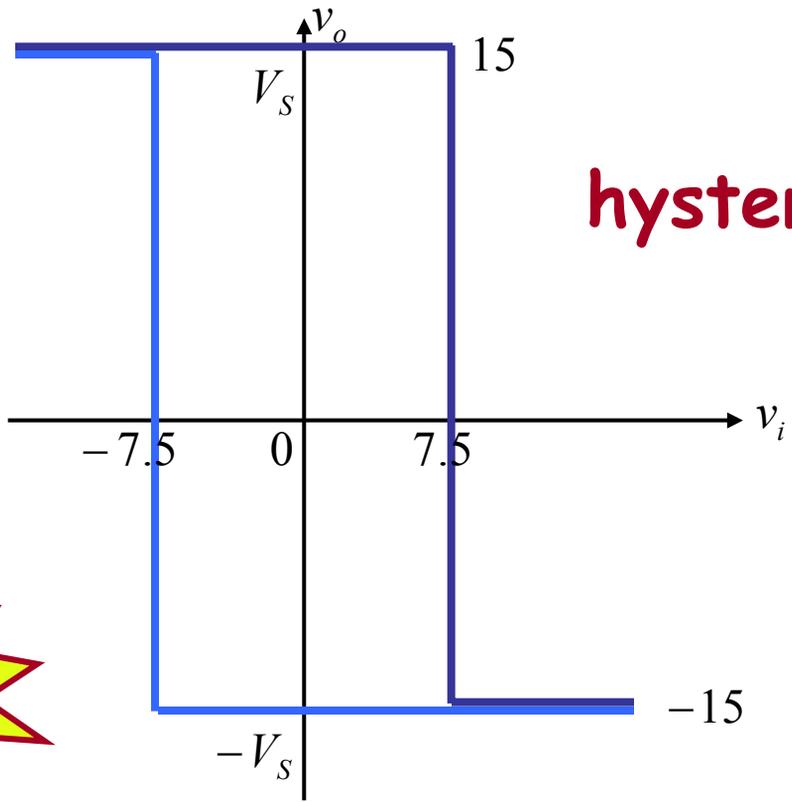



Demo

Why is hysteresis useful?

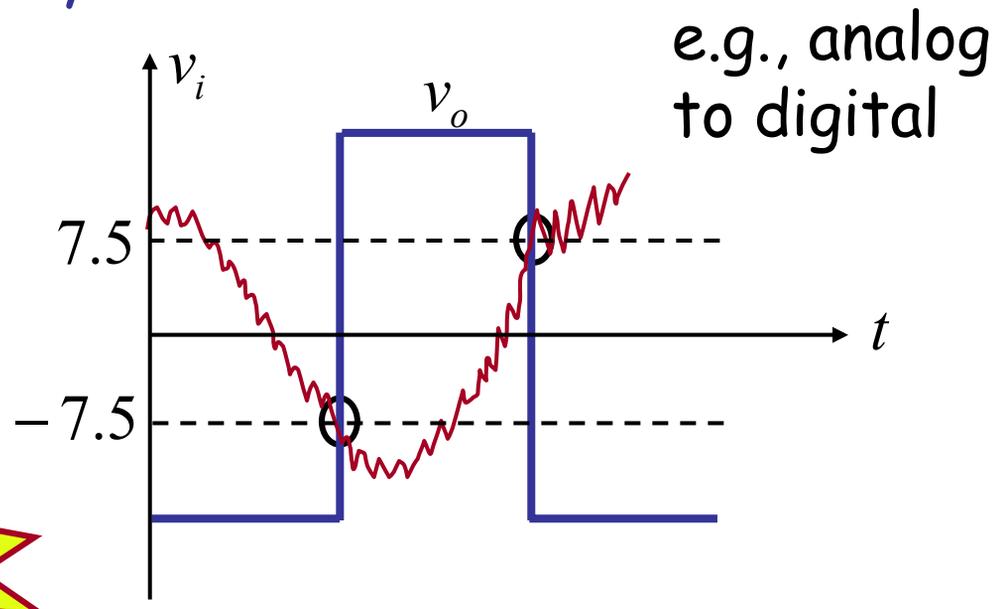

Demo

Oscillator — can create a clock

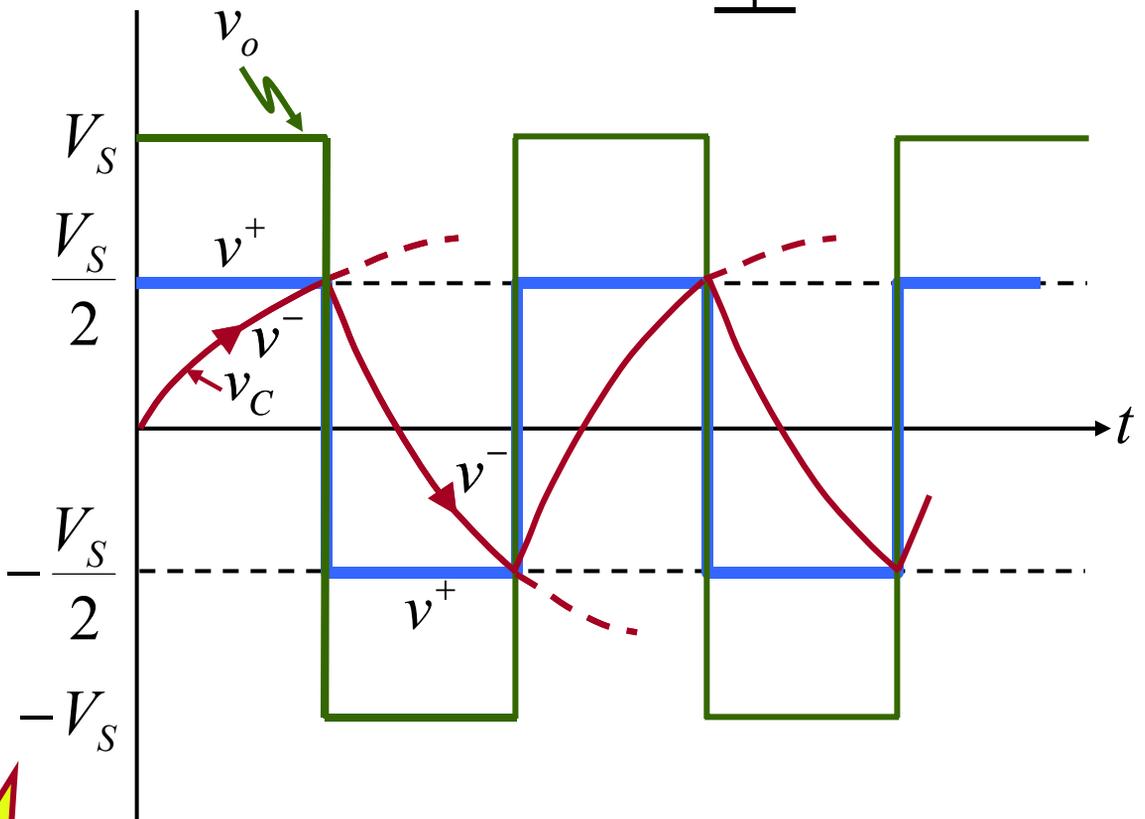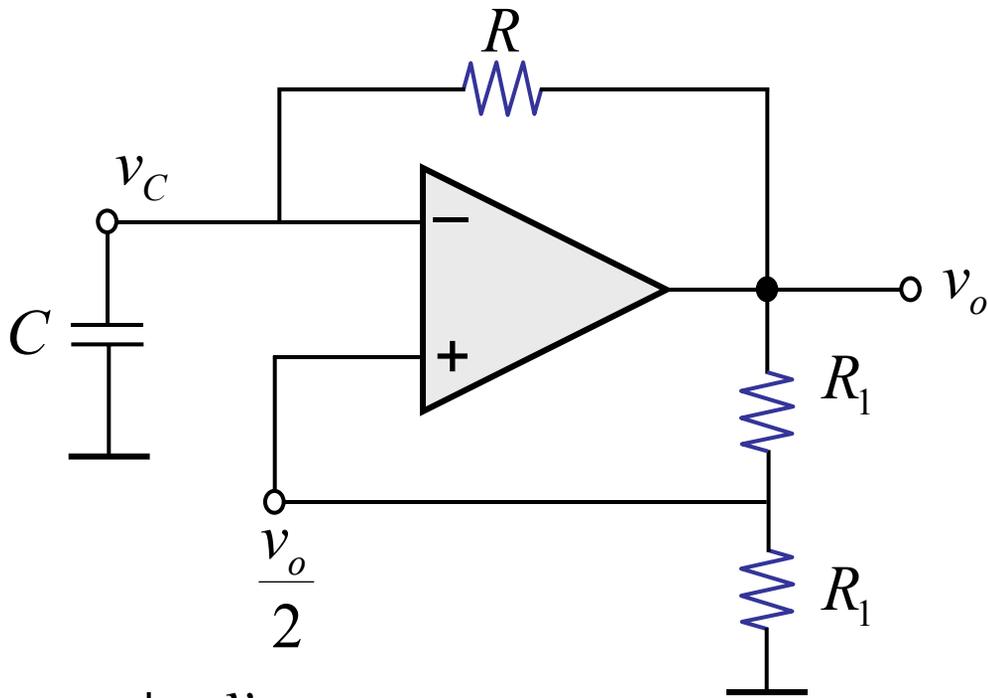


Assume $v_o = V_S$ at $t = 0$
 $v_C = 0$


Demo

Clocks in Digital Systems

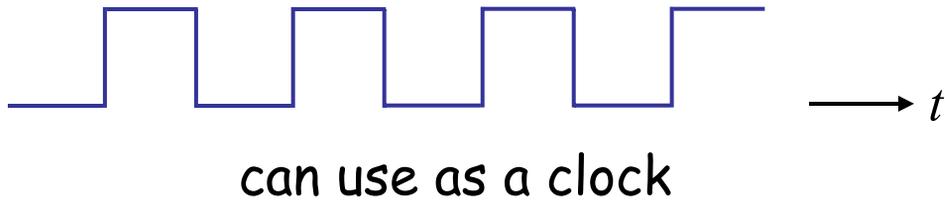- We built an oscillator using an op amp.



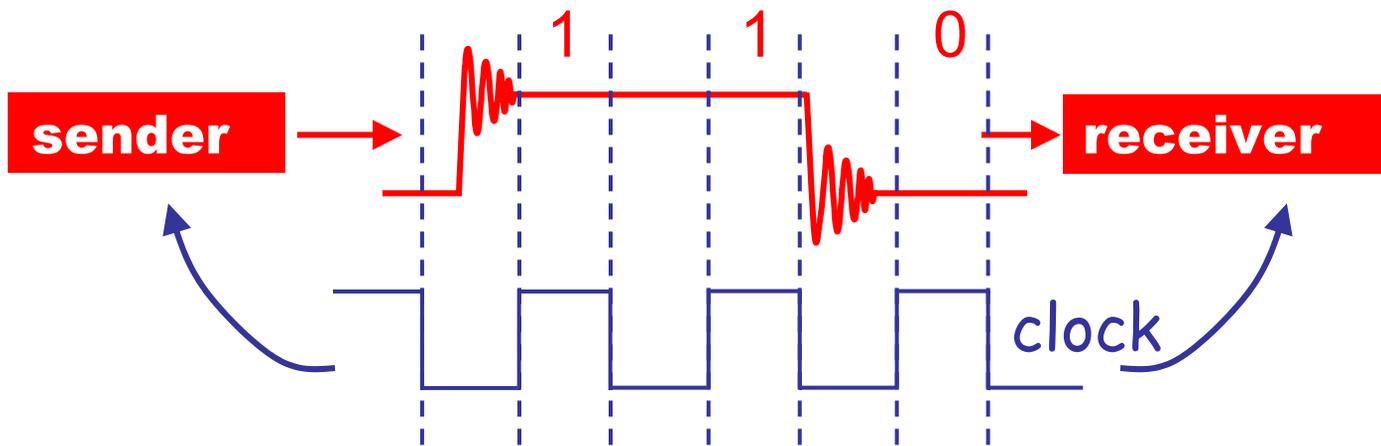- Why do we use a clock in a digital system?
(See page 735 of A & L)



(a) 1,1,0?

(b) When is the signal valid?

common timebase -- when to "look" at a signal
(e.g. whenever the clock is high)

→ Discretization of time
one bit of information associated with
an interval of time (cycle)