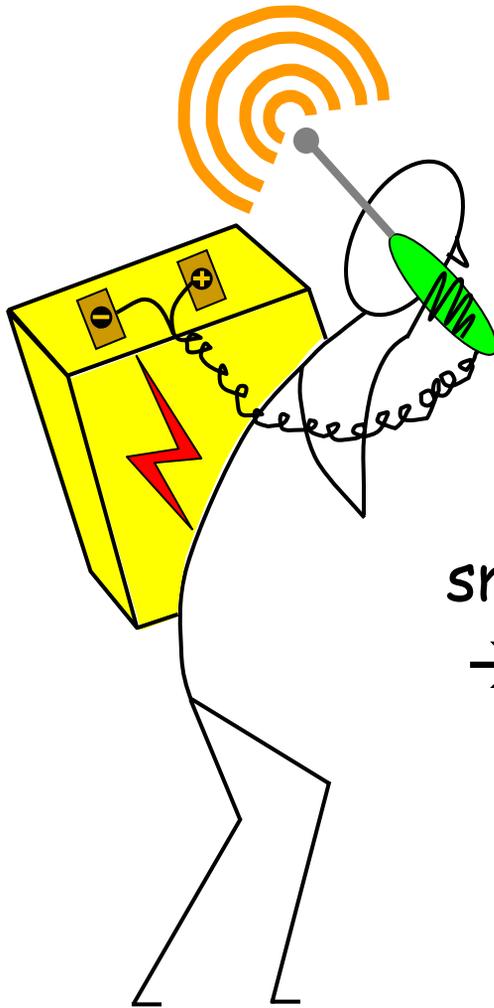


6.002

**CIRCUITS AND
ELECTRONICS**

Energy and Power

Why worry about energy?




small batteries
→ good

Today:

- How long will the battery last?
 - in standby mode
 - in active use
- Will the chip overheat and self-destruct?

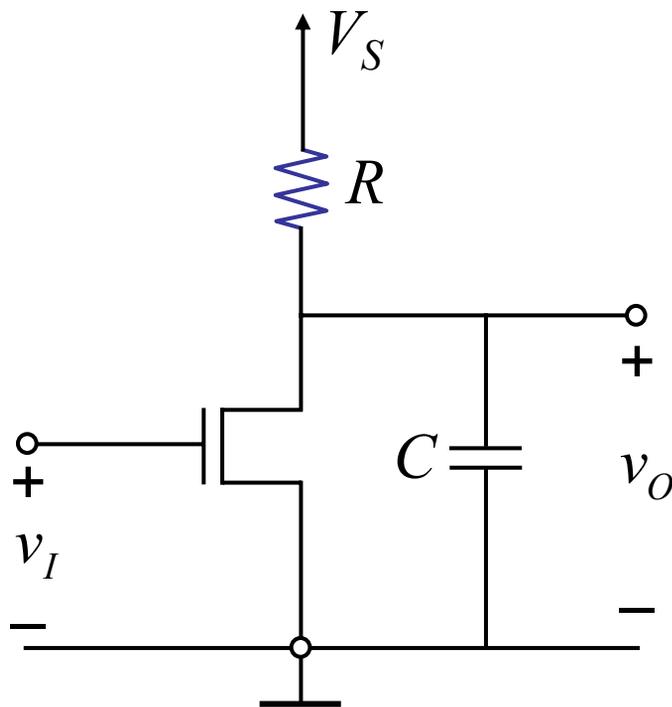Look at energy dissipation in MOSFET gates




C : wiring capacitance and C_{GS} of following gate

Let us determine
standby power
active use power

Let's work out a few related examples first.

Example 1:

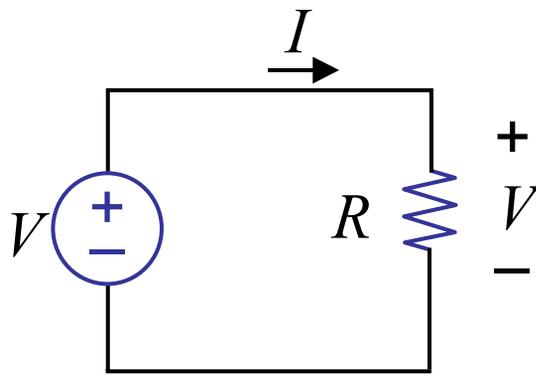


Power $P = VI = \frac{V^2}{R}$

Energy dissipated in time T


$$E = VIT$$

Example 1:

for our gate

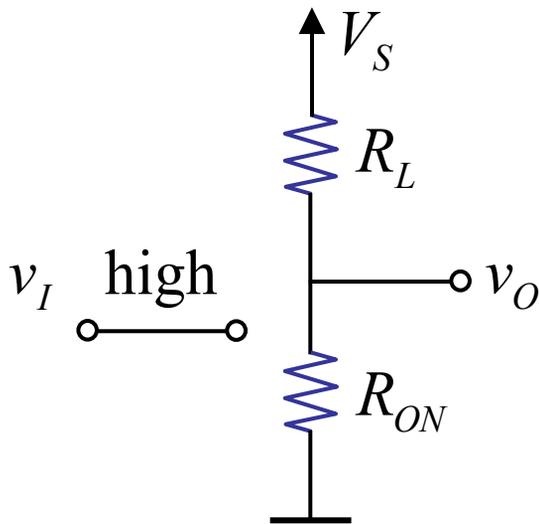



$$P = \frac{V_S^2}{R_L + R_{ON}}$$

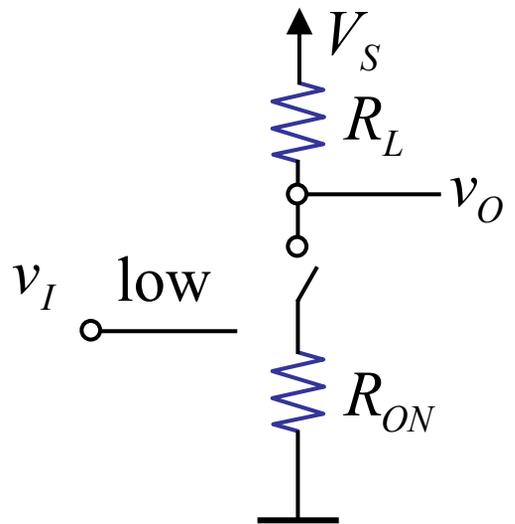

$$P = 0$$

Example 2:


Consider

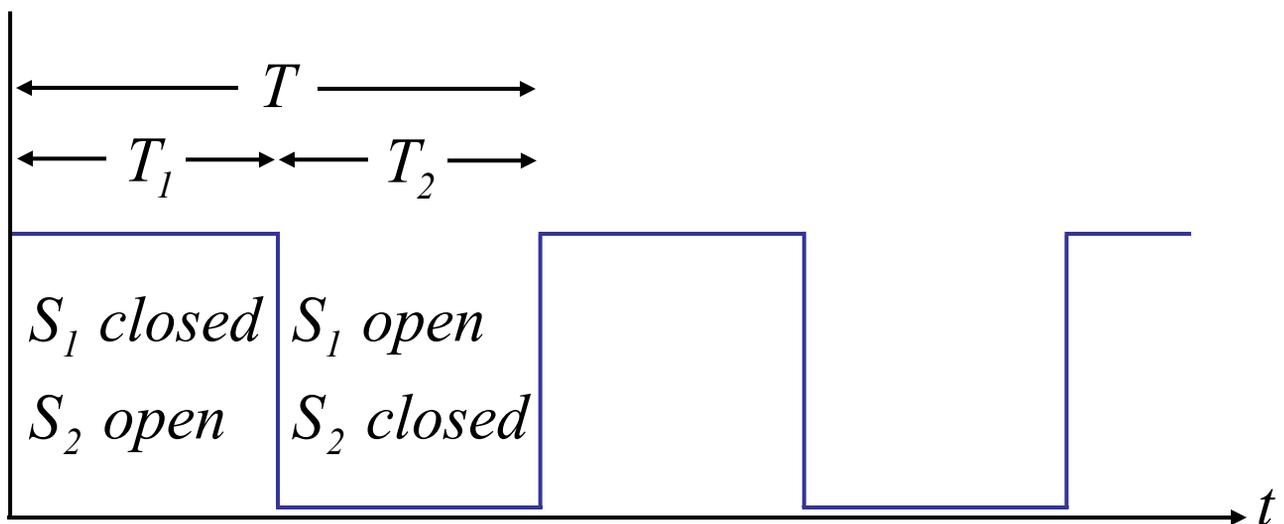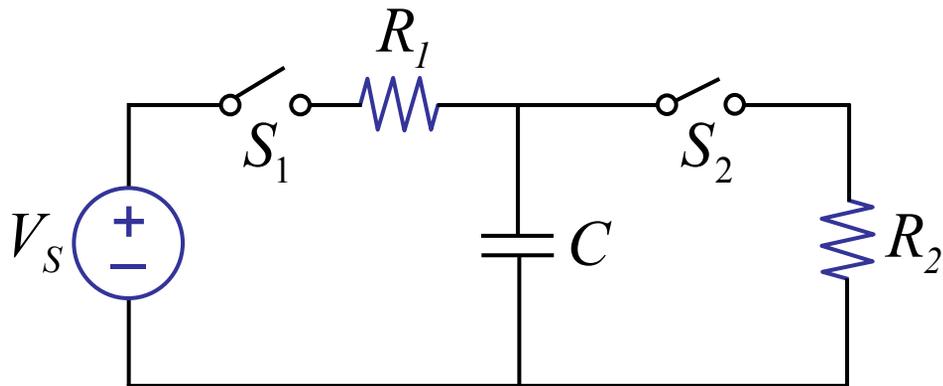



Find energy dissipated in each cycle.

Find average power \overline{P} .

T_1 : S_1 closed, S_2 open

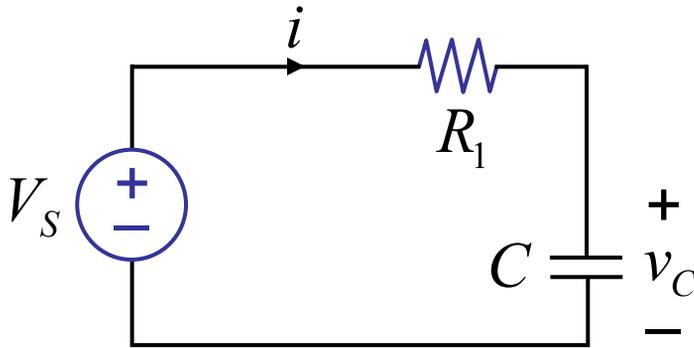

assume
 $v_C = 0$ at $t = 0$

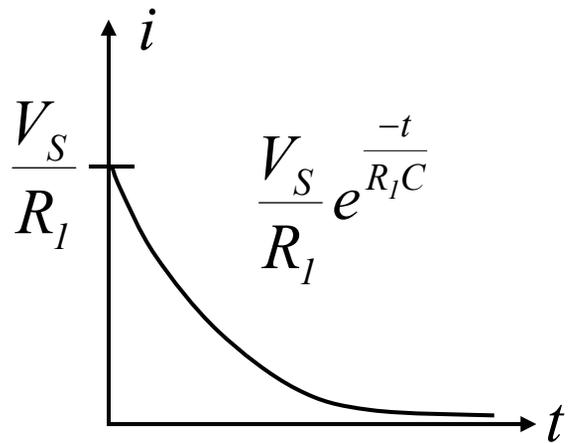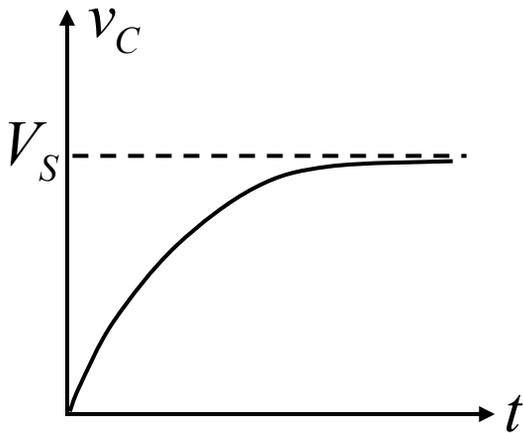

Total energy provided by source during T_1


$$\begin{aligned} E &= \int_0^{T_1} V_S i \, dt \\ &= \int_0^{T_1} \frac{V_S^2}{R_1} e^{\frac{-t}{R_1 C}} \, dt \\ &= -\frac{V_S^2}{\cancel{R_1} R_1 C} e^{\frac{-t}{R_1 C}} \Bigg|_0^{T_1} \\ &= C V_S^2 \left(1 - e^{\frac{-T_1}{R_1 C}} \right) \end{aligned}$$

$$\approx C V_S^2 \text{ if } T_1 \gg R_1 C$$

I.e., if we wait long enough

$$\left. \begin{aligned} \frac{1}{2} C V_S^2 \text{ stored on } C, \\ E_1 = \frac{1}{2} C V_S^2 \text{ dissipated in } R_1 \end{aligned} \right\} \text{Independent of } R!$$

T_2 : S_2 closed, S_1 open

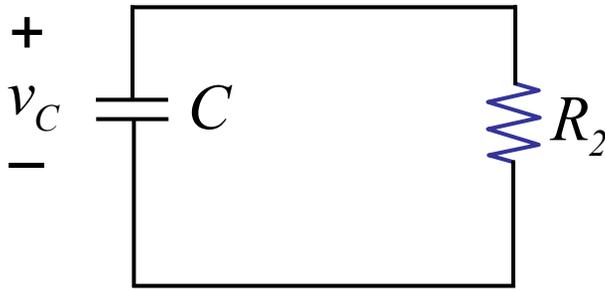

Initially, $v_C = V_S$ (recall $T_1 \gg R_1 C$)

So, initially,

$$\text{energy stored in capacitor} = \frac{1}{2} C V_S^2$$

Assume $T_2 \gg R_2 C$

So, capacitor discharges ~fully in T_2

So, energy dissipated in R_2 during T_2

$$E_2 = \frac{1}{2} C V_S^2$$

E_1, E_2 independent of R_2 !

Putting the two together:

Energy dissipated in each cycle

$$E = E_1 + E_2$$

$$= \frac{1}{2}CV_s^2 + \frac{1}{2}CV_s^2$$

$$E = CV_s^2 \text{ energy dissipated in}$$

charging & discharging C

Assumes C charges and discharges fully.

Average power

$$\bar{P} = \frac{E}{T}$$


$$= \frac{CV_s^2}{T}$$

$$= CV_s^2 f$$


★★

frequency $f = \frac{1}{T}$


Back to our inverter —

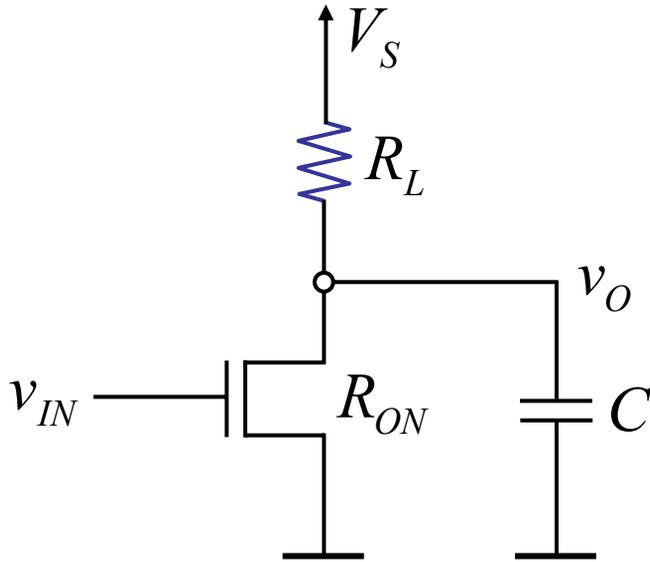


What is \bar{P} for the following input?

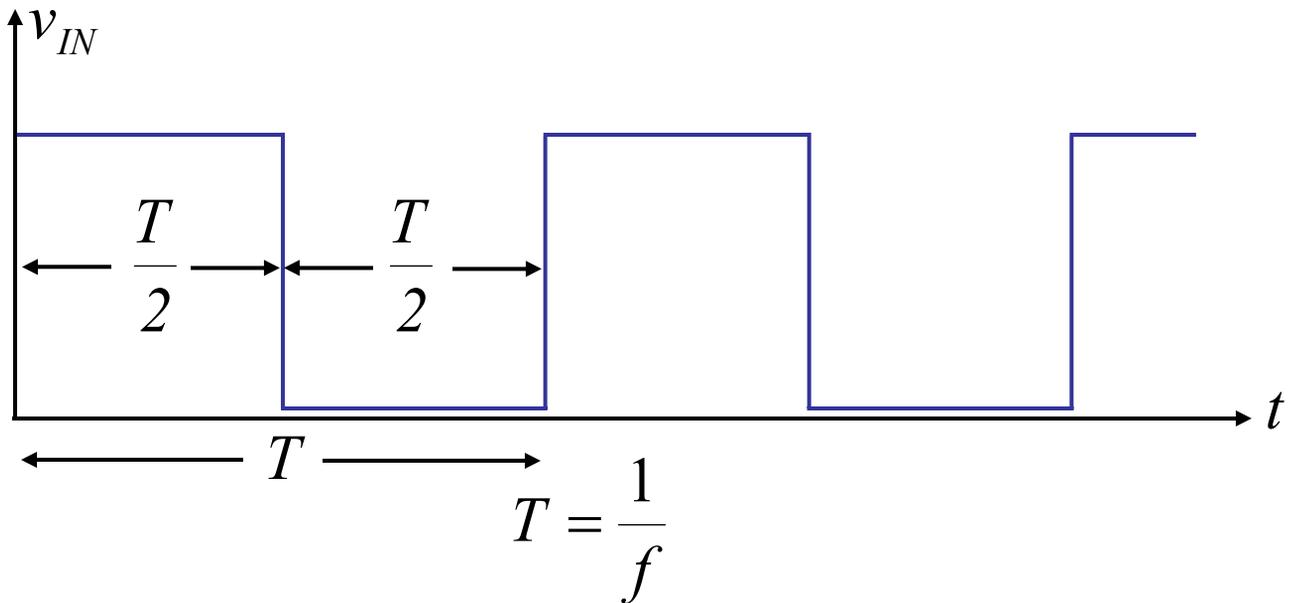

Equivalent Circuit

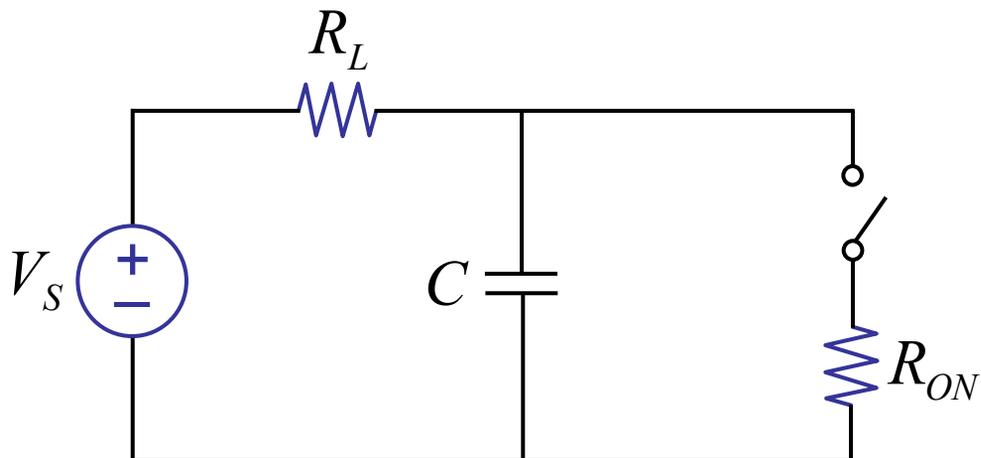

What is \bar{P} for the following input?

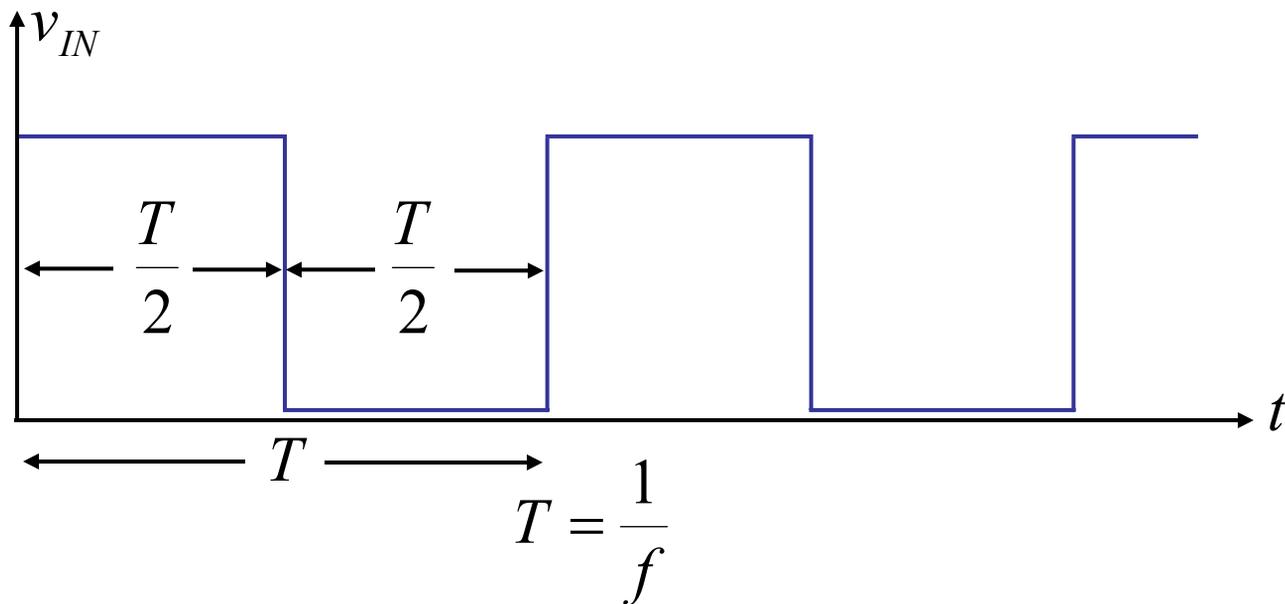

What is \bar{P} for gate?

We can show (see section 12.2 of A & L)

$$\bar{P} = \frac{V_S^2}{2(R_L + R_{ON})} + CV_S^2 f \frac{R_L^2}{(R_L + R_{ON})^2}$$

when $R_L \gg R_{ON}$

$$\bar{P} = \frac{V_S^2}{2R_L} + CV_S^2 f$$

remember ★

\bar{P}_{STATIC}

independent of f .
MOSFET ON half
the time.

remember ★★

$\bar{P}_{DYNAMIC}$

related to switching
capacitor

What is \bar{P} for gate?

when $R_L \gg R_{ON}$

$$\bar{P} = \frac{V_S^2}{2R_L} + CV_S^2 f$$

In standby mode,
half the gates in a
chip can be
assumed to be on.

So \bar{P}_{STATIC} per
gate is still $\frac{V_S^2}{2R_L}$.

Relates to standby
power.

In standby mode,
 $f \rightarrow 0$,
so dynamic power
is 0

Some numbers...

a chip with 10^6 gates clocking
at 100 MHz

$$C = 1fF$$

$$R_L = 10k\Omega$$

$$f = 100 \times 10^6$$

$$V_S = 5V$$

$$\bar{P} = 10^6 \left[\frac{25}{2 \times 10^4} + 10^{-15} \times 25 \times 100 \times 10^6 \right]$$

$$= 10^6 [1.25 \text{ milliwatts} + 2.5 \text{ microwatts}]$$

problem!

must get rid of this

1.25KW!

2.5W

not bad

$$\propto V_S^2$$

$$\propto f$$

reduce V_S

$$5V \rightarrow 1V$$

$$2.5W \rightarrow 150mW$$

