

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Science**

**6.002 - Electronic Circuits**  
**Fall 2000**

**Homework #7**  
**Handout F00-036**

**Issued 10/19/2000 - Due 10/27/2000**


**Reading:** 8.2, Chapter 9, 10.1, 10.2, 10.3

**Exercise 7.1:** a) Exercise 9.1, Chapter 9.  
 b) Repeat part (a) with capacitors replaced by inductors. Take the value of each inductor in mH to be numerically equal to the value of the capacitor it replaces in  $\mu F$ .

**Exercise 7.2:** Exercise 10.16, Chapter 10.

**Exercise 7.3:** Exercise 10.22, Chapter 10.

**Problem 7.1:**

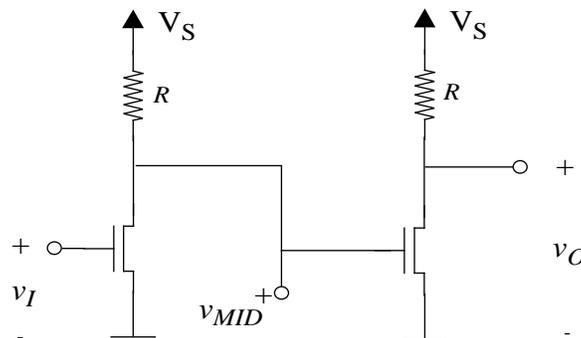

The two-stage non-inverting MOSFET amplifier shown above is the same as the one examined in Problem 6.2 except that it is biased differently. In this problem,  $V_I$  is chosen such that  $V_I = V_{MID} = V_O$ .


a) Show that the input bias  $V_I$  for which  $V_I = V_{MID} = V_O$  is given by

$$V_I = V_T + \frac{-1 + \sqrt{1 + 2KR(V_S - V_T)}}{KR}.$$

b) Draw the small-signal circuit for the amplifier and use it to determine the small-signal gain  $G = \frac{v_{out}}{v_{in}}$ . Express  $G$  as a function of  $K$ ,  $V_T$ ,  $V_I$ , and  $R$ .

**Problem 7.2:** Problem 10.22, Chapter 10.

**Problem 7.3:**

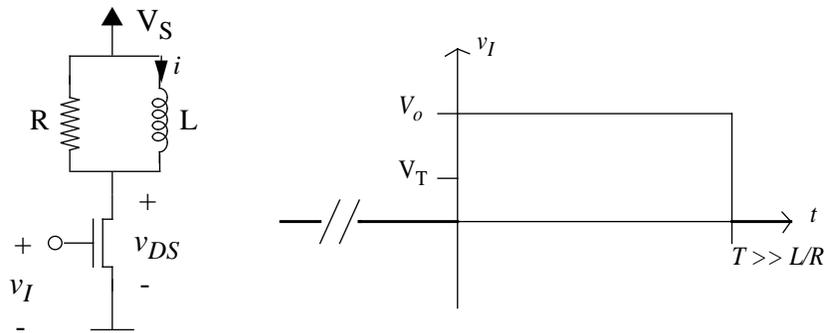

$$i_{DS} = \frac{K}{2}(v_{GS} - V_T)^2$$

The circuit shown is used to pulse the current in the coil of a relay. The design is such that the relay contacts close when the current reaches 70% of its steady-state value

(i.e. the value reached at the time  $T \gg \frac{L}{R}$ ).

a) Assume that the MOSFET operates in the saturation region for  $0 < t < T$ .

Determine and sketch  $i(t)$  and  $v_{DS}(t)$ , indicating clearly the waveforms for  $t < 0$ ,  $0 < t < T$ , and  $T < t$ .

b) For the case examined in part (a), what limit must be placed on the *maximum* coil current if the MOSFET is required to stay in the saturation region for  $0 < t < T$ ? Express the answer in terms of  $V_S$ ,  $R$ ,  $K$ ,  $V_T$ , and  $V_o$ .

c) For the case examined in part (a), what limit must be placed on the coil current if the maximum value of  $v_{DS}$  is limited to  $1.5V_S$ ?