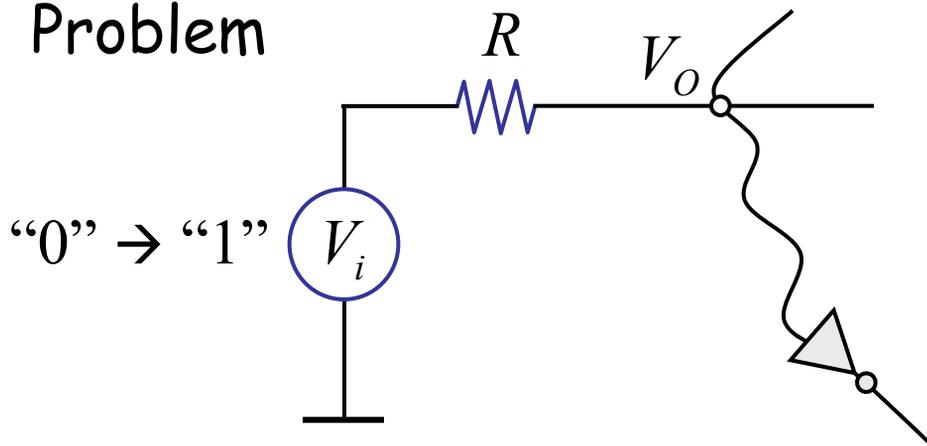



Violating the Abstraction Barrier

Case 1: The Double Take


Problem



expected

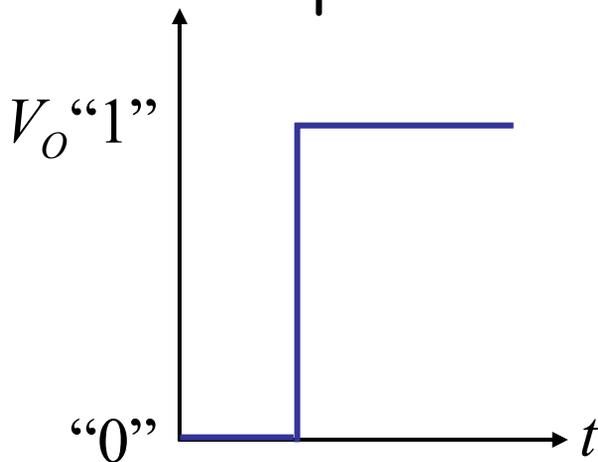


observed

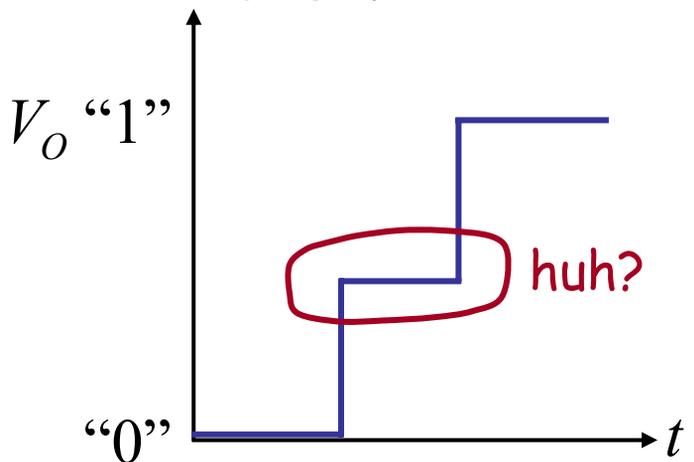

in forbidden region!


(a) DC case

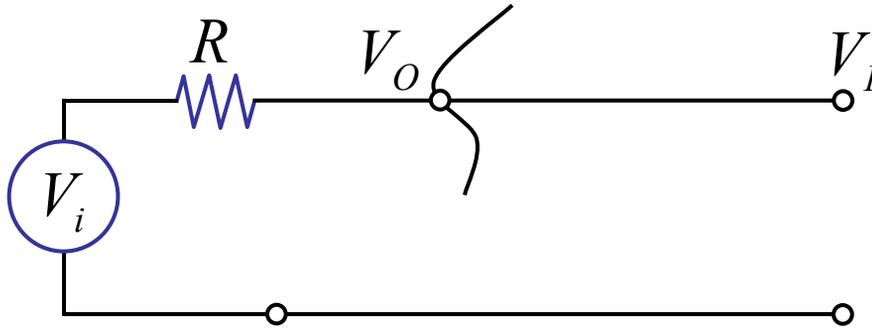

very high
impedance,
like open
circuit


$$V_i = 5V \text{ DC} \quad V_o = 5V \text{ DC} \quad V_1 = 5V \text{ DC} \longrightarrow \text{OK}$$

(b) Step

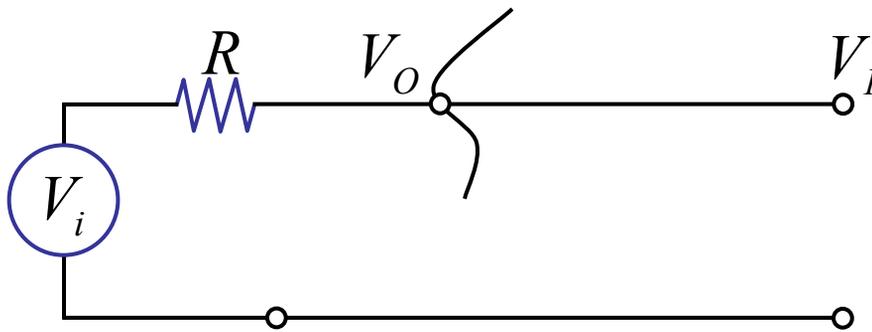


very high impedance,
like open
circuit


b.1

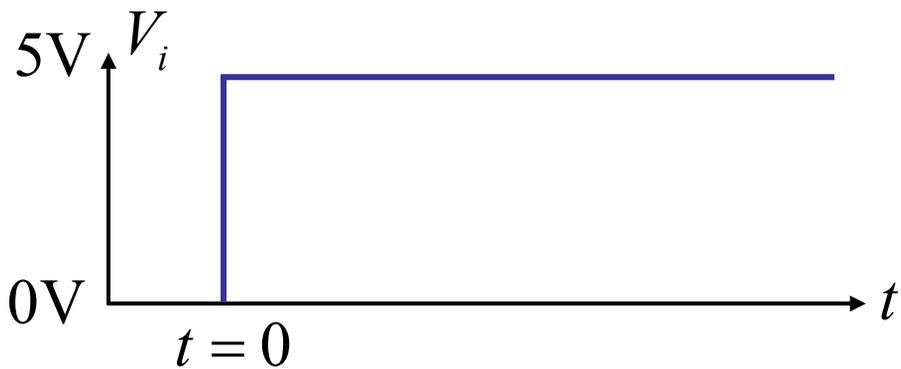


b.3

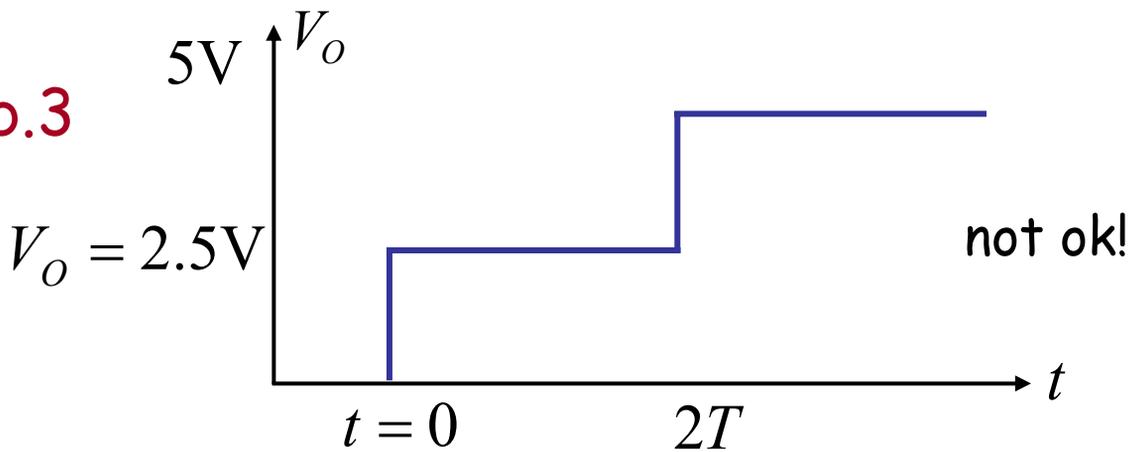

b.2

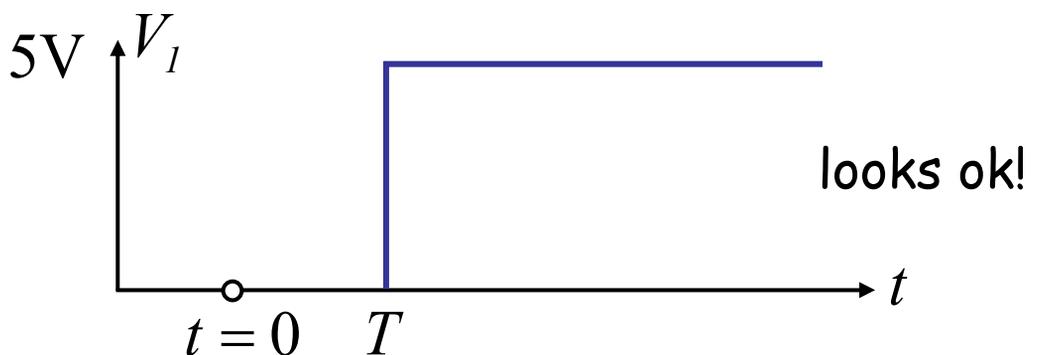


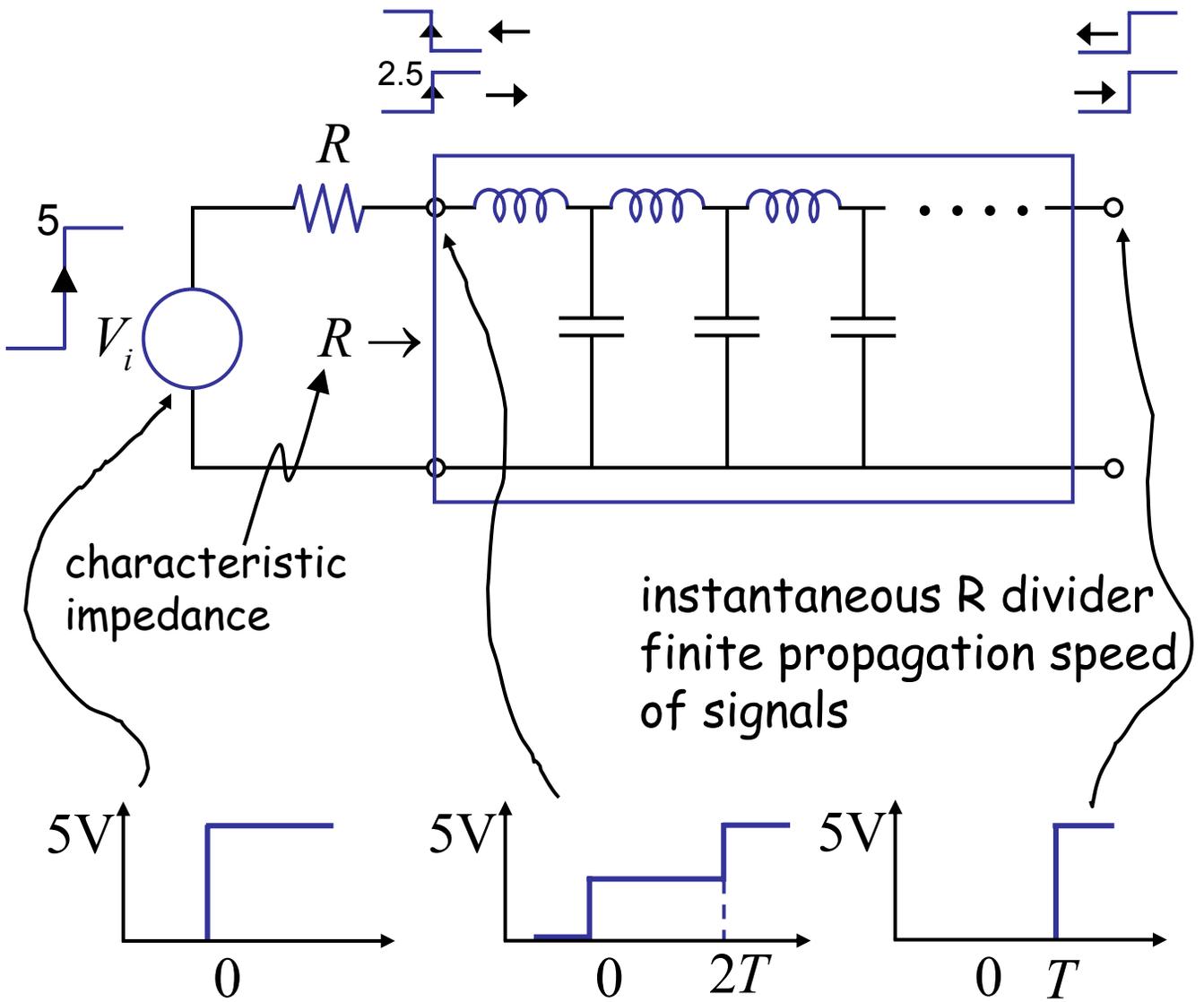

Question: So why did our circuits work?


1. Look only at V_I

DEMO

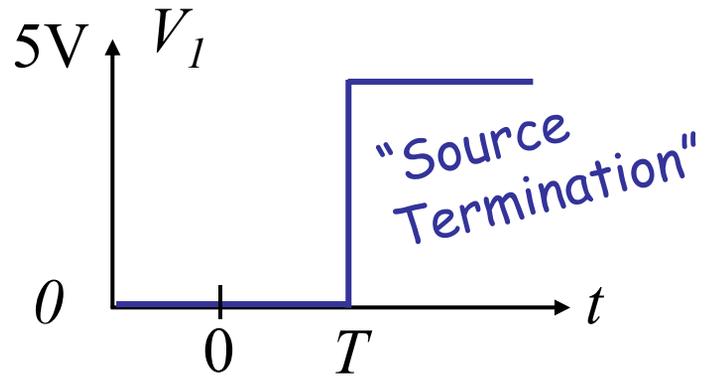


2. Keep wires short

DEMO
use small wire

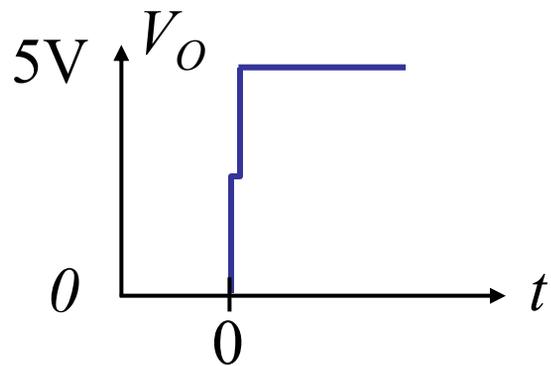

3. Termination


DEMO
add R at the end

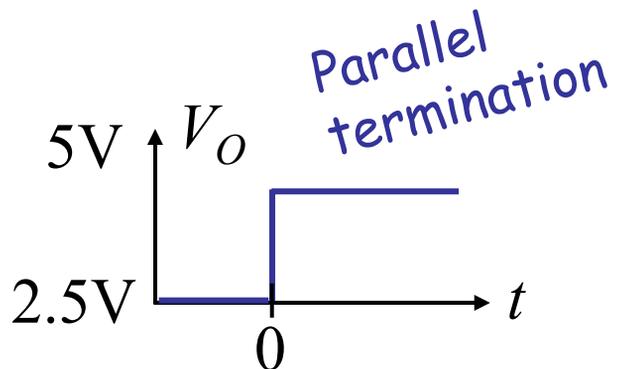


More in 6.014

Case 2: The Double Dip

Problem → strange spikes on supply

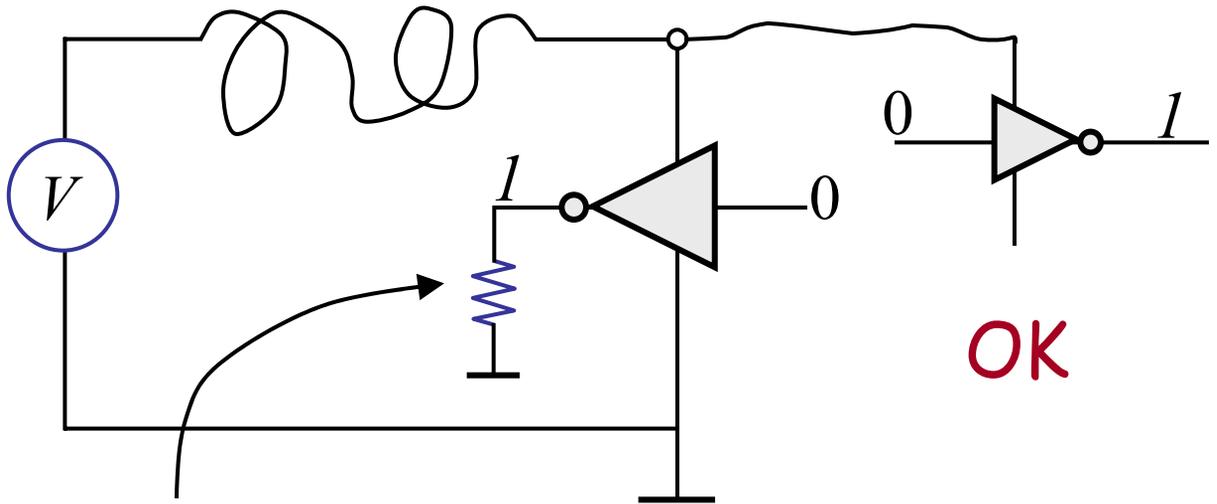



driving a $50\ \Omega$ resistor!

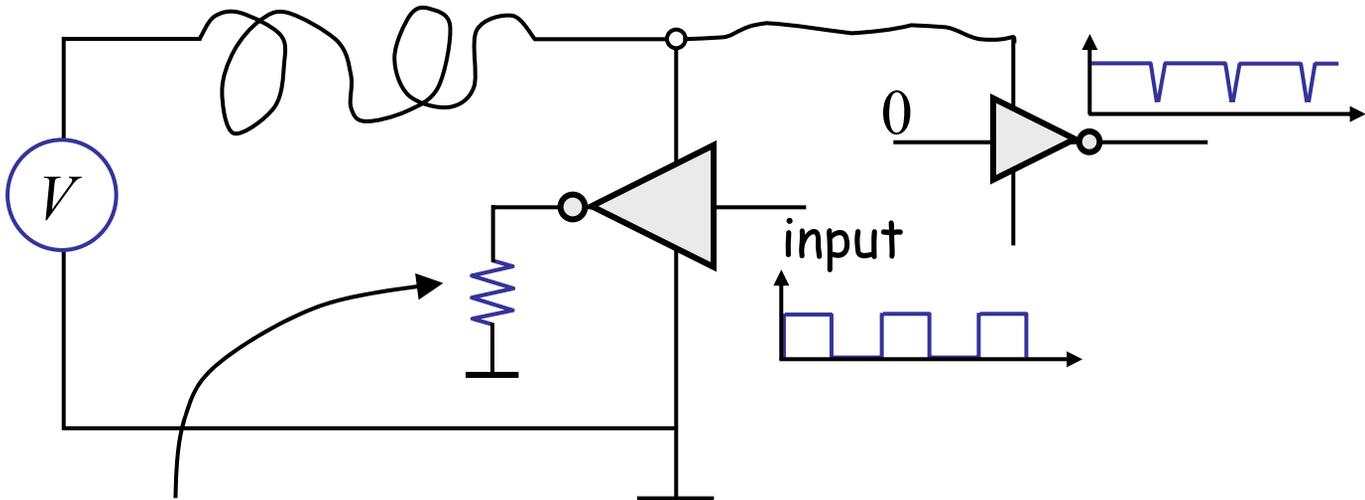

driving a $50\ \Omega$ resistor!

Why?


Drop across inductor

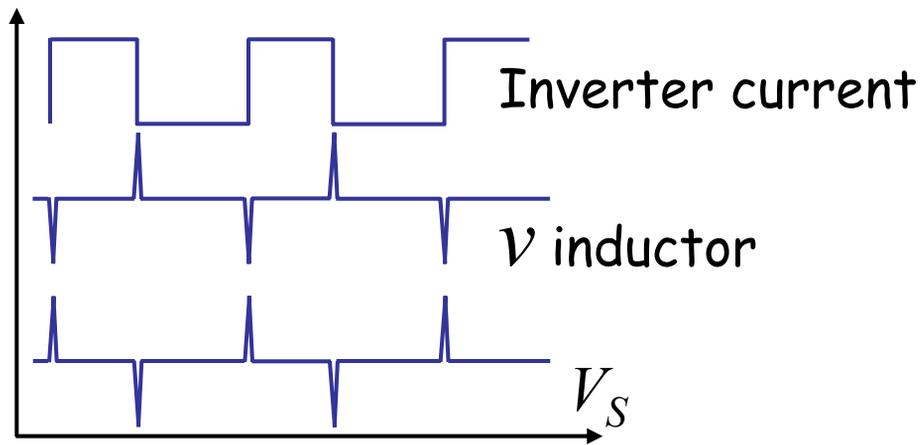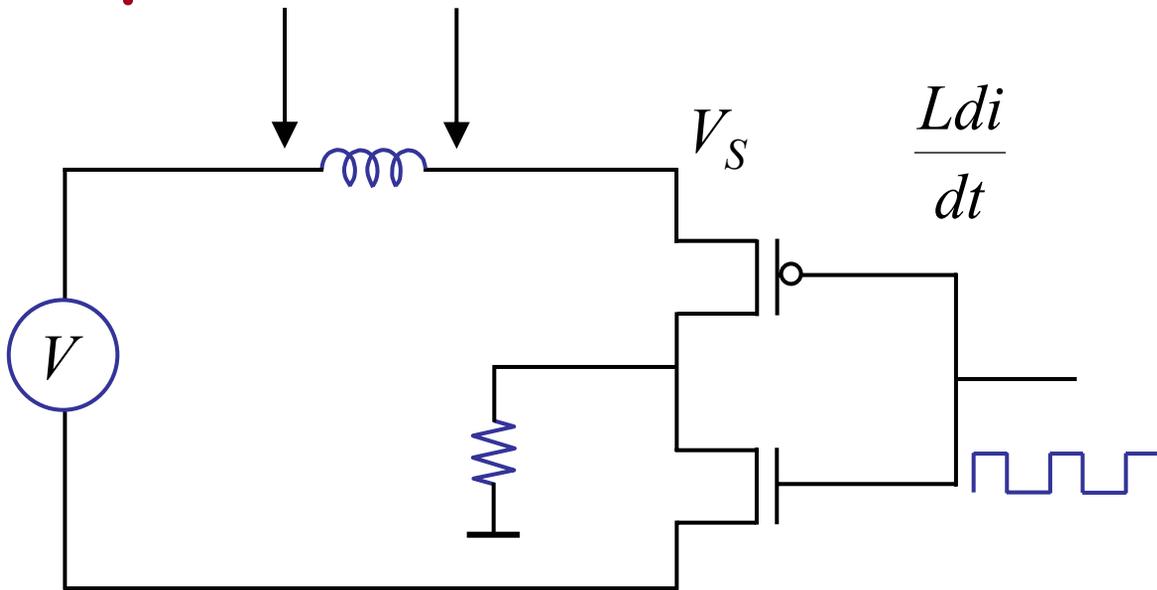


- solution
1. short wires
 2. low inductance wires
 3. avoid big current swings

Case 3: The Double Team, or, Slower may be faster!



Problem

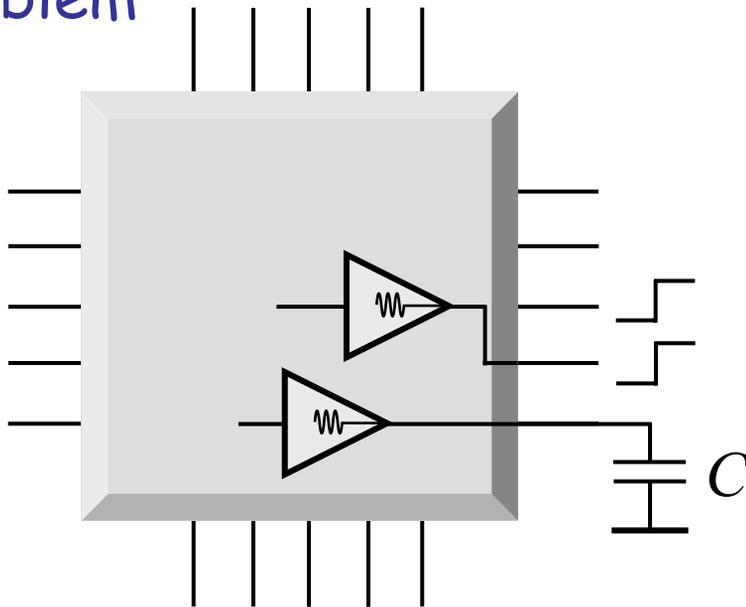

a given chip worked, but was slow.

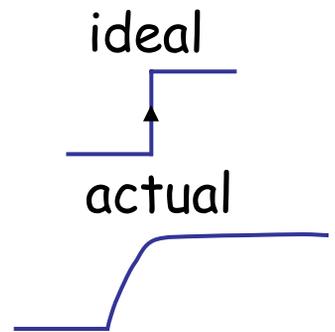


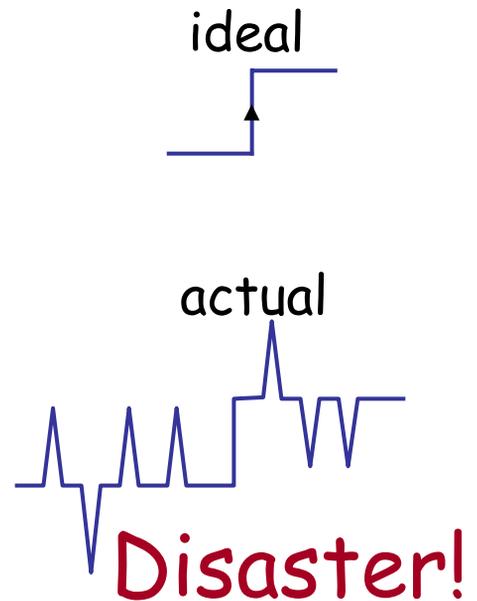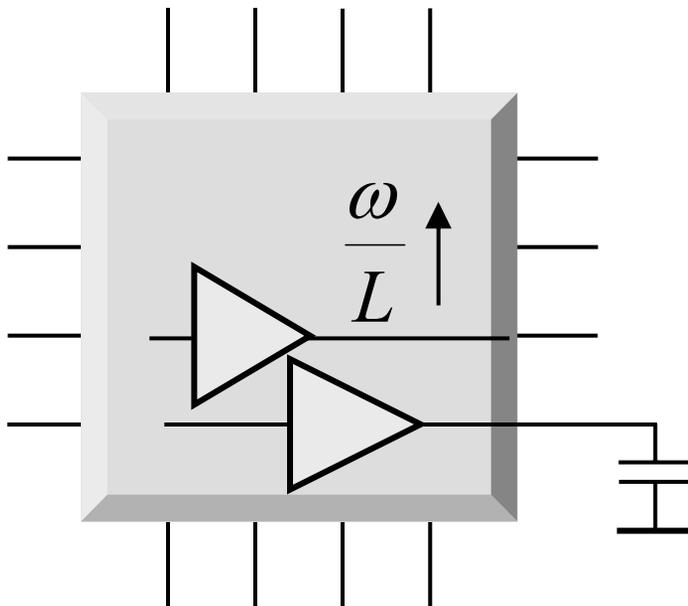Let's try speeding it up by using stronger drivers



Why?


Consider

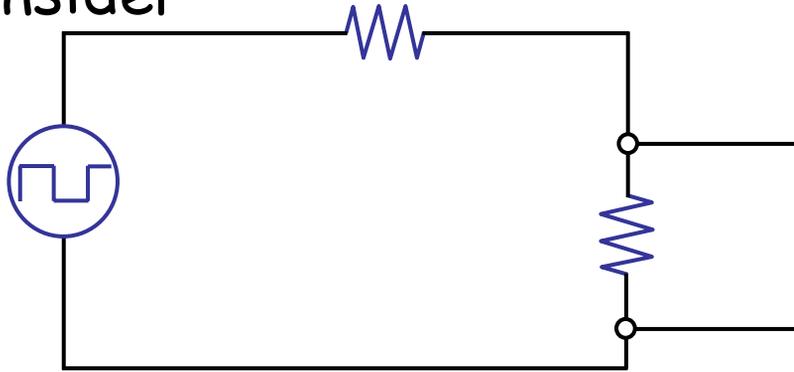

DEMO




ok

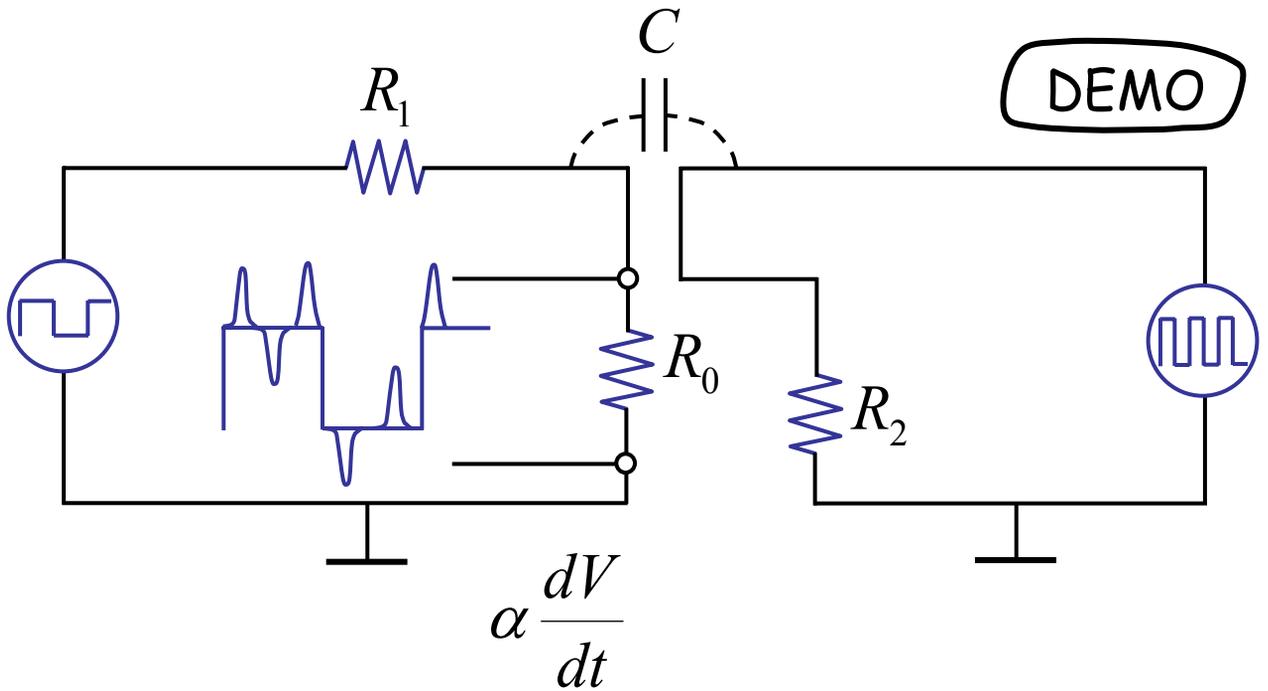


DEMO

$$C \frac{dV}{dt}$$


crosstalk!

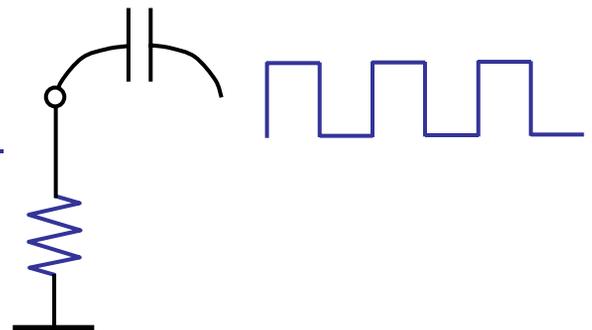

How does this relate to chip?

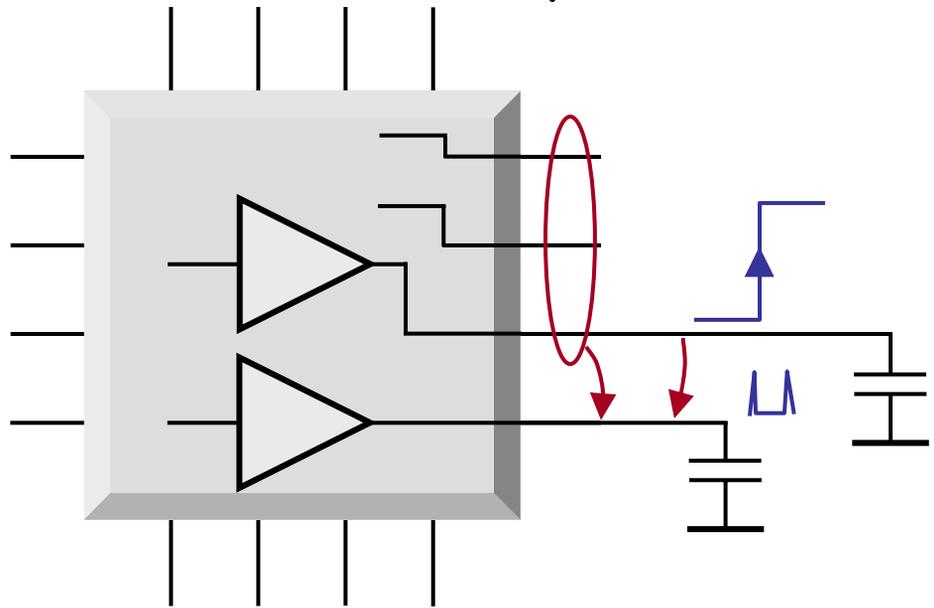


Solution

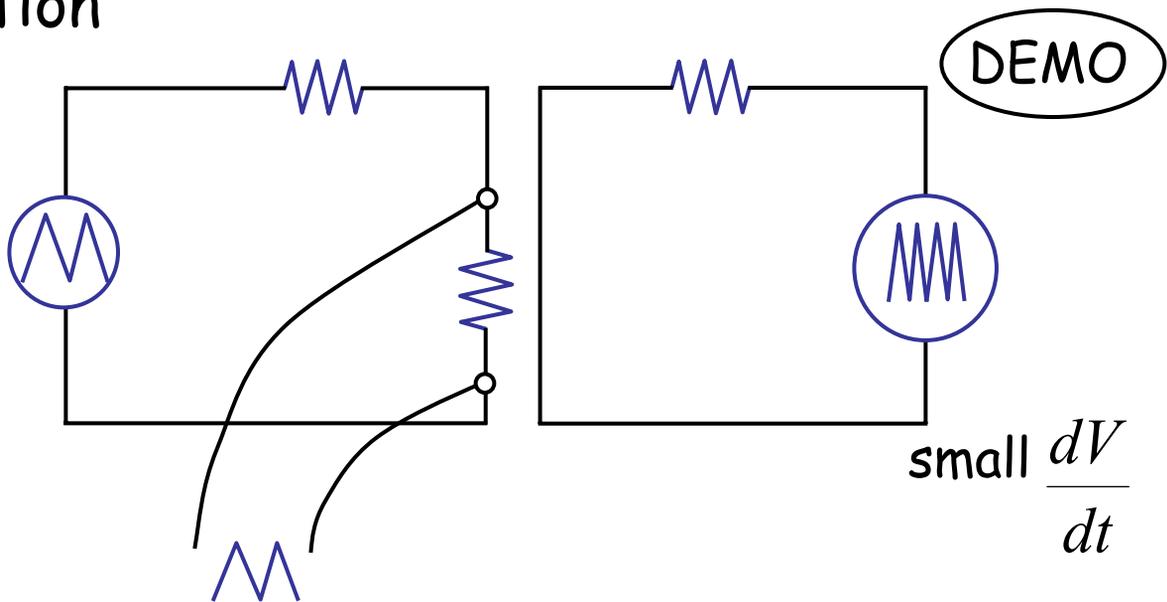


- Load output!
- put cap on outputs of chip
 - jitter edges
 - slew edges

Case 4: The Double Jump

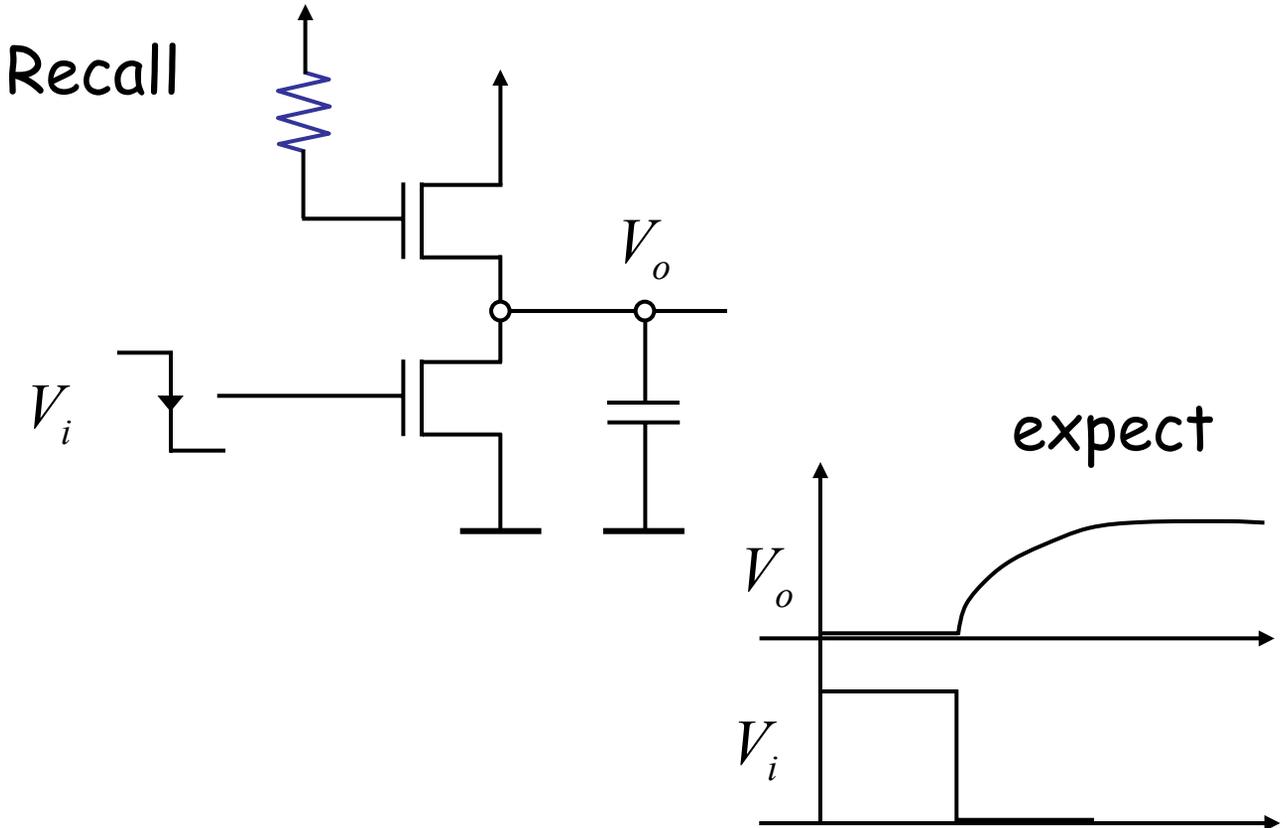Careful abstraction violation for the better...




but, observe

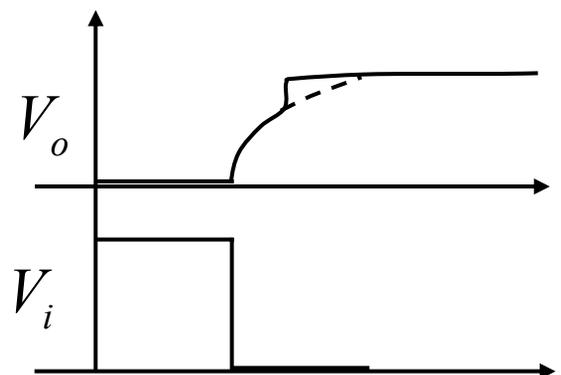

Case 4: The Double Jump

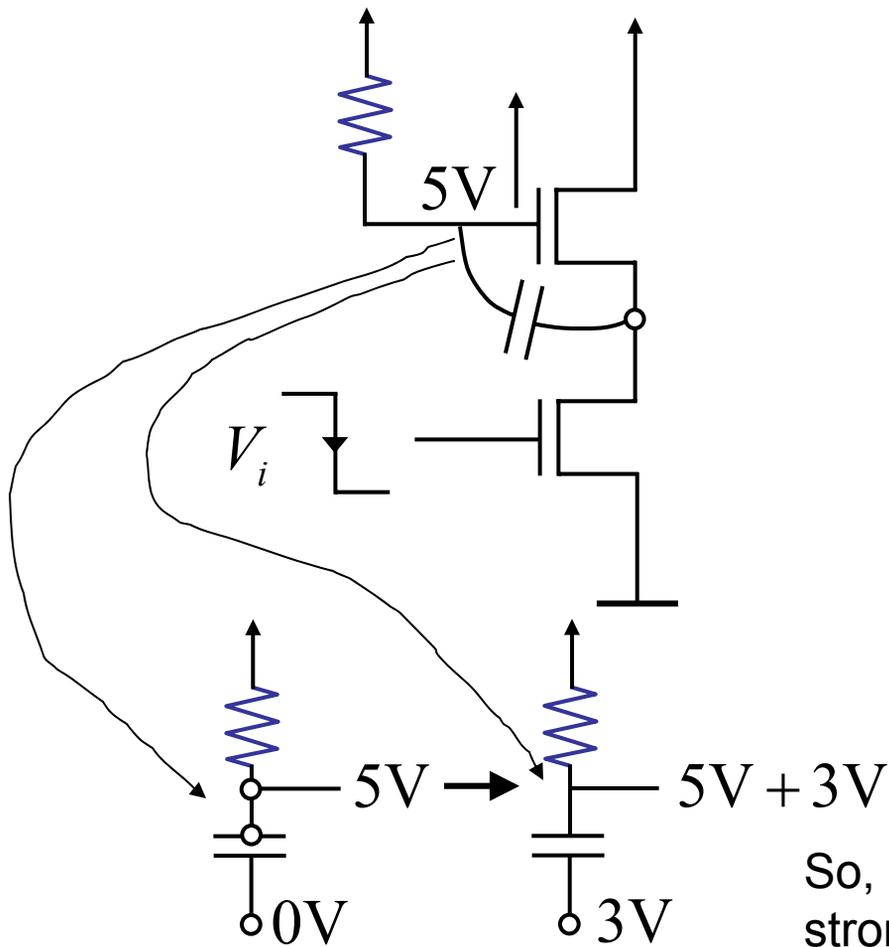Careful abstraction violation for the better...



So, pullup has stronger drive as output rises