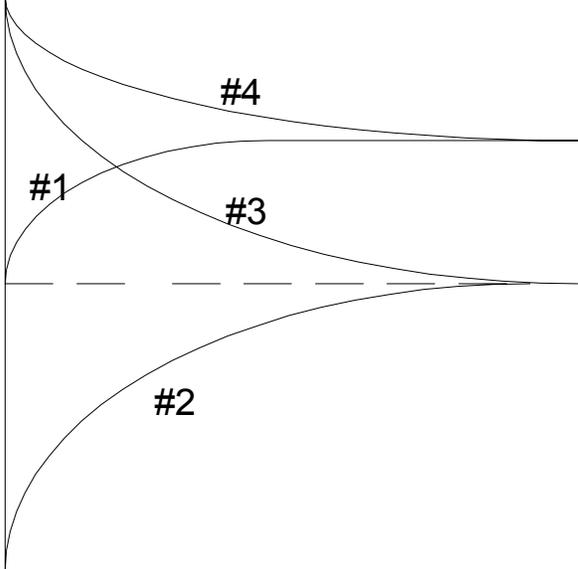




**6.002 Demo# 26**  
**RC Response**  
**Lecture 12**

**Agarwal Fall 00**

Purpose:  
Displays the response of an RC circuit for various initial and final conditions.


Steps:



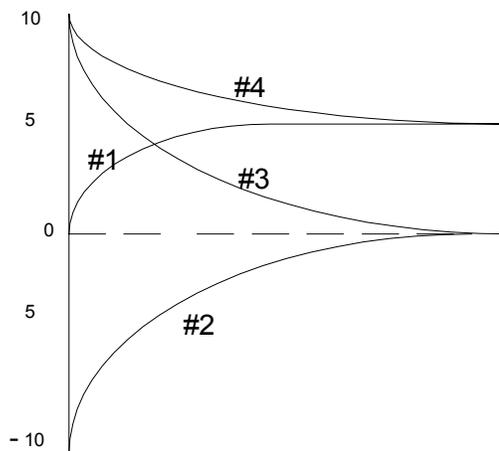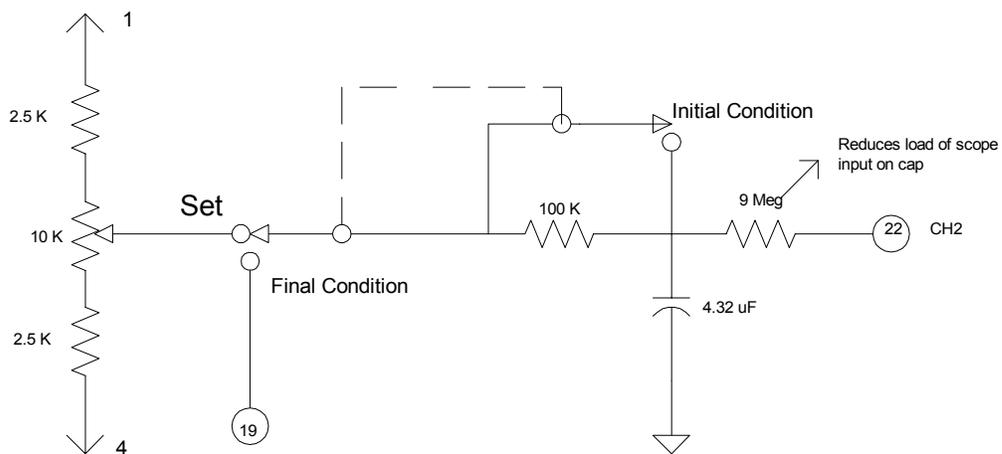

### Procedure:

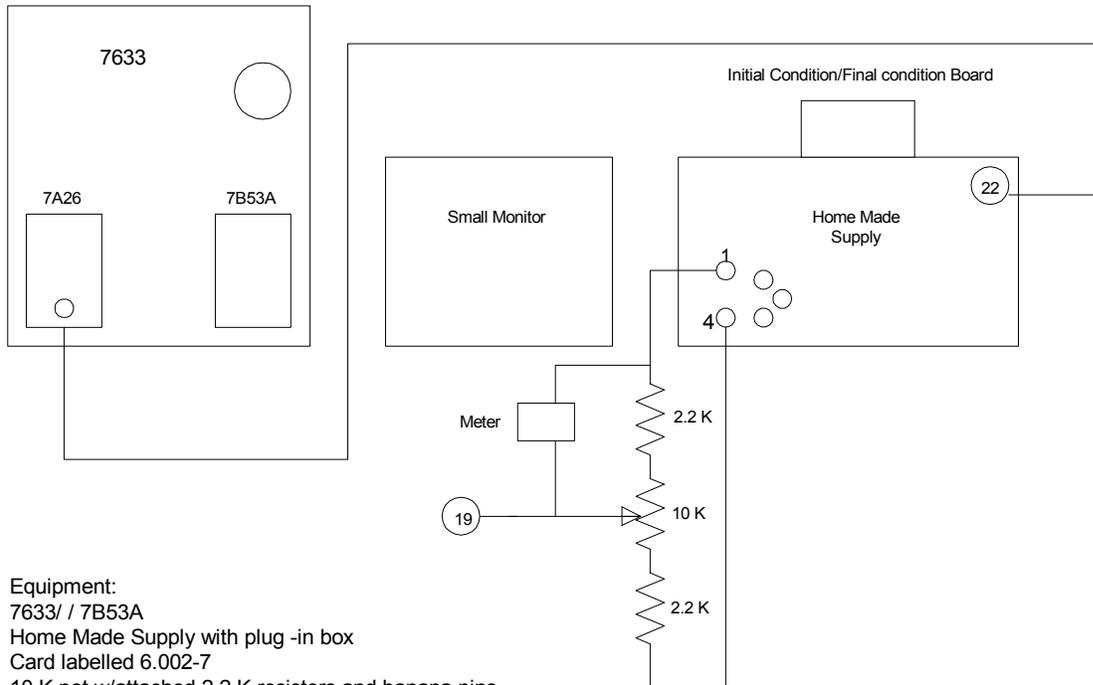- 1) Preset lower pot to 5 v, using scope don't show this ( Calibration )
- 2) Set upper pot to 0 volts with meter, sweep a trace. [ #1 ]
- 3) Short wiper of lower pot to ground @ (19).  
Set upper pot to -10 v with meter , sweep a trace. [#2]  
Set upper pot to +10 v with meter, sweep a trace. [#3]
- 4) Unclip wiper of the lower pot, sweep the trace [#4] total



Equipment:  
 7633/ / 7B53A  
 Home Made Supply with plug -in box  
 Card labelled 6.002-7  
 10 K pot w/attached 2.2 K resistors and banana pins

Scope Settings  
 Vert Mode = Left  
 Store  
 Var persist = In  
 Persistence Knob = Max  
 Storage Level ~ 12:00  
 Trig Source = Vert mode  
 CH2 = .5v/Div ( Actual sens = 5v/Div due tp 10:1 ratio resistor  
 on circuit board amd 1 Meg input resistor of scope.

Main Triggering settings:  
 Mode = Single Sweep, Coupling =AC, Source=Line,  
 Sweep=.5 Sec/Div  
 ( Press Reset Button when a sweep is desired )  
 Make sure Mag in switch is on [IN]