
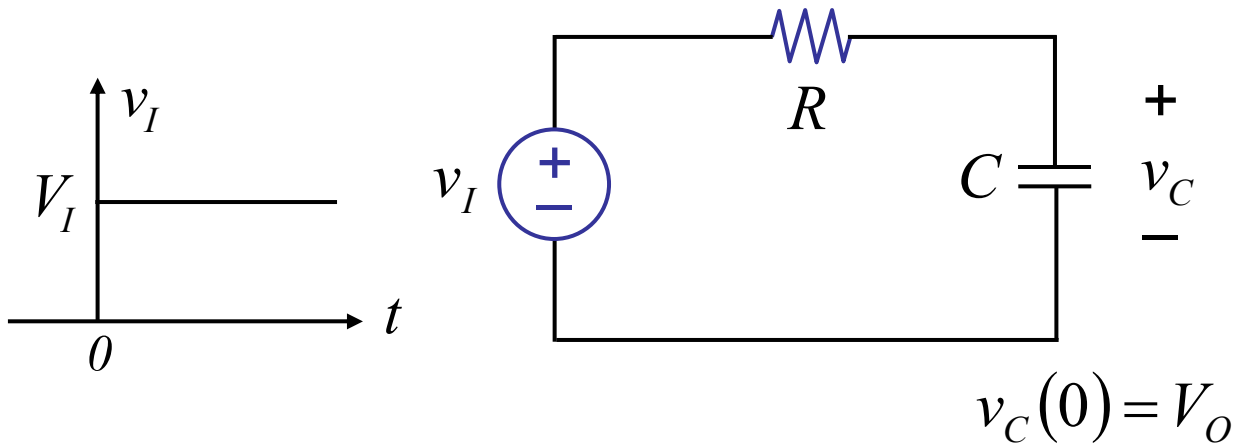


Digital Circuit **Speed**


Review

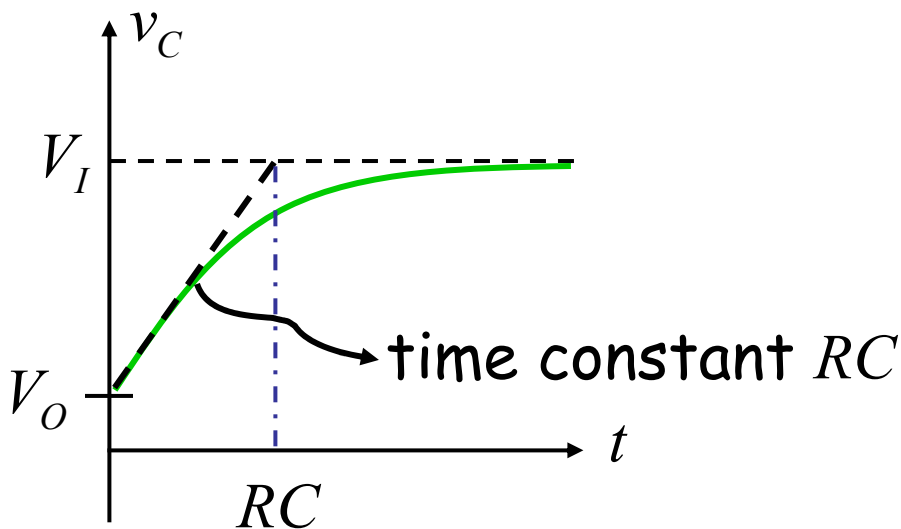


$$v_C = V_I + (V_O - V_I) e^{\frac{-t}{RC}} \quad \text{—————} \quad \textcircled{1}$$




Let's apply the result to an inverter.

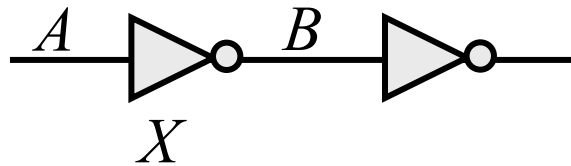


First, rising delay t_r at B

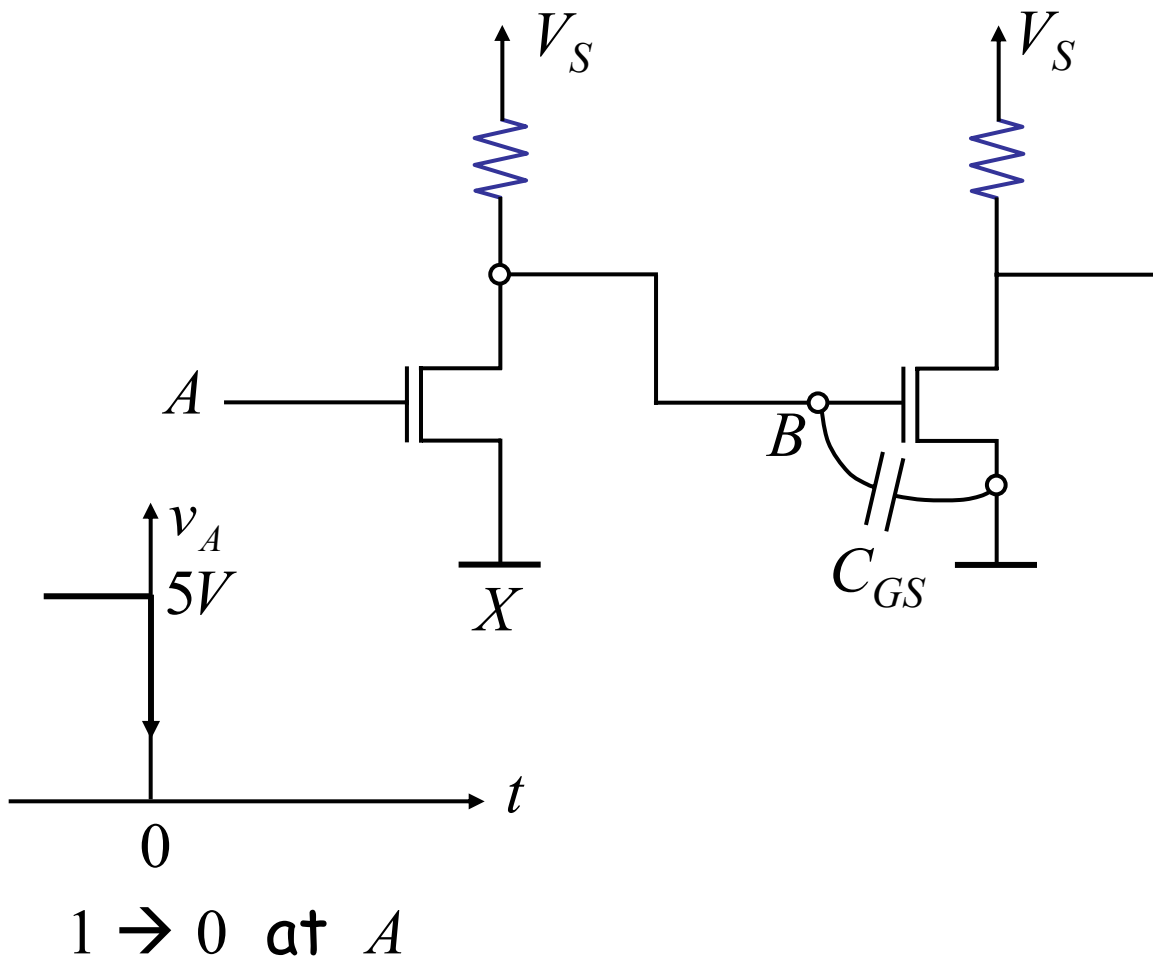


First, rising delay t_r at B

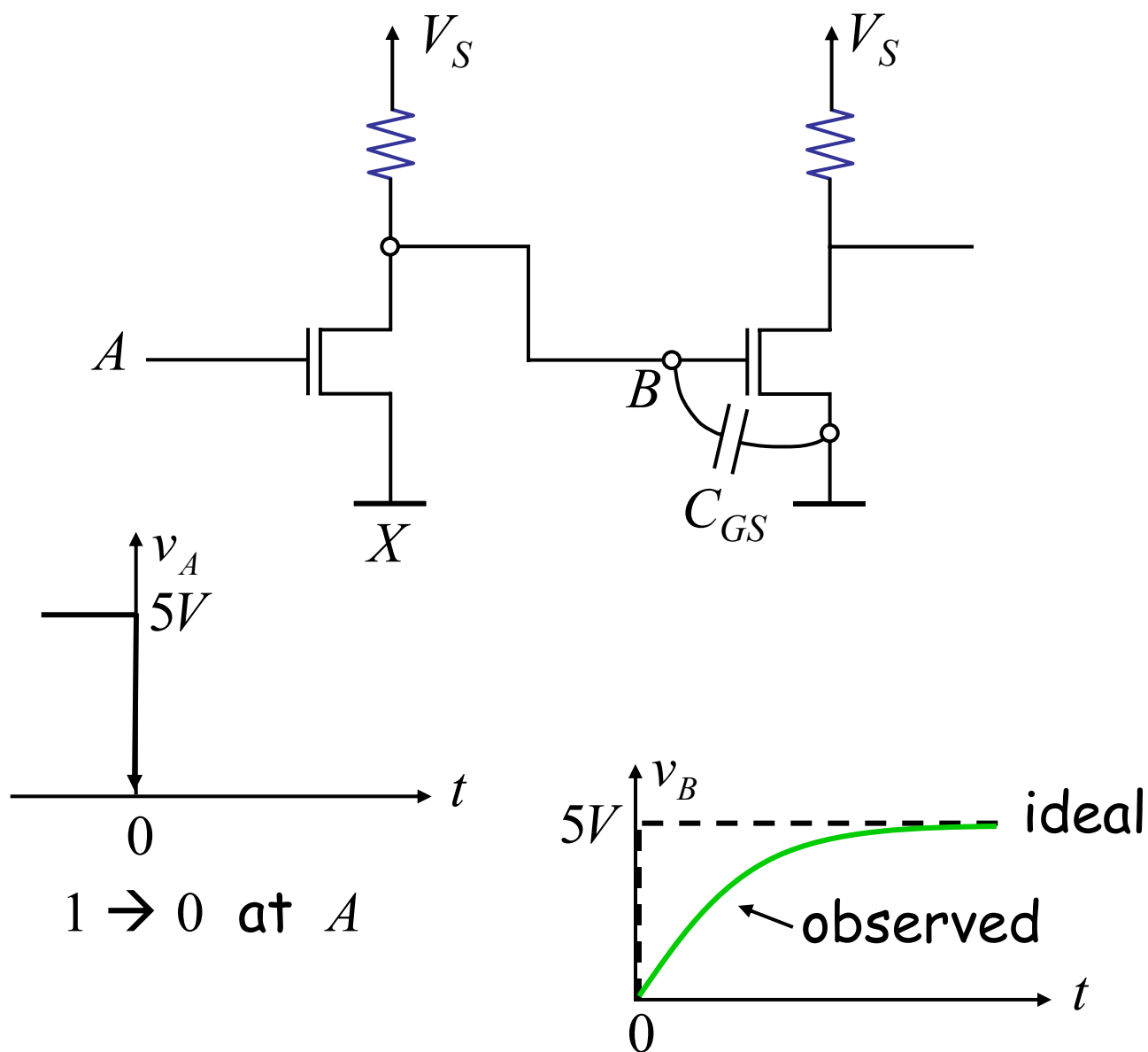

First, rising delay t_r at B

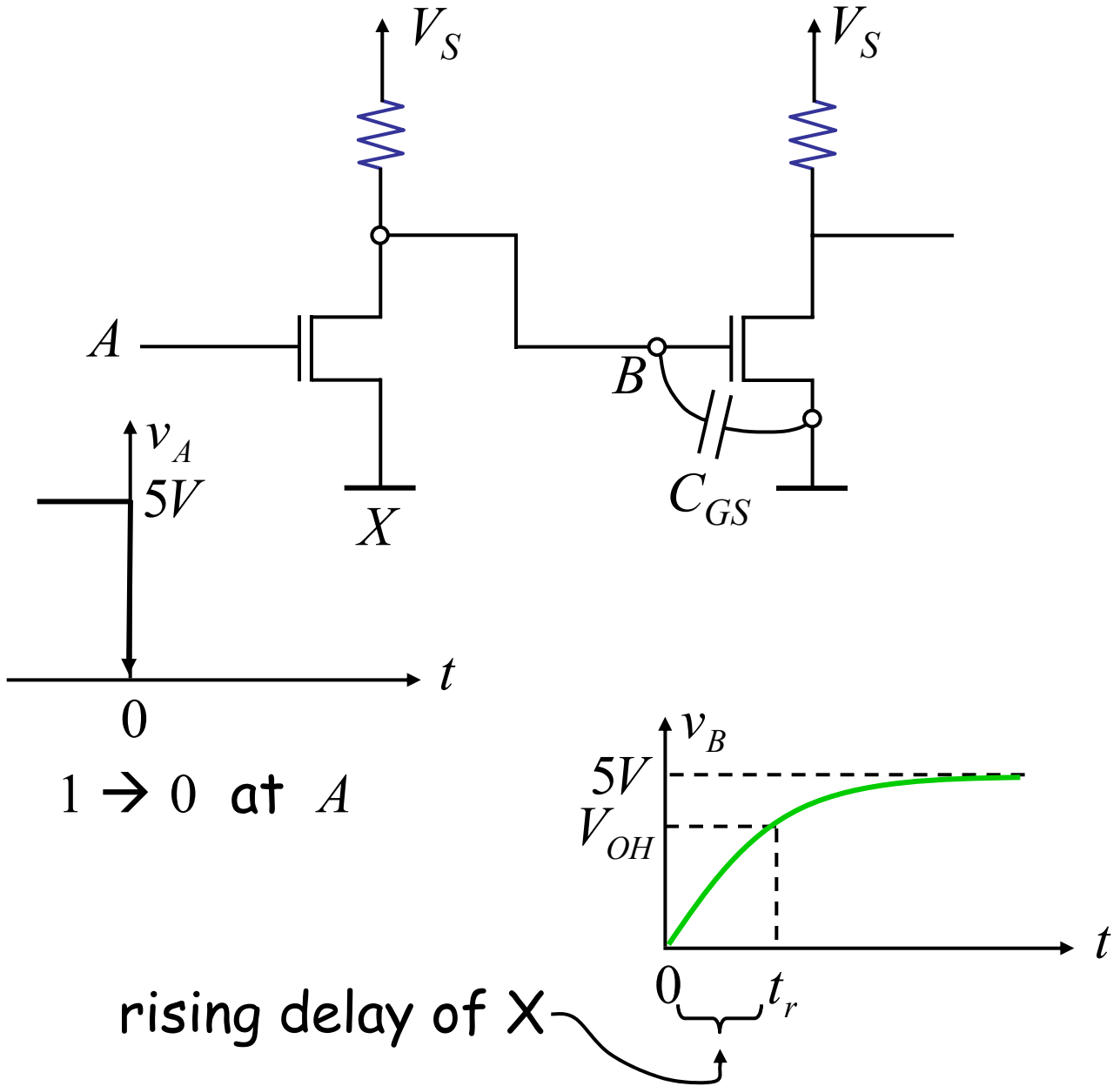

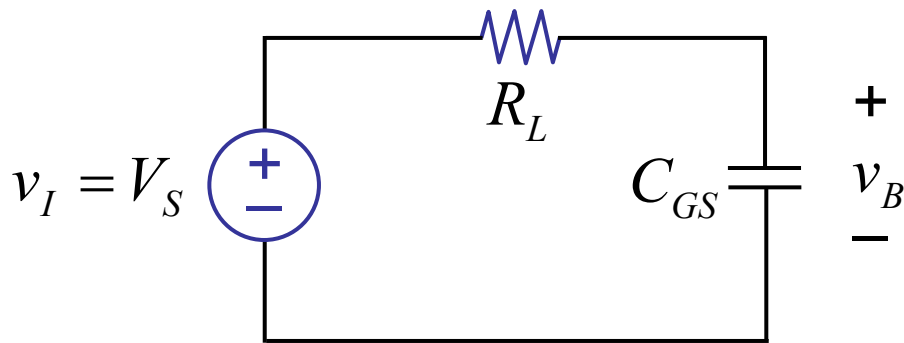Equivalent circuit for $0 \rightarrow 1$ at B



$$\begin{aligned} v_I &= V_S \\ v_B(0) &= 0 \quad \text{for } t \geq 0 \end{aligned}$$

From ①

$$v_B = V_S + (0 - V_S) e^{\frac{-t}{R_L C_{GS}}}$$

Now, we need to find t for which
 $v_B = V_{OH}$.

Or

$$v_{OH} = V_S - V_S e^{\frac{-t}{R_L C_{GS}}}$$

Find t_r :

$$V_S e^{\frac{-t_r}{R_L C_{GS}}} = V_S - V_{OH}$$

$$\frac{-t_r}{R_L C_{GS}} = \ln \frac{V_S - V_{OH}}{V_S}$$

$$t_r = -R_L C_{GS} \ln \frac{V_S - V_{OH}}{V_S}$$

Or

$$v_{OH} = V_S - V_S e^{\frac{-t}{R_L C_{GS}}}$$

Find t_r :

$$V_S e^{\frac{-t_r}{R_L C_{GS}}} = V_S - V_{OH}$$

$$\frac{-t_r}{R_L C_{GS}} = \ln \frac{V_S - V_{OH}}{V_S}$$

$$t_r = -R_L C_{GS} \ln \frac{V_S - V_{OH}}{V_S}$$

e.g.

$$R_L = 1K$$

$$V_S = 5V$$

$$C_{GS} = 0.1 pF$$

$$V_{OH} = 4V$$


$$\begin{aligned} t_r &= -1 \times 10^3 \times 0.1 \times 10^{-12} \ln \frac{5-4}{5} \\ &= 0.16 ns \end{aligned}$$

$$RC = 0.1 ns !$$

Falling Delay t_f


Falling delay t_f is
the t for which v_B falls to V_{OL}

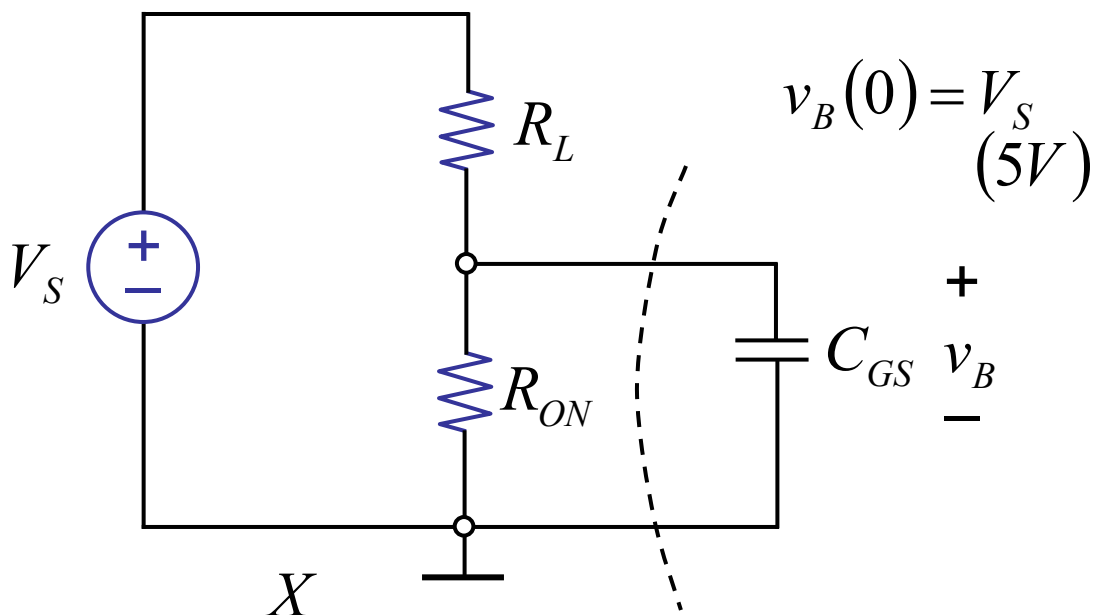Equivalent circuit for $1 \rightarrow 0$ at B




Falling Delay t_f

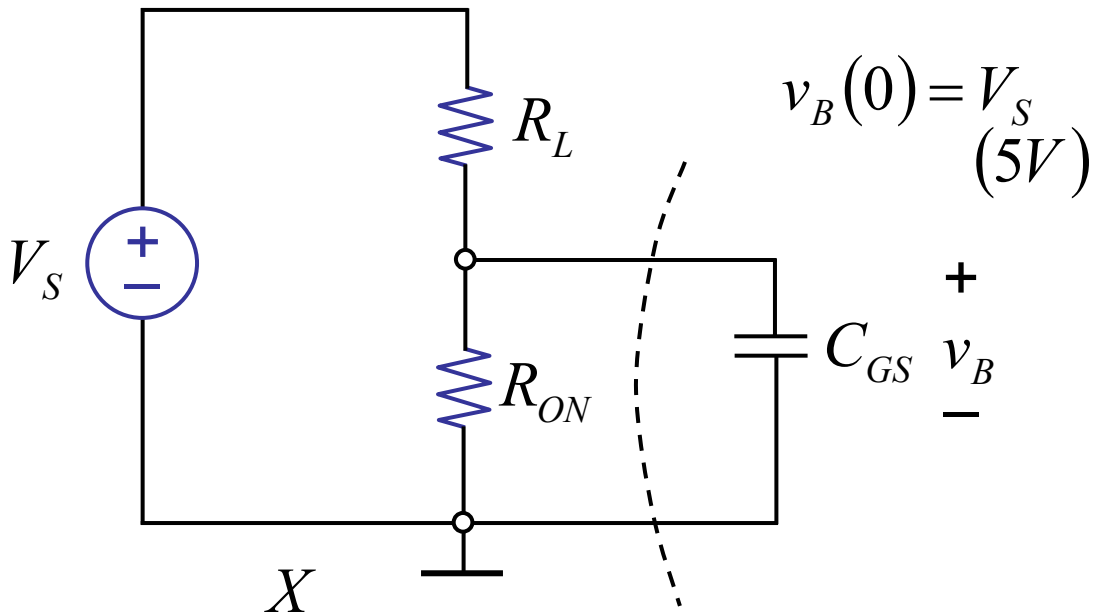Equivalent circuit for $1 \rightarrow 0$ at B



Thévenin replacement ...

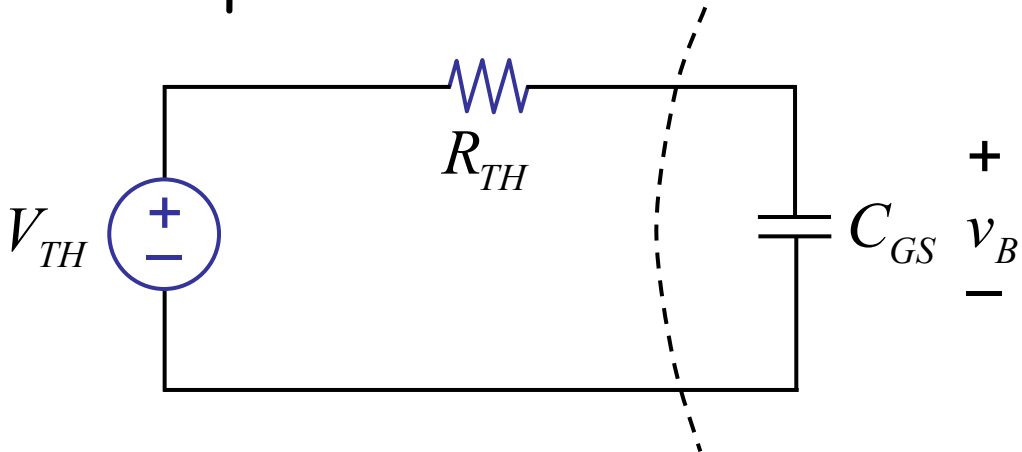

$$R_{TH} = R_L \parallel R_{ON}$$

$$V_{TH} = V_S \frac{R_{ON}}{R_{ON} + R_L}$$

From ①

$$v_B = V_{TH} + (V_S - V_{TH}) e^{\frac{-t}{R_{TH}C_{GS}}}$$

Falling decay t_f is
the t for which v_B falls to V_{OL}

$$V_{OL} = V_{TH} + (V_S - V_{TH}) e^{\frac{-t_f}{R_{TH}C_{GS}}}$$

or

$$t_f = -R_{TH}C_{GS} \ln \frac{V_{OL} - V_{TH}}{V_S - V_{TH}}$$

$$t_f = -R_{TH} C_{GS} \ln \frac{V_{OL} - V_{TH}}{V_S - V_{TH}}$$

e.g. $R_L = 1K$ $V_S = 5V$ $R_{ON} = 10\Omega$

$C_{GS} = 0.1 pF$ $V_{OL} = 1V$


$R_{TH} \approx 10\Omega$, $V_{TH} \approx 0V$

$$t_f = -10 \cdot 0.1 \cdot 10^{-12} \ln \frac{1}{5}$$

$$= 1.6 ps$$

$$RC = 1 ps !$$

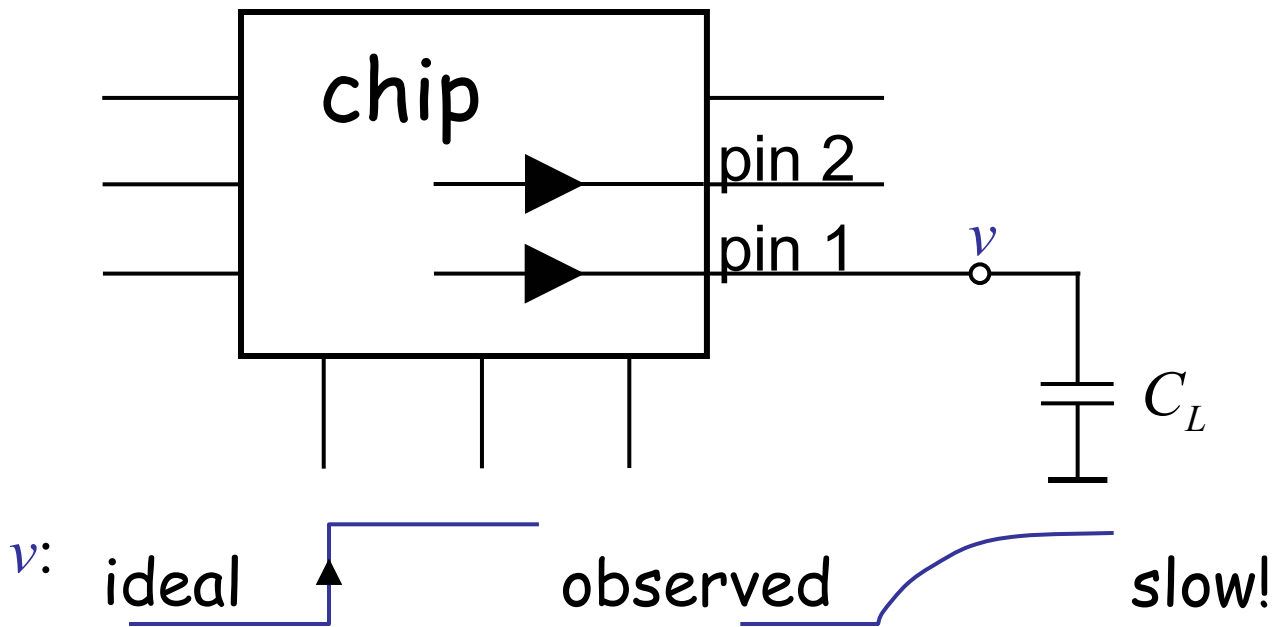
For recitation: Slow may be better Problem




So the engineers decided to speed it up...



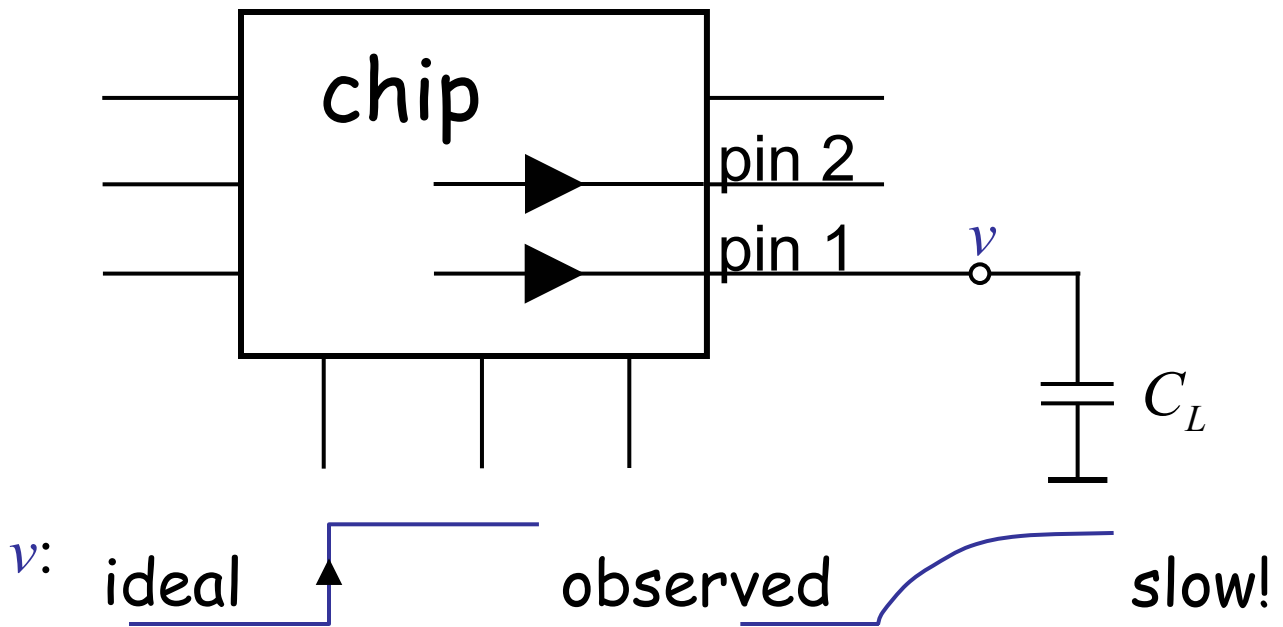For recitation: Slow may be better Problem





... but, disaster!

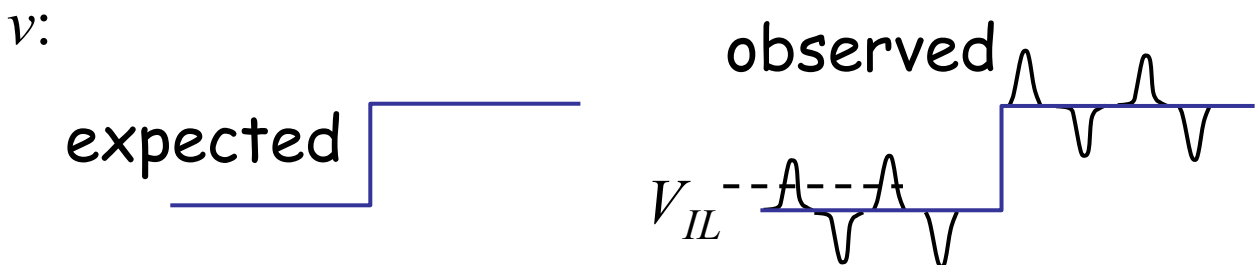

Why? Consider ...


Case ①

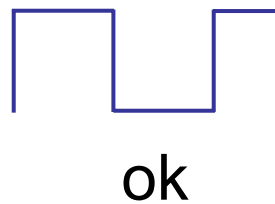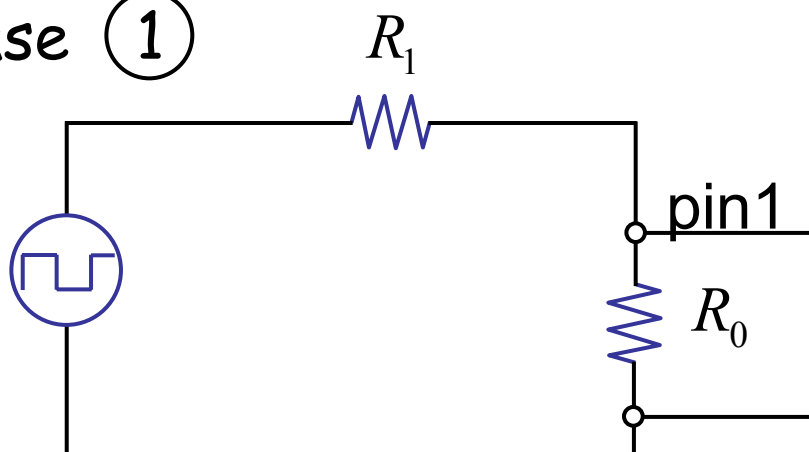


Why? Consider ...



Case (2)

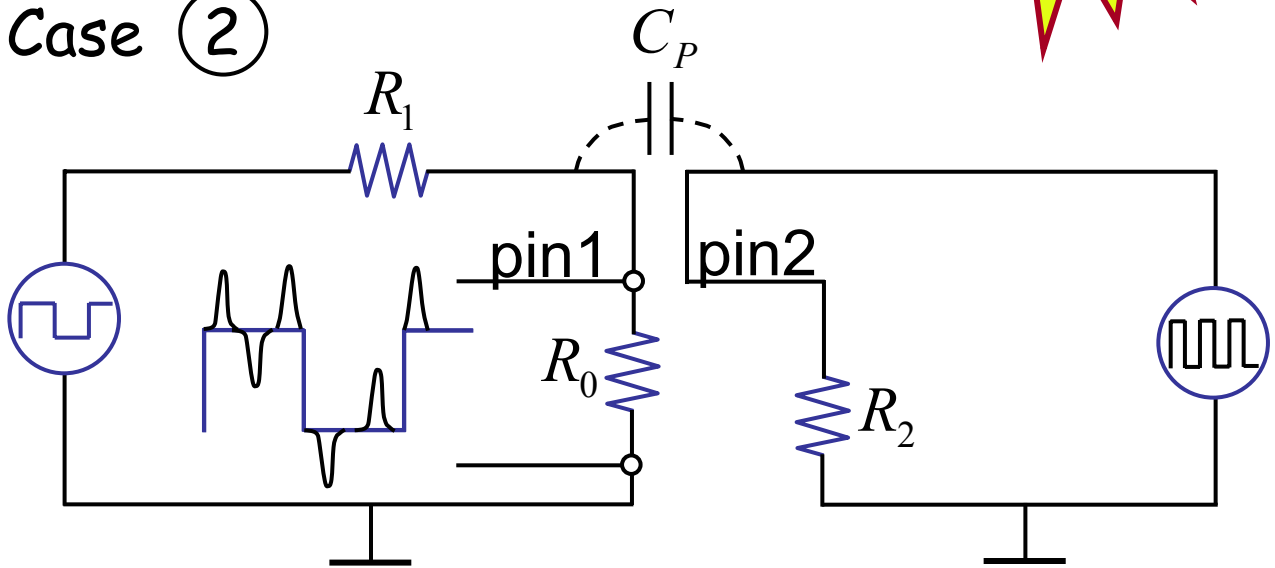


crosstalk!

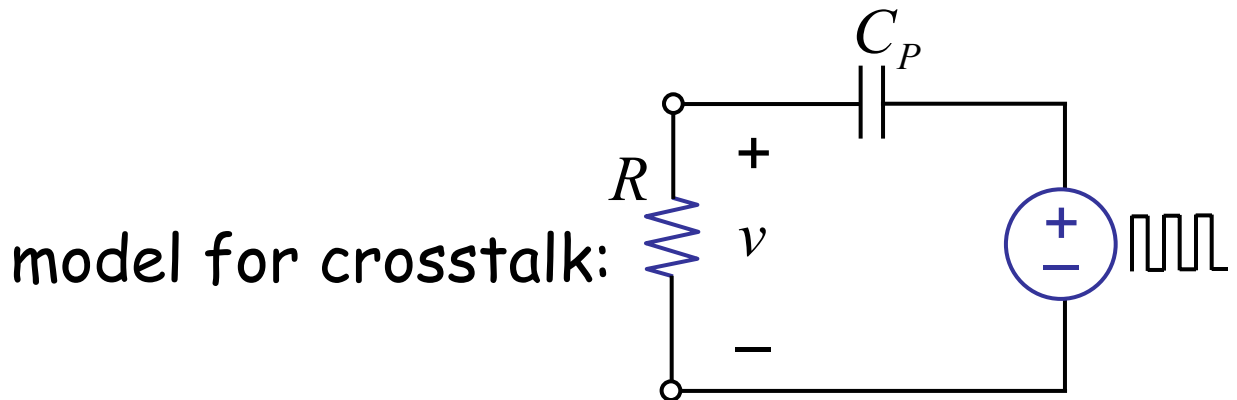

Case ③

... 6.002 expert saw the solution

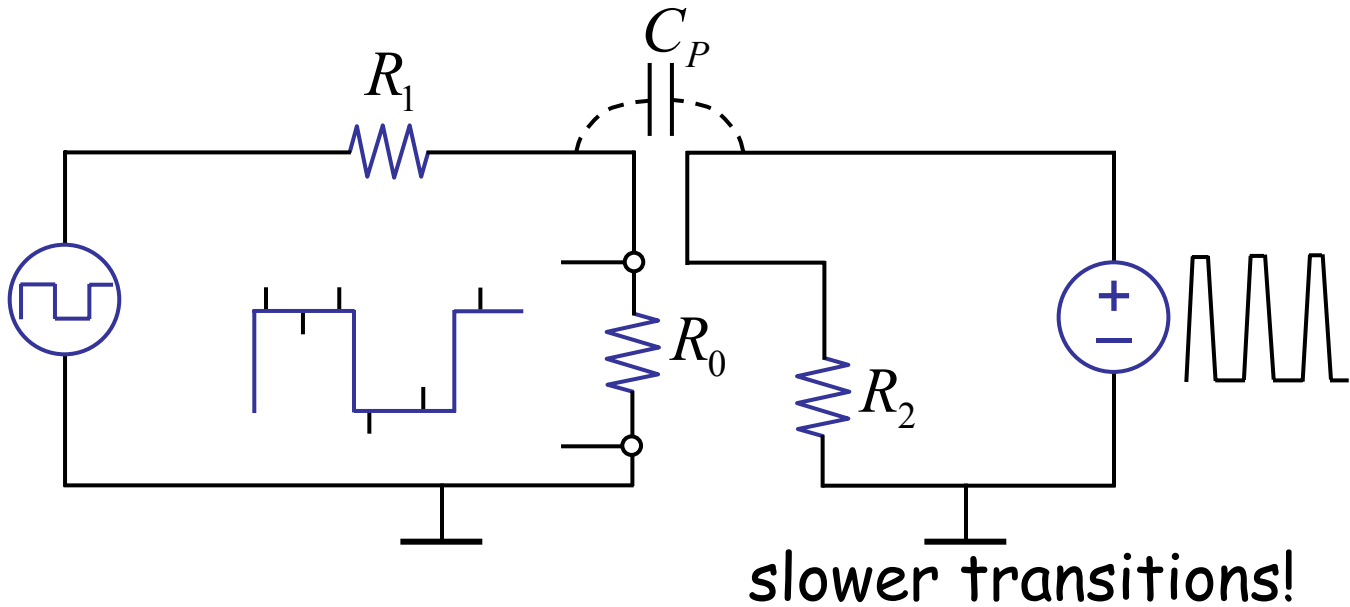

Detailed analysis in recitation.