


6.002

**CIRCUITS AND
ELECTRONICS**


The Operational Amplifier Abstraction

Review


- MOSFET amplifier – 3 ports

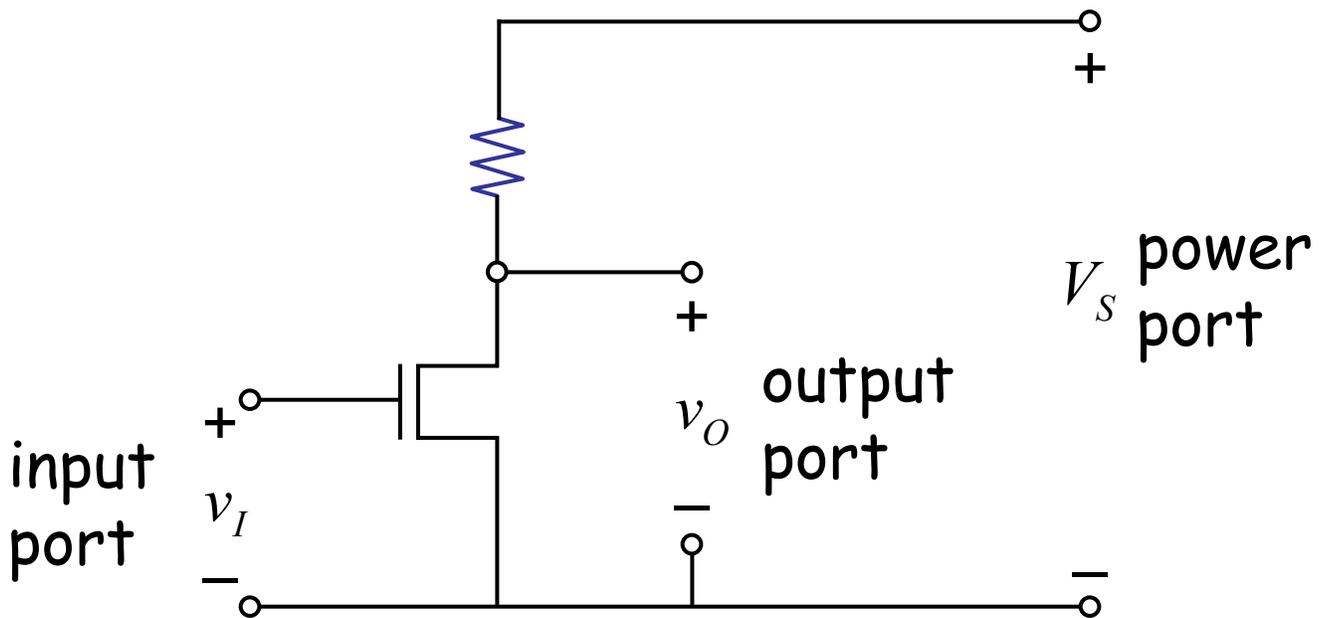

- Amplifier abstraction

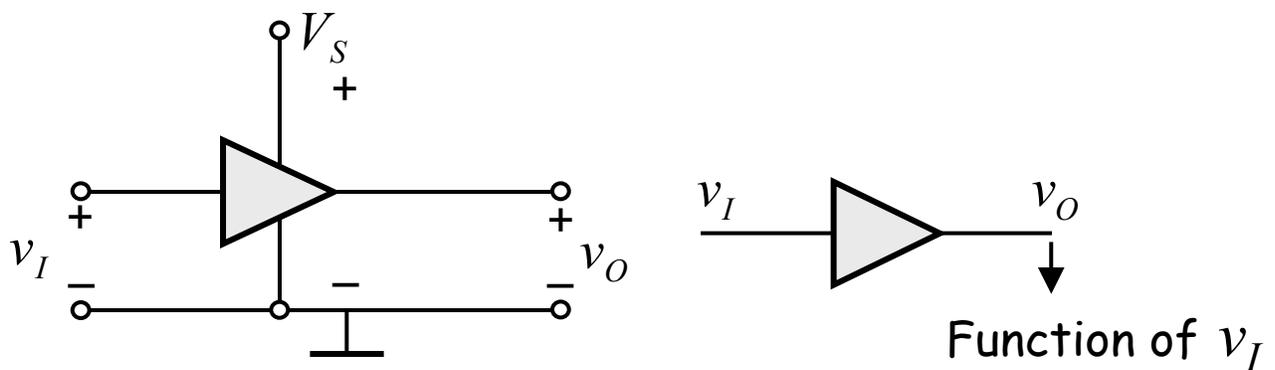


Review

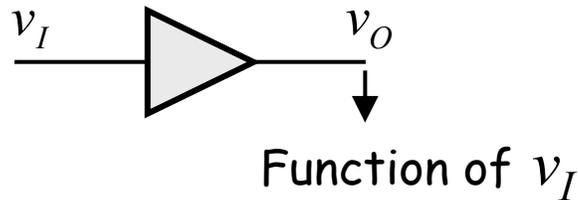


- Can use as an abstract building block for more complex circuits (of course, need to be careful about input and output).
- **Today**
Introduce a more powerful amplifier abstraction and use it to build more complex circuits.

Reading: Chapter 15 from A & L.


Operational Amplifier Op Amp

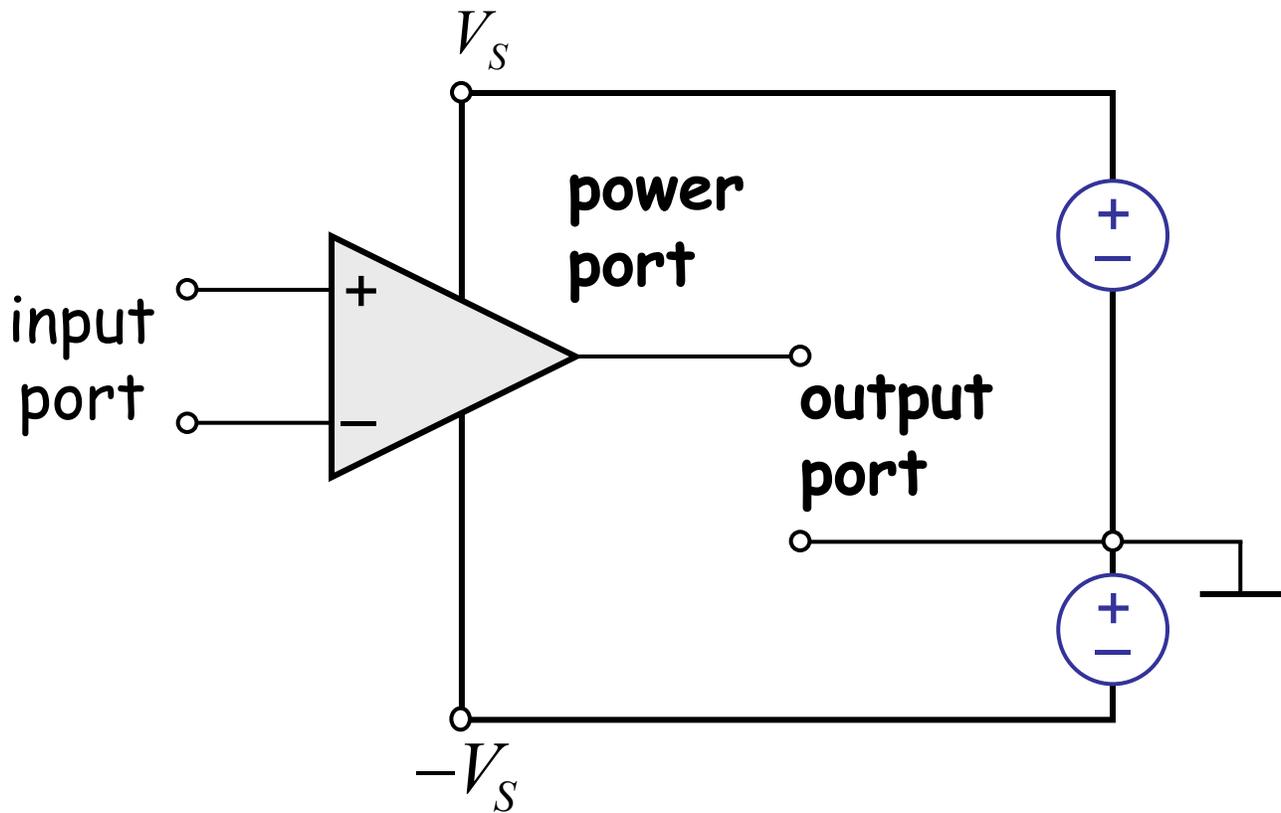

More abstract representation:


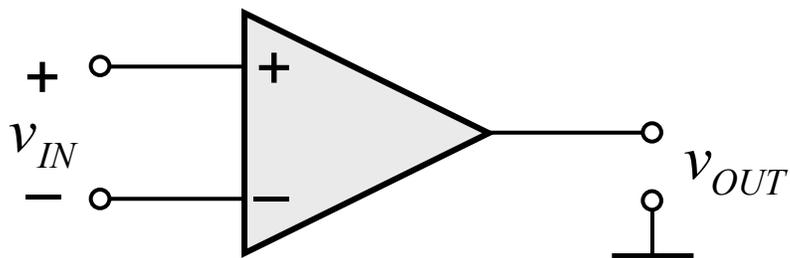


Circuit model (ideal):

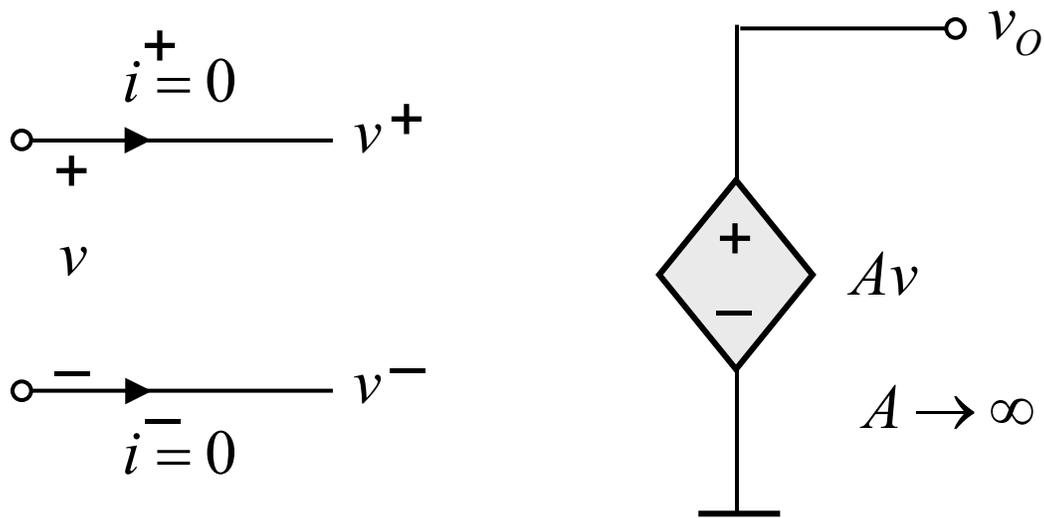

- i.e.
- ◆ ∞ input resistance
 - ◆ 0 output resistance
 - ◆ "A" virtually ∞
 - ◆ No saturation


Using it...

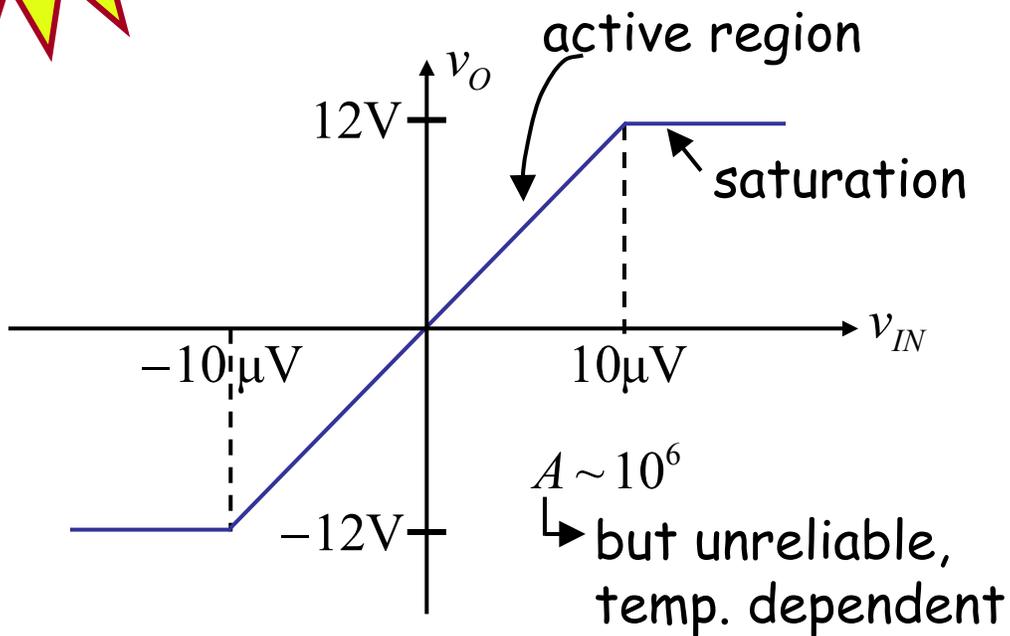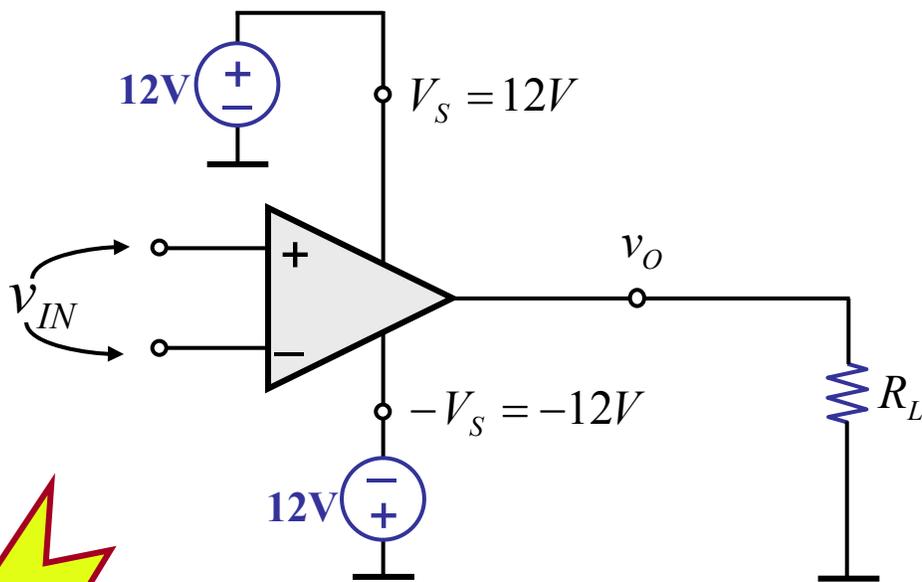


(Note: possible confusion with MOSFET saturation!)

Let us build a circuit...

Circuit: noninverting amplifier

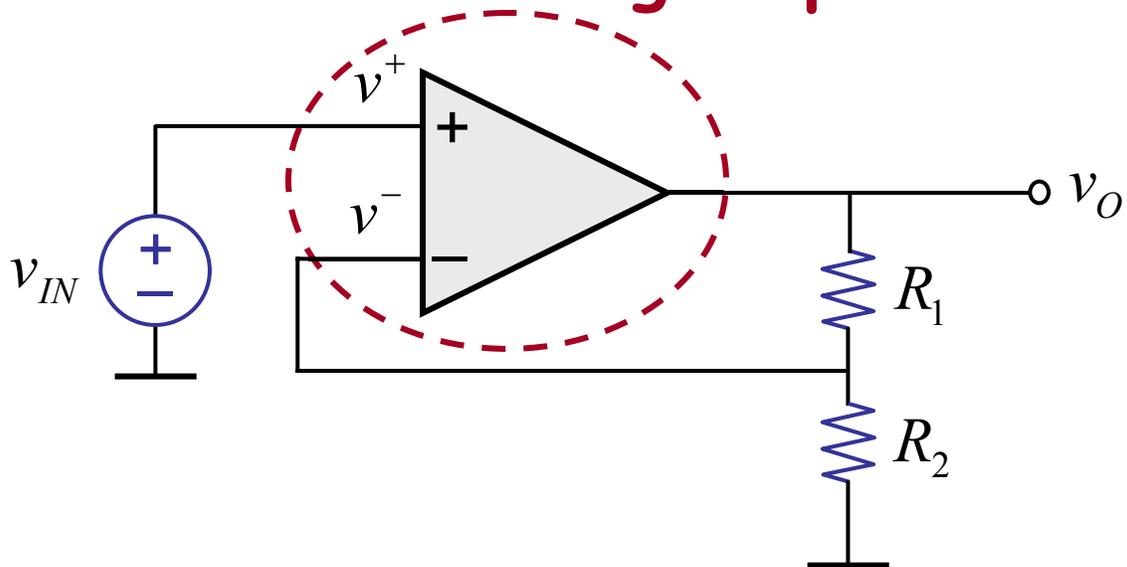

Equivalent circuit model

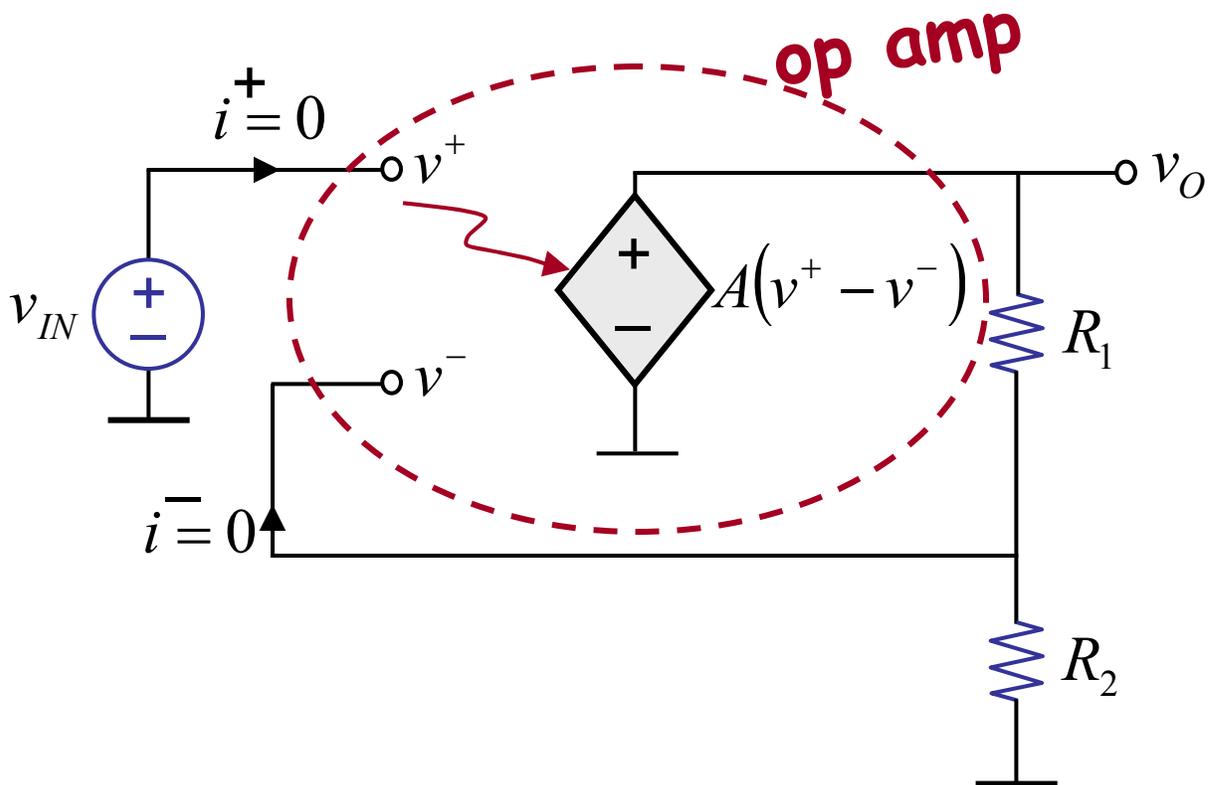

Let us analyze the circuit:

Find v_o in terms of v_{IN} , etc.

$$v_o = A(v^+ - v^-)$$

$$= A\left(v_{IN} - v_o \frac{R_2}{R_1 + R_2}\right)$$

$$v_o \left(1 + \frac{AR_2}{R_1 + R_2}\right) = Av_{IN}$$

$$v_o = \frac{Av_{IN}}{1 + \frac{AR_2}{R_1 + R_2}}$$

What happens when "A" is very large?

Let's see... When A is large

$$v_O = \frac{Av_{IN}}{1 + \frac{AR_2}{R_1 + R_2}} \approx \frac{Av_{IN}}{\frac{AR_2}{R_1 + R_2}}$$
$$\approx v_{IN} \underbrace{\frac{(R_1 + R_2)}{R_2}}_{\text{gain}}$$

Suppose

$$A = 10^6$$
$$R_1 = 9R$$
$$R_2 = R$$

$$v_O = \frac{10^6 \cdot v_{IN}}{1 + \frac{10^6 R}{9R + R}}$$
$$= \frac{10^6 \cdot v_{IN}}{1 + 10^6 \cdot \frac{1}{10}}$$

$$v_O \approx v_{IN} \cdot 10$$




Gain:

- determined by resistor ratio
- insensitive to A , temperature, fab variations

Why did this happen?

Insight:

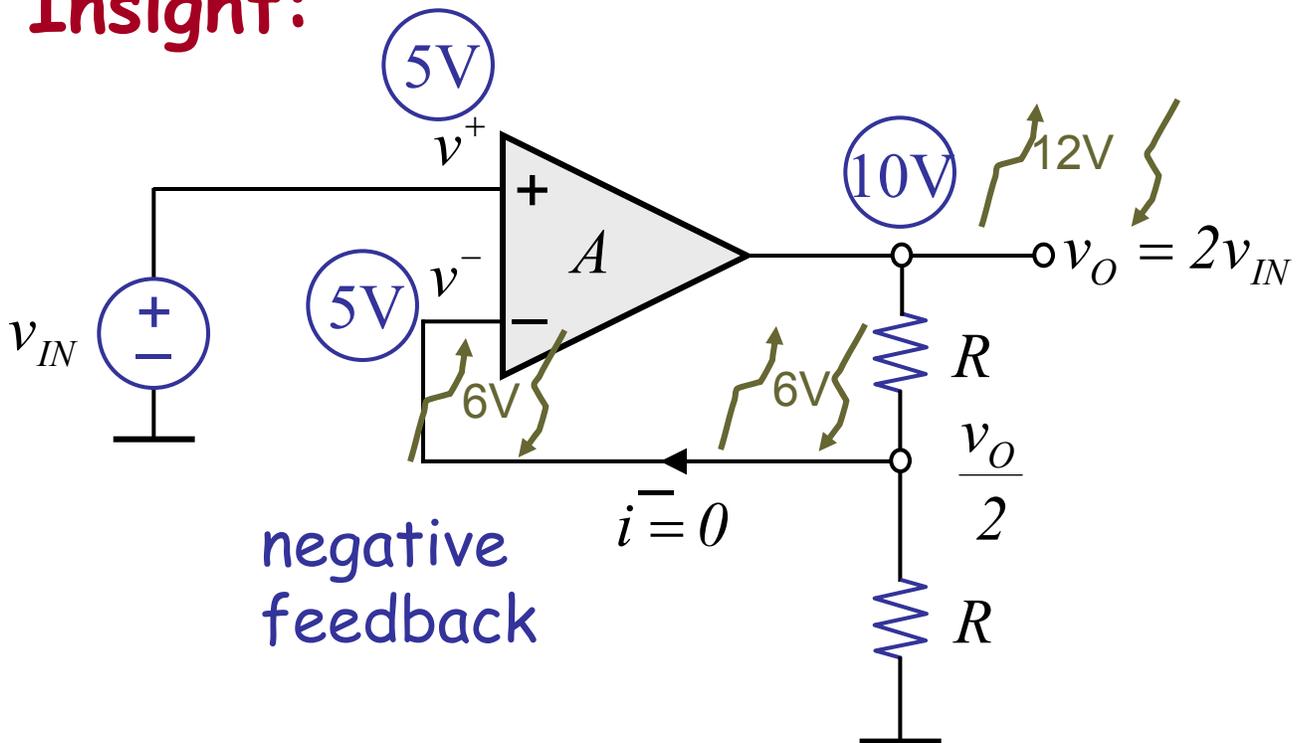

e.g. $v_{IN} = 5V$

Suppose I perturb the circuit...

(e.g., force v_O momentarily to 12V somehow).


Stable point is when $v^+ \approx v^-$.

Key: negative feedback \rightarrow portion of output fed to $-ve$ input.

e.g. Car antilock brakes
 \rightarrow small corrections.

Question: How to control a high-strung device?

Antilock brakes

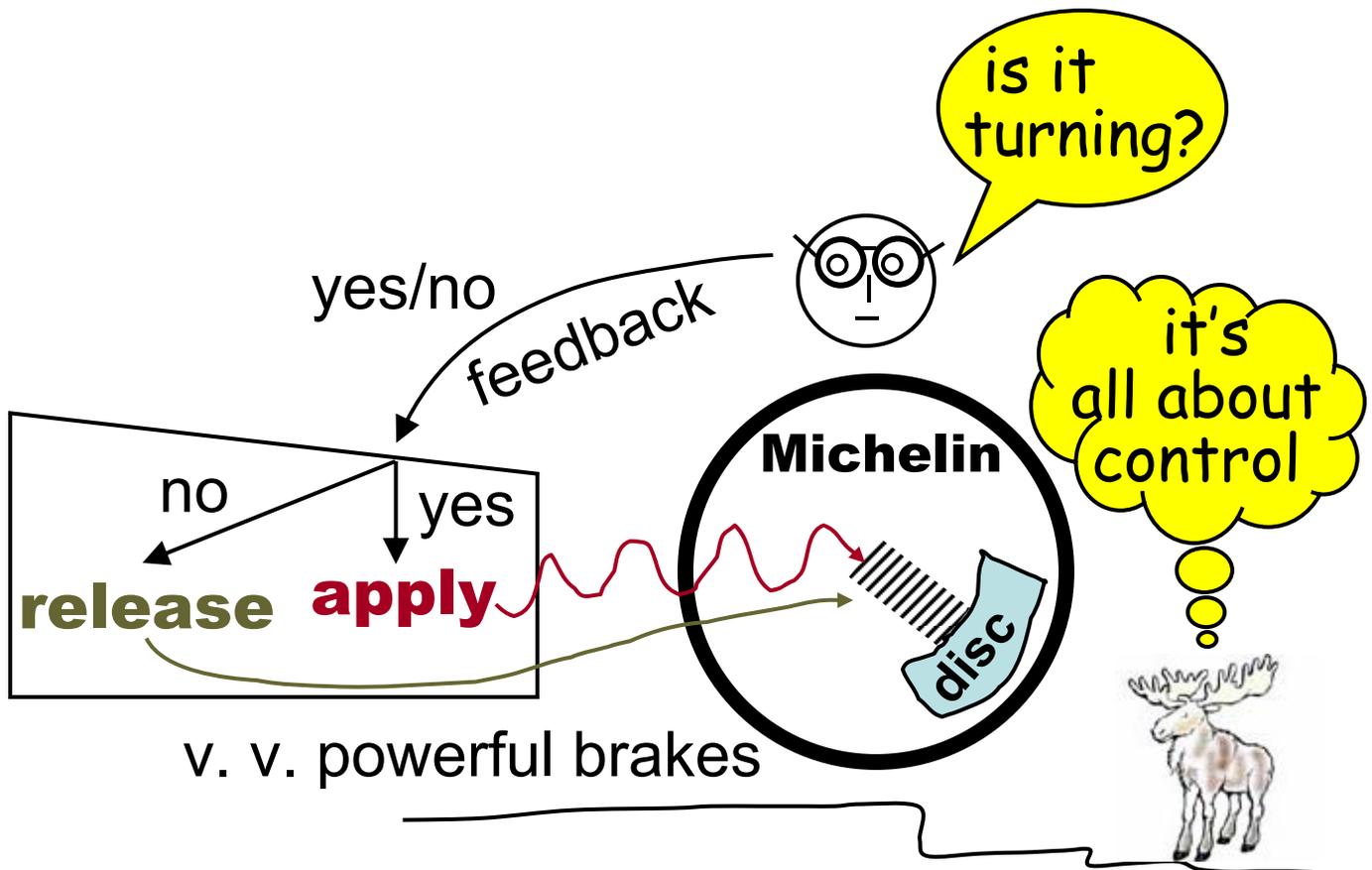

More op amp insights:

Observe, under negative feedback,

$$v^+ - v^- = \frac{v_O}{A} = \frac{\left(\frac{R_1 + R_2}{R_1}\right)v_{IN}}{A} \rightarrow 0$$

$$v^+ \approx v^-$$

We also know

$$i^+ \approx 0$$

$$i^- \approx 0$$


→ yields an easier analysis method
(under negative feedback).

Insightful analysis method under negative feedback


$$v^+ \approx v^-$$

$$i^+ \approx 0$$

$$i^- \approx 0$$

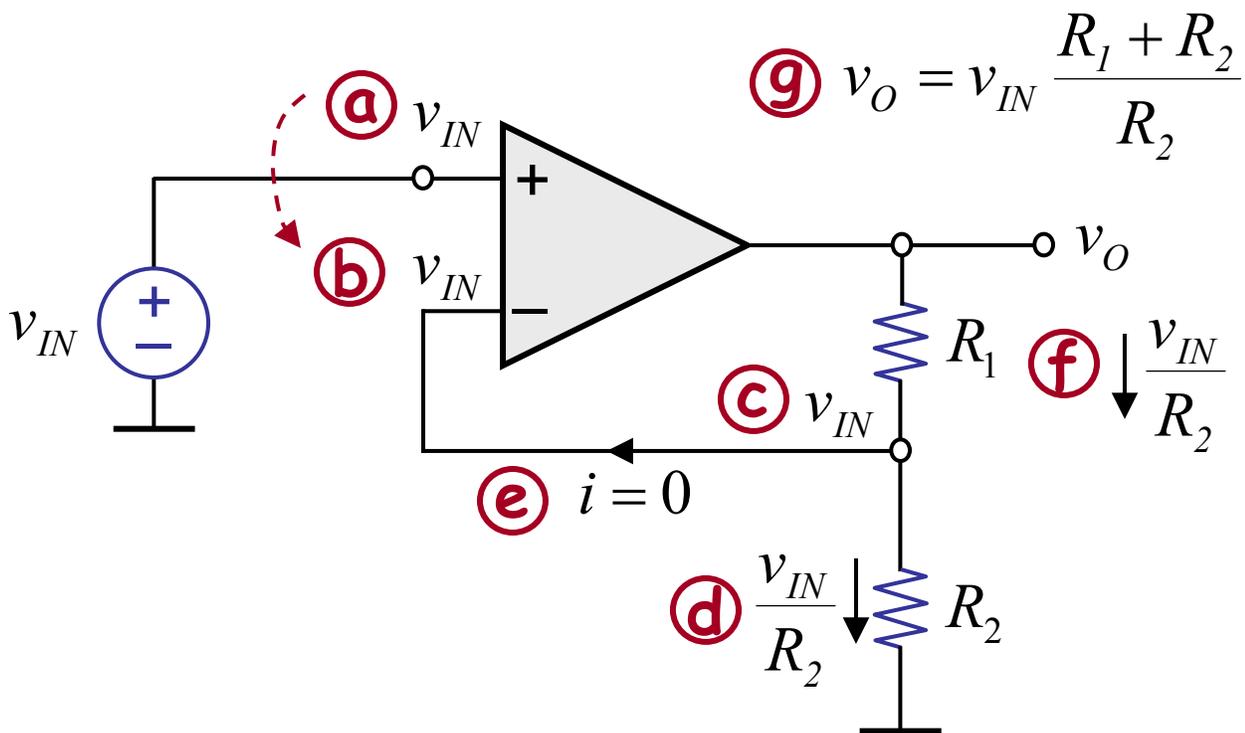

Question:

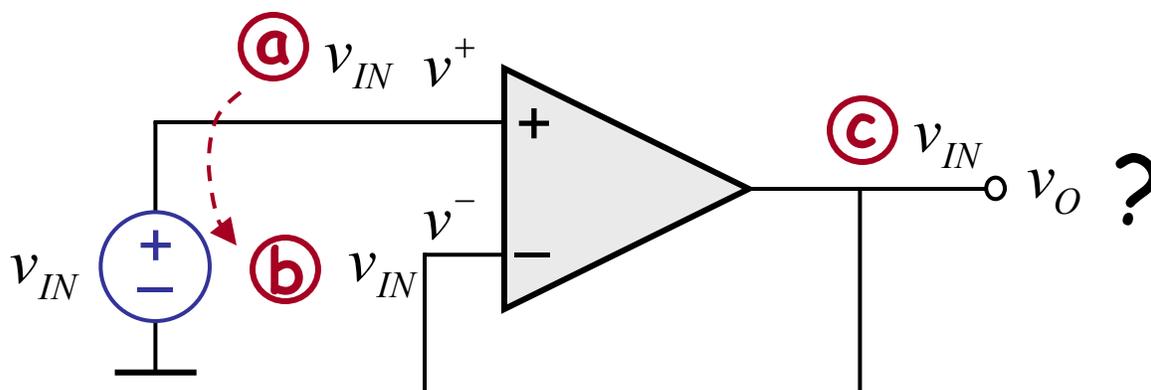


$$v_O \approx v_{IN}$$

or
$$v_O = v_{IN} \frac{R_1 + R_2}{R_2}$$

with $R_1 = 0$

$$R_2 = \infty$$

Why is this circuit useful?

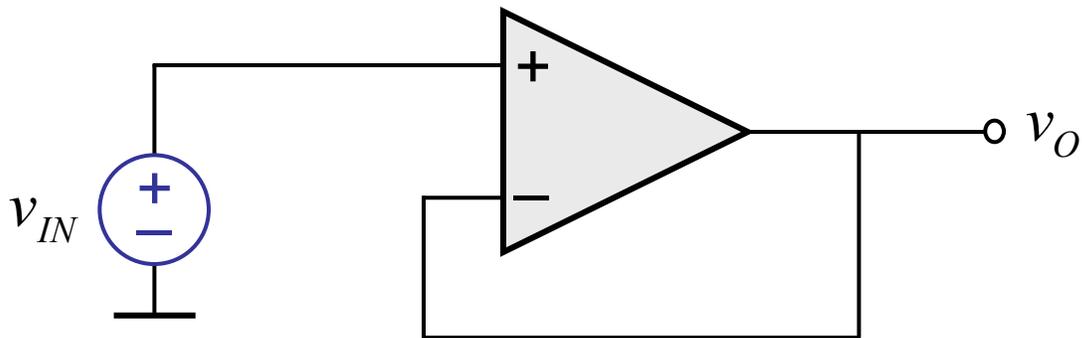

$$v_O \approx v_{IN}$$

Buffer

- voltage gain = 1
- input impedance = ∞
- output impedance = 0
- current gain = ∞
- power gain = ∞