



Care and
Feeding of
Power Grid
Tubes

CARE AND FEEDING OF POWER GRID TUBES

Copy right © 1967 by Varian. All right reserved. Printed in the United States of America. This book, or parts thereof may not be reproduced in any form without permission of the publisher.

LIBRARY OF CONGRESS NO. 67-30070

Table of Contents

SECTION I **1**

INTRODUCTION **1**

SECTION 2 **3**

WHAT IS A POWER GRID TUBE? **3**

2.1 TRIODES 3

2.2 TETRODE 8

2.3 PENTODES 13

2.4 INDUCTIVE OUTPUT TUBE (IOT) 14

**2.5 MULTISTAGE DEPRESSED COLLECTOR IOT
(MSDC IOT)** 21

2.6 CATHODE EMITTERS 23

SECTION 3 **31**

ELECTRICAL DESIGN CONSIDERATIONS **31**

3.1 CLASS OF OPERATION 31

**3.2 TUBE PERFORMANCE COMPUTER FOR R-F
AMPLIFIERS** 33

3.3 TYPICAL R-F AMPLIFIER CIRCUIT DESIGNS
47

- 3.4 COMPONENT PARTS 53**
- 3.6 FILAMENT BY-PASSING 56**
- 3.7 SCREEN AND SUPPRESSOR GRID BY-PASSING AND SCREEN TUNING 58**
- 3.8 GROUNDED-GRID CIRCUITS 59**
- 3.9 PROTECTION 61**
- 3.10 KEYING 63**
- 3.11 AMPLITUDE MODULATION 65**
- 3.12 POWER SUPPLY CONSIDERATION 67**
- 3.13 STABILIZING THE AMPLIFIER 69**

SECTION 4 74

LINEAR AMPLIFIER AND SINGLE SIDEBAND SERVICE 74

- 4.1 WHY SINGLE SIDEBAND 74**
- 4.2 RATING TUBES FOR LINEAR AMPLIFIER SERVICE 75**
- 4.3 SELECTION OF TUBES FOR SINGLE SIDEBAND SERVICE 83**
- 4.4 LINEAR AMPLIFIER DESIGN 91**
- 4.5 ADJUSTING AND MONITORING THE LINEAR AMPLIFIER 95**

SECTION 5

98

NEUTRALIZATION

98

- 5.1 NEUTRALIZATION BELOW VHF 98**
- 5.2 PUSH-PULL NEUTRALIZATION 100**
- 5.3 SINGLE-ENDED NEUTRALIZATION 100**
- 5.4 NEUTRALIZING GROUNDED-GRID AMPLIFIERS
102**
- 5.5 NEUTRALIZATION PROCEDURE 106**
- 5.6 SELF-NEUTRALIZING FREQUENCIES OF
TETRODES AND PENTODES 109**

SECTION 6

114

VARIOUS APPLICATIONS

114

- 6.1 ADJUSTMENT OF LOADING AND EXCITATION
114**
- 6.2 OPERATING VOLTAGES AND CURRENTS 115**
- 6.3 EFFECT OF DIFFERENT SCREEN VOLTAGES
116**
- 6.4 THE THREE HALVES POWER LAW 116**
- 6.5 BALANCE OF AMPLIFIERS 118**
- 6.6 HARMONIC AMPLIFIER AND CONTROL OF
HARMONICS 119**
- 6.7 SHIELDING 121**
- 6.8 DRIVE POWER REQUIREMENTS 123**

**6.9 VHF AND UHF OPERATING CONDITIONS FOR
SATISFACTORY PLATE EFFICIENCY AND
MINIMUM DRIVE 125**

6.10 COOLING TECHNIQUES 127

6.11 TUBE LIFE 159

BIBLIOGRAPHY

164

Illustrations

Figure 1:	Constant current curves for 3CX3000A1 ($\mu = 5$).	5
Figure 2:	Constant current curves for 3CX3000A7 ($\mu = 160$).	5
Figure 3:	Constant current curves for a zero-bias triode with a μ of 200.	6
Figure 4:	Internal configuration of a planar triode.	7
Figure 5:	Incorrect screen circuit for tube requiring low impedance screen supply.	10
Figure 6:	A correct screen circuit for tube requiring low impedance screen supply.	11
Figure 7:	Another approach to swamping the screen circuit.	11
Figure 8:	Typical curve of grid current as a function of control grid voltage for a high power thoriated tungsten filament tetrode.	12
Figure 9:	Secondary-emission characteristics of the metals under ordinary conditions. The curve shows the ratio of the number of secondary to primary electrons for various primary-electron impact velocities expressed in volts. (After Harries.)	13
Figure 10:	Eimac K2 IOT Amplifier	17
Figure 11:	Eimac K2 Inductive Output Tube	18
Figure 12:	Typical tuning curves for UHF TV IOT. The lower curve is the reflected drive signal. The upper curve shows the output tuning.	20
Figure 13:	Equipotential Lines in a three stage collector. The potentials are determined by collector geometry and collector voltages.	22
Figure 14:	Electron trajectories at near to ideal power. The tube gap is at the left side of the image, which is only half the collector. The right collector element is at cathode to anode potential. The middle section is approximately half the cathode	22
Figure 15:	Electron trajectories at higher than ideal power. Less power is recovered in the middle, depressed collector segment.	23
Figure 16:	Typical MSDC IOT power supply schematic	23
Figure 17:	Pulse derating curve.	24
Figure 18:	Typical oxide cathode.	25
Figure 18:	Typical spiral tungsten filament.	26
Figure 19:	Typical bar tungsten filament.	27
Figure 20:	Typical mesh tungsten filament.	28
Figure 21:	Typical Focus Cathode (LPT-62). The horizontal assembly is the cathode assembly. The white area between the shiny bars is the actual cathode emitting areas. The shiny bars are essentially shadow grids. This cathode assembly is mounted insid	29
Figure 22:	Tungsten Matrix (Dispenser) Cathode from a K2 series Inductive Output Tube.	30
Figure 23:	Anode efficiency vs. conduction angle for an amplifier with tuned load. (From Thomas L. Martin, Jr., "Electronic Circuits," p. 452, Prentice-Hall, Inc., Englewood Cliffs, N.J., 1955).	32
Figure 24:	Variation of anode and grid voltage	34
Figure 25:	Anode voltage and grid voltage scales.	35
Figure 26:	Instantaneous values of anode and grid current.	35
Figure 27:	Constant current characteristics for 4CX20,000A/8990 tetrode.	36

Figure 28.	Constant current characteristics for 4CW100,000D tetrode.	45
Figure 29.	A typical circuit for an R-F amplifier.	48
Figure 30.	Relative harmonic vs. resonant circuit Q.	49
Figure 31:	Determination of input capacitor C1.	49
Figure 32:	Determination of loading Capacitor C2.	50
Figure 33A.	Determination of Inductor L.	51
Figure 33B.	Reactance of an r-f choke vs. frequency.	52
Figure 34.	A typical circuit using "zero-bias" triodes showing metering circuits and method of grounding the grid to r-f. The grid current is measured in the return lead from ground to filament.	59
Figure 35.	A typical circuit using "Zero-bias" triodes showing metering circuits. The grid is grounded to r-f with a by-pass capacitor. The grid is raised 1Ω above d-c ground to allow the grid current to be measured.	60
Figure 36.	3CX5000A7 with grid flange.	60
Figure 37.	Tetrode and pentode protection chart. This chart indicates the location of a suitable relay which should act to remove the principal supply voltage from the stage or transmitter to prevent damage to the tubes.	62
Figure 38.	Triode protection chart. This chart indicates the location of a suitable relay which should act to remove the principal supply voltage from the stage or transmitter to prevent damage to the tube or transmitter.	63
Figure 39A.	Screen voltage control circuit for exciter keying or protection against loss of excitation when supplying screen from high voltage source.	64
Figure 39B.	A typical method of keying a tetrode or pentode amplifier.	65
Figure 40.	Basic screen and anode modulation circuits.	65
Figure 41.	Usual circuit supporting VHF parasitic oscillation in HF r-f amplifiers.	71
Figure 42:	Placement of parasitic suppressors to eliminate VHF parasitic oscillations in HF r-f amplifiers.	72
Figure 43.	Relative spectrum space occupied by AM signal and SSB signal modulated by frequencies of 200 to 3000 Hz.	75
Figure 44.	R-F output of SSB transmitter with single-tone modulation. (a) Oscilloscope pattern (b) Spectrum for 1000-Hz tone.	76
Figure 45.	Spectrum of SSB transmitter modulated by two-tone test signal containing 400- and 2500-Hz tones and transmitting upper sideband.	77
Figure 46.	Spectrum of SSB transmitter modulated by 1500-Hz tone and injecting carrier to obtain second r-f signal equal in amplitude to tone.	77
Figure 47.	R-f output of SSB transmitter modulated by two-tone test signal as seen on the oscilloscope.	78
Figure 48.	Single-tone condition.	80
Figure 49.	Two-tone condition.	82
Figure 50.	Three-tone condition.	82
Figure 51.	Spectrum at the output of a non-linear device with an input of two equal amplitude sine waves of $f_1 = 2.001$ MHz and $f_2 = 2.003$	

	MHz.....	86
Figure 52.	Ideal grid-plate transfer curve for Class AB operation.....	88
Figure 53.	Block diagram of Intermodulation Distortion Analyzer. A low-distortion two-tone r-f signal is generated at 2 MHz and applied to the test amplifier. The output of the amplifier is dissipated in a dummy load and a portion of the output signal is examined on the screen of a high-resolution panoramic analyzer or tunable voltmeter. Distortion products as low as - 75 decibels below one tone of a	89
Figure 54.	Intermodulation distortion products may be predicted mathematically. This universal family of IMD curves applies to all perfect tubes obeying the 3/2-power law. (See Section 6.4.) The curves are plots of IMD level (Y axis) referred to the drivibias. As the drive is increased, the various IMD products pass through maxima and minima. Misleading conclusions of amplifier performance may be drawn if the equipment happens to be tested near a cusp on the IMD curve, where a particular product drops to an extremely low level. The whole operating range of the equipment must be examined to draw a true picture of IMD per 91	
Figure 55.	IM Distortion Test Data for EIMAC 4CX1500B (EC2 = 225V)	94
Figure 56.	IM Distortion Test Data for E1MAC 4CX1500B (EC2 = 250V) ..	94
Figure 57.	Wire neutralizing system.	99
Figure 58.	Push-pull grid neutralization, basic circuit.	100
Figure 59.	Single-ended grid neutralization described by Bruene, basic circuit.	100
Figure 60.	Single-ended plate neutralization, basic circuit.	101
Figure 61.	Single-ended plate neutralization showing capacitance bridge circuit present.....	102
Figure 62.	Neutralization of a symmetrical grid-excited amplifier by cross-connected capacitors.	104
Figure 63.	Neutralization by cross-connected capacitors of a symmetrical cathode-excited amplifier with grounded grids.....	104
Figure 64.	Neutralization by cross-connected capacitors of a symmetrical cathode-excited amplifier with compensation of lead inductance. .	105
Figure 65.	Circuit of grounded-grid amplifier having grid impedance and neutralized for reactive currents.....	106
Figure 66.	Tetrode characteristics involved in feedback circuit.	108
Figure 67.	Graphical presentation of components of output circuit voltages in tetrode when self neutralized.	108
Figure 68.	Components of output voltage of a tetrode when neutralized by added series screenlead capacitance.....	111
Figure 68A.	Components of output voltage of a tetrode when neutralized by added external grid-to-plate capacitance.	112
Figure 69.	Components of output voltage of a tetrode neutralized by adding inductance common to screen and cathode return.....	112
Figure 70.	Three-halves power of commonly-used factors.	117
Figure 71.	Plate-Current Pulse Length and Power Output of Harmonic Amplifiers.	120

Figure 72.	4.125A mounting providing cooling, shielding and isolation of output and input compartments.	129
Figure 73.	4CX250B chassis mounting providing cooling, shielding and isolation of output and input compartments.	129
Figure 74.	Incorrectly mounted tube. Submounted metal base shell tube prevents effective cooling and does not contribute to shielding.	130
Figure 75.	Measuring back-pressure.	131
Figure 76.	Cooling Airflow Requirements.	133
Figure 77.	Combined correction factors for land-based installations.	136
Figure 78.	Conversion of mass airflow rate to volumetric airflow rate.	137
Figure 79.	Typical vapor-phase cooling system.	142
Figure 80.	4CV35,000A tetrode mounted in BR-200 boiler.	143
Figure 81.	EIMAC vapor-cooled tubes for mounting in EIMAC Boilers.	143
Figure 82.	CB-202 control box.	145
Figure 83	Cutaway of "classic" boiler and tube combination (BR-101 boiler and 4CV8000A tetrode).	146
Figure 84.	Cutaway view of EIMAC Control Box showing position of float switches and overflow pipe.	146
Figure 85.	Typical 4-tube vapor cooling system with common water .. supply.	147
Figure 86.	Cutaway of pressure equalizer fitting.	148
Figure 87.	Typical 4-tube system using "steam-out-the-bottom" boilers.	149
Figure 88.	Cutaway view of "steam-out-the-bottom" boilers.	151
Figure 89.	Nukiyama heat transfer curves.	153
Figure 91.	Useful conversion factors.	156
Figure 92.	Different conduction cooled tubes manufactured by EIMAC.	157
Figure 93.	Variation in properties due to changes in temperature.	158
Figure 94.	Relative thermal conductivity of BeO.	158